

# AC STEADY-STATE ANALYSIS

## LEARNING GOALS

### SINUSOIDALS

Review basic facts about sinusoidal signals

### SINUSOIDAL AND COMPLEX FORCING FUNCTIONS

Behavior of circuits with sinusoidal independent sources and modeling of sinusoids in terms of complex exponentials

### PHASORS

Representation of complex exponentials as vectors. It facilitates steady-state analysis of circuits.

### IMPEDANCE AND ADMITANCE

Generalization of the familiar concepts of resistance and conductance to describe AC steady state circuit operation

### PHASOR DIAGRAMS


Representation of AC voltages and currents as complex vectors

### BASIC AC ANALYSIS USING KIRCHHOFF LAWS


### ANALYSIS TECHNIQUES

Extension of node, loop, Thevenin and other techniques

## SINUSOIDAL SIGNALS

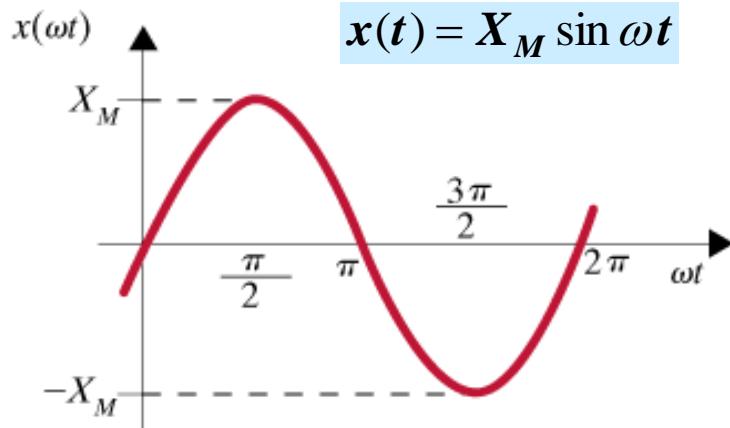

Adimensional plot

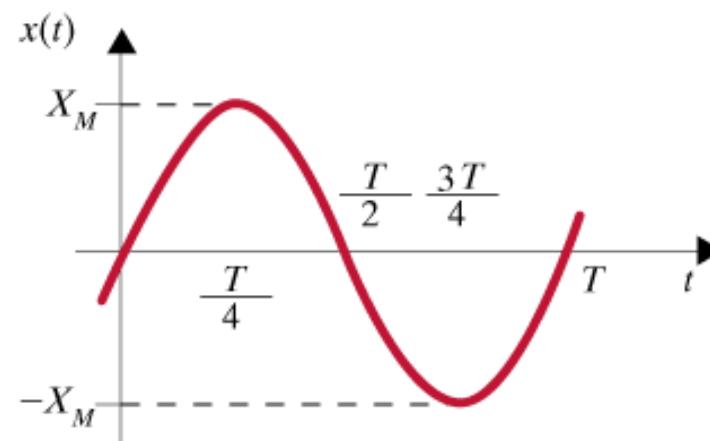


As function of time

$X_M$  = amplitude or maximum value  
 $\omega$  = angular frequency (rads/sec)  
 $\omega t$  = argument (radians)

$$T = \frac{2\pi}{\omega} = \text{Period} \Rightarrow x(t) = x(t + T), \forall t$$

$$f = \frac{1}{T} = \frac{\omega}{2\pi} = \text{frequency in Hertz (cycle/sec)}$$

$$\omega = 2\pi f$$

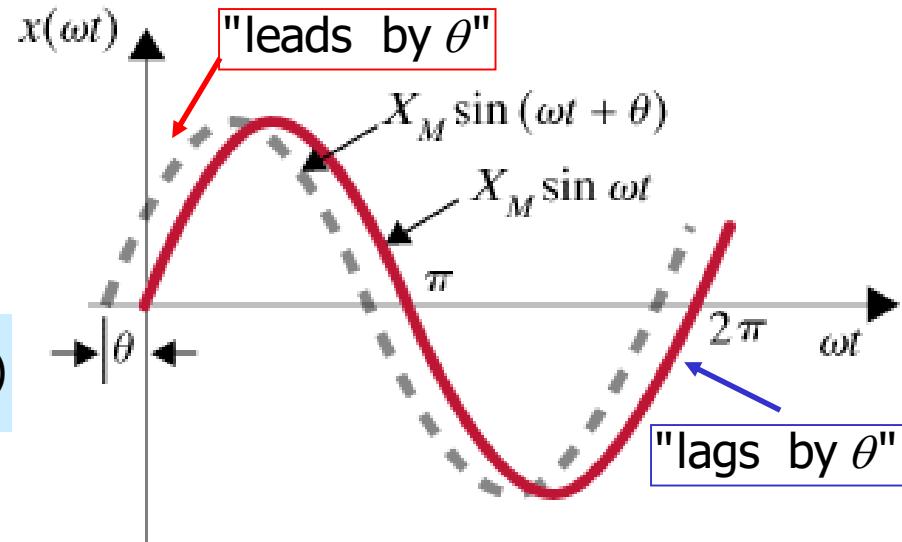

# BASIC TRIGONOMETRY (RECALL FROM HIGH SCHOOL)

## ESSENTIAL IDENTITIES

$$\sin(\alpha + \beta) = \sin \alpha \cos \beta + \cos \alpha \sin \beta$$

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$\sin(-\alpha) = -\sin \alpha$$

$$\cos(-\alpha) = \cos \alpha$$

## SOME DERIVED IDENTITIES

$$\sin(\alpha - \beta) = \sin \alpha \cos \beta - \cos \alpha \sin \beta$$

$$\cos(\alpha - \beta) = \cos \alpha \cos \beta + \sin \alpha \sin \beta$$

$$\sin \alpha \cos \beta = \frac{1}{2} \sin(\alpha + \beta) + \frac{1}{2} \sin(\alpha - \beta)$$

$$\cos \alpha \cos \beta = \frac{1}{2} \cos(\alpha + \beta) + \frac{1}{2} \cos(\alpha - \beta)$$

## RADIANS AND DEGREES

$$2\pi \text{ radians} = 360 \text{ degrees}$$

$$\theta(\text{rads}) = \frac{180}{\pi} \theta \text{ (degrees)}$$

## ACCEPTED EE CONVENTION

$$\sin(\omega t + \frac{\pi}{2}) = \sin(\omega t + 90^\circ)$$

## APPLICATIONS


$$\cos \omega t = \sin(\omega t + \frac{\pi}{2})$$

$$\sin \omega t = \cos(\omega t - \frac{\pi}{2})$$

$$\cos \omega t = -\cos(\omega t \pm \pi)$$

$$\sin \omega t = -\sin(\omega t \pm \pi)$$


## EXAMPLE 1

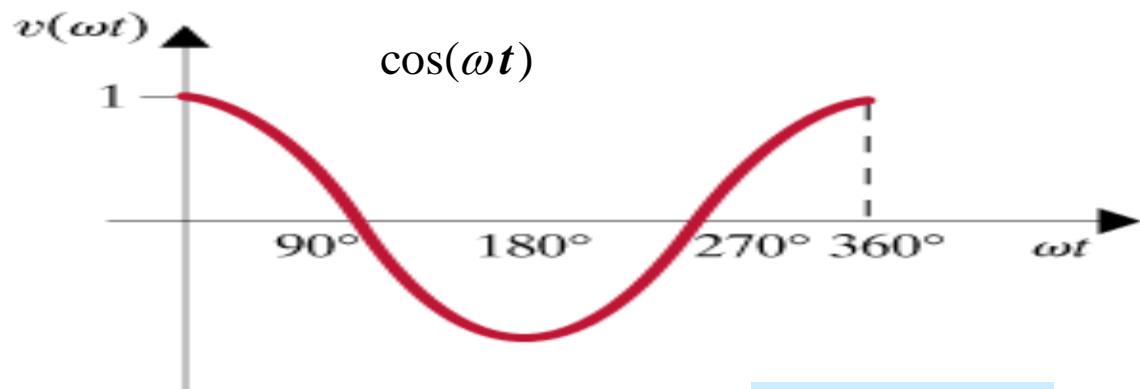

$$\begin{aligned} &\cos(\omega t + 45^\circ) \\ &\cos(\omega t + 45 - 360^\circ) \end{aligned}$$


Leads by 45 degrees

Lags by 315

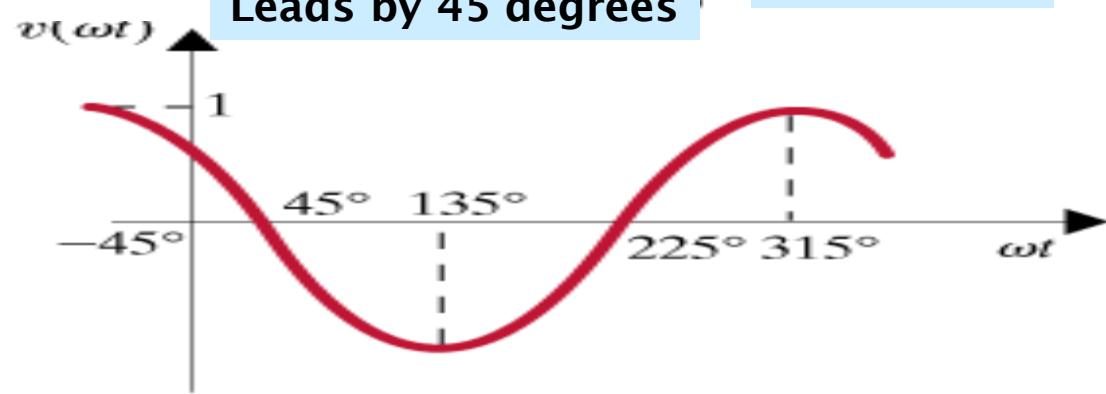

$$\begin{aligned} &-\cos(\omega t + 45^\circ) \\ &\cos(\omega t + 45^\circ \pm 180^\circ) \end{aligned}$$

Leads by 225 or lags by 135

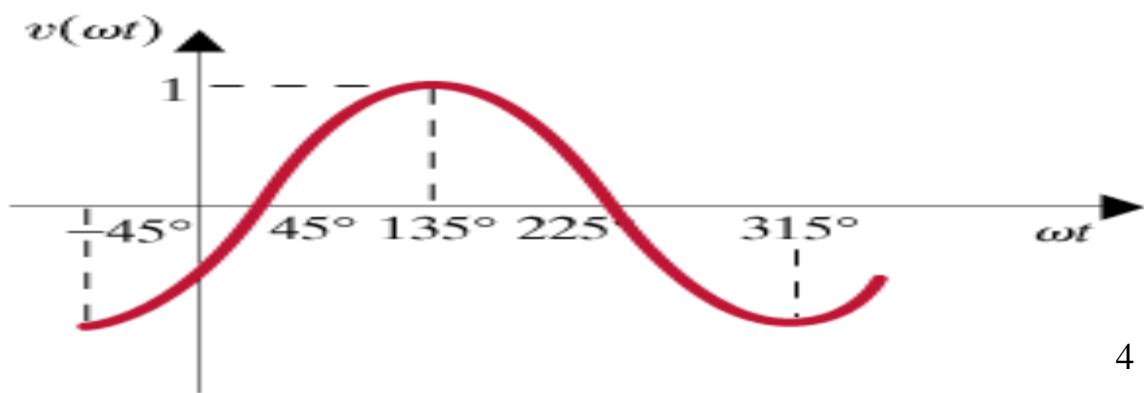

(c)

## EXAMPLE 2

$$v_1(t) = 12 \sin(1000t + 60^\circ), v_2(t) = -6 \cos(1000t + 30^\circ)$$

FIND FREQUENCY AND PHASE ANGLE BETWEEN VOLTAGES

Frequency in radians per second is the factor of the time variable

$$\omega = 1000 \text{ sec}^{-1}$$

$$f(\text{Hz}) = \frac{\omega}{2\pi} = 159.2 \text{ Hz}$$

To find phase angle we must express both sinusoids using the same trigonometric function; either sine or cosine with positive amplitude

take care of minus sign with  $\cos(\alpha) = -\cos(\alpha \pm 180^\circ)$

$$-6 \cos(1000t + 30^\circ) = 6 \cos(1000t + 30^\circ + 180^\circ)$$

Change sine into cosine with  $\cos(\alpha) = \sin(\alpha + 90^\circ)$

$$6 \cos(1000t + 210^\circ) = 6 \sin(1000t + 210^\circ + 90^\circ)$$

We like to have the phase shifts less than 180 in absolute value

$$6 \sin(1000t + 300^\circ) = 6 \sin(1000t - 60^\circ)$$

$$v_1(t) = 12 \sin(1000t + 60^\circ)$$

$$(1000t + 60^\circ) - (1000t - 60^\circ) = 120^\circ$$

$v_1$  leads  $v_2$  by 120°

$$v_2(t) = 6 \sin(1000t - 60^\circ)$$

$$(1000t - 60^\circ) - (1000t + 60^\circ) = -120^\circ$$

$v_2$  lags  $v_1$  by 120°

## EXAMPLE 3

$$i_1(t) = 2 \sin(377t + 45^\circ)$$

$$i_2(t) = 0.5 \cos(377t + 10^\circ)$$

$$i_3(t) = -0.25 \sin(377t + 60^\circ)$$

$i_1$  leads  $i_2$  by \_\_\_\_\_?

$i_1$  leads  $i_3$  by \_\_\_\_\_?

$$\cos \alpha = \sin(\alpha + 90^\circ)$$

$$0.5 \cos(377t + 10^\circ) = 0.5 \sin(377t + 10^\circ + 90^\circ)$$

$$(377t + 45^\circ) - (377t + 100^\circ) = -55^\circ$$

$i_1$  leads  $i_2$  by  $-55^\circ$


$$\sin \alpha = -\sin(\alpha \pm 180^\circ)$$

$$-0.25 \sin(377t + 60^\circ) = 0.25 \sin(377t + 60^\circ - 180^\circ)$$

$$(377t + 45^\circ) - (377t - 120^\circ) = 165^\circ$$

$i_1$  leads  $i_3$  by  $165^\circ$
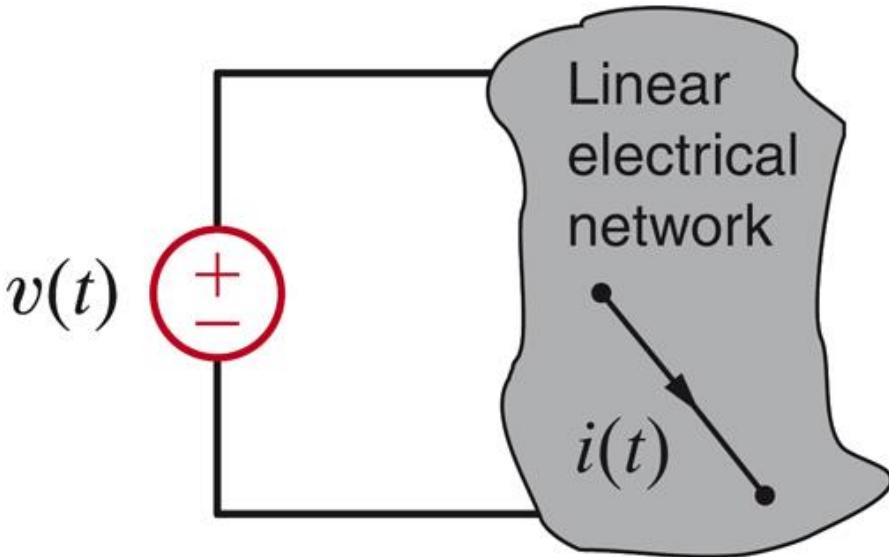
## SINUSOIDAL AND COMPLEX FORCING FUNCTIONS



If the independent sources are sinusoids of the same frequency then for any variable in the linear circuit the steady state response will be sinusoidal and of the same frequency


$$v(t) = A \sin(\omega t + \theta) \Rightarrow i_{ss}(t) = B \sin(\omega t + \phi)$$

To determine the steady state solution we only need to determine the parameters  $B, \phi$
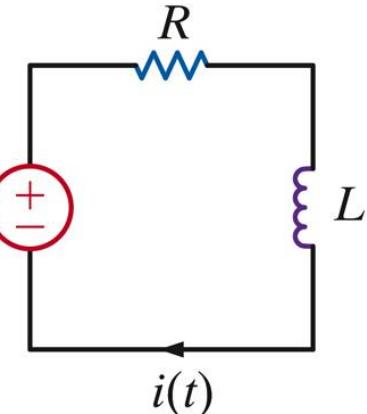
### Example 4

$$v(t) = V_M \cos \omega t$$

$$\text{KVL: } L \frac{di}{dt}(t) + R i(t) = v(t)$$



In steady state  $i(t) = A \cos(\omega t + \phi)$ , or

$$i(t) = A_1 \cos \omega t + A_2 \sin \omega t \quad */R$$

$$\frac{di}{dt}(t) = -A_1 \omega \sin \omega t + A_2 \omega \cos \omega t \quad */L$$

$$(-L\omega A_1 + RA_2) \sin \omega t + (L\omega A_2 + RA_1) \cos \omega t = \\ = V_M \cos \omega t$$

$$-L\omega A_1 + RA_2 = 0 \quad \text{algebraic problem}$$

$$L\omega A_2 + RA_1 = V_M$$

$$A_1 = \frac{RV_M}{R^2 + (\omega L)^2}, \quad A_2 = \frac{\omega LV_M}{R^2 + (\omega L)^2}$$

Determining the steady state solution can be accomplished with only algebraic tools!

## FURTHER ANALYSIS OF THE SOLUTION

The solution is  $i(t) = A_1 \cos \omega t + A_2 \sin \omega t$

The applied voltage is  $v(t) = V_M \cos \omega t$

For comparison purposes one can write  $i(t) = A \cos(\omega t + \phi)$

$$A_1 = A \cos \phi, \quad A_2 = -A \sin \phi \quad A = \sqrt{A_1^2 + A_2^2}, \quad \tan \phi = -\frac{A_2}{A_1}$$

$$A_1 = \frac{RV_M}{R^2 + (\omega L)^2}, \quad A_2 = \frac{\omega LV_M}{R^2 + (\omega L)^2}$$

$$A = \frac{V_M}{\sqrt{R^2 + (\omega L)^2}}, \quad \varphi = \tan^{-1} \frac{\omega L}{R}$$

$$i(t) = \frac{V_M}{\sqrt{R^2 + (\omega L)^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

For  $L \neq 0$  the current ALWAYS lags the voltage


If  $R = 0$  (pure inductor) the current lags the voltage by  $90^\circ$

SOLVING A SIMPLE ONE LOOP CIRCUIT CAN BE VERY LABORIOUS  
IF ONE USES SINUSOIDAL EXCITATIONS

TO MAKE ANALYSIS SIMPLER ONE RELATES SINUSOIDAL SIGNALS  
TO COMPLEX NUMBERS. THE ANALYSIS OF STEADY STATE WILL BE  
CONVERTED TO SOLVING SYSTEMS OF ALGEBRAIC EQUATIONS ...

... WITH COMPLEX VARIABLES

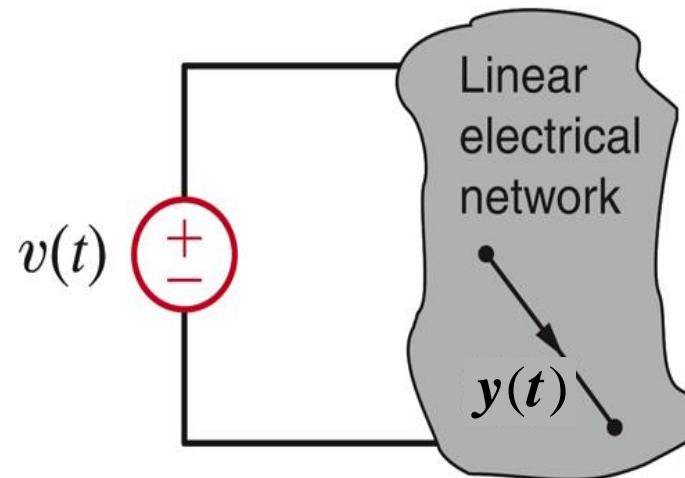ESSENTIAL IDENTITY:  $e^{j\theta} = \cos\theta + j\sin\theta$  (Euler identity)



$$v(t) = V_M \cos \omega t \rightarrow y(t) = A \cos(\omega t + \theta)$$


$$v(t) = V_M \sin \omega t \rightarrow y(t) = A \sin(\omega t + \theta) \quad */ j \text{ (and add)}$$

$$V_M e^{j\omega t} \rightarrow A e^{j(\omega t + \theta)} = A e^{j\theta} e^{j\omega t}$$

If everybody knows the frequency of the sinusoid  
then one can skip the term  $\exp(j\omega t)$

$$V_M \rightarrow A e^{j\theta}$$

## Example 5

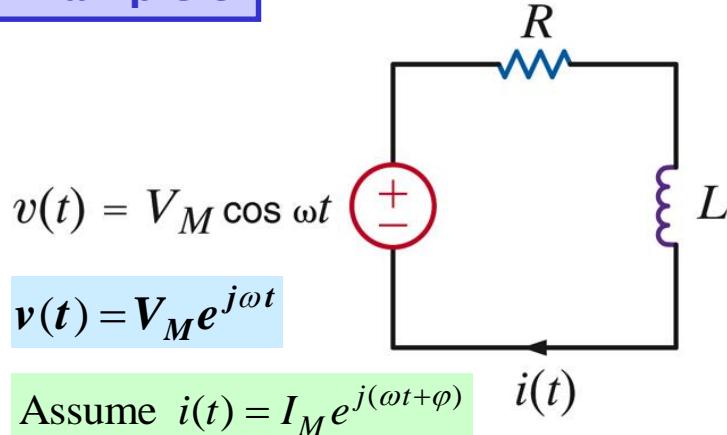

KVL:  $L \frac{di}{dt}(t) + Ri(t) = v(t)$

$$\frac{di}{dt}(t) = j\omega I_M e^{j(\omega t + \phi)}$$

$$\begin{aligned} L \frac{di}{dt}(t) + Ri(t) &= j\omega L I_M e^{j(\omega t + \phi)} + RI_M e^{j(\omega t + \phi)} \\ &= (j\omega L + R)I_M e^{j(\omega t + \phi)} \\ &= (j\omega L + R)I_M e^{j\phi} e^{j\omega t} \end{aligned}$$

$$(j\omega L + R)I_M e^{j\phi} e^{j\omega t} = V_M e^{j\omega t}$$

$$I_M e^{j\phi} = \frac{V_M}{j\omega L + R} * / \frac{R - j\omega L}{R - j\omega L}$$

$$I_M e^{j\phi} = \frac{V_M (R - j\omega L)}{R^2 + (\omega L)^2}$$

$$R - j\omega L = \sqrt{R^2 + (\omega L)^2} e^{-\tan^{-1} \frac{\omega L}{R}}$$

$$I_M e^{j\phi} = \frac{V_M}{\sqrt{R^2 + (\omega L)^2}} e^{-\tan^{-1} \frac{\omega L}{R}}$$

$$I_M = \frac{V_M}{\sqrt{R^2 + (\omega L)^2}}, \quad \phi = -\tan^{-1} \frac{\omega L}{R}$$

$$\begin{aligned} v(t) &= V_M \cos \omega t = \operatorname{Re}\{V_M e^{j\omega t}\} \\ \Rightarrow i(t) &= \operatorname{Re}\{I_M e^{(j\omega t - \phi)}\} = I_M \cos(\omega t - \phi) \end{aligned}$$

$C \leftrightarrow P$

$$x + jy = r e^{j\theta}$$

$$r = \sqrt{x^2 + y^2}, \quad \theta = \tan^{-1} \frac{y}{x}$$

$$x = r \cos \theta, \quad y = r \sin \theta$$

# PHASORS

ESSENTIAL CONDITION

ALL INDEPENDENT SOURCES ARE SINUSOIDS OF THE SAME FREQUENCY

BECAUSE OF SOURCE SUPERPOSITION ONE CAN CONSIDER A SINGLE SOURCE

$$u(t) = U_M \cos(\omega t + \theta)$$

THE STEADY STATE RESPONSE OF ANY CIRCUIT VARIABLE WILL BE OF THE FORM

$$y(t) = Y_M \cos(\omega t + \phi)$$

SHORTCUT 1

$$u(t) = U_M e^{j(\omega t + \theta)} \Rightarrow y(t) = Y_M e^{j(\omega t + \phi)}$$

$$\text{Re}\{U_M e^{j(\omega t + \theta)}\} \Rightarrow \text{Re}\{Y_M e^{j(\omega t + \phi)}\}$$

NEW IDEA:

$$U_M e^{j(\omega t + \theta)} = U_M e^{j\theta} e^{j\omega t} \quad u = U_M e^{j\theta} \Rightarrow y = Y_M e^{j\phi}$$

SHORTCUT IN NOTATION

INSTEAD OF WRITING  $u = U_M e^{j\theta}$  WE WRITE  $u = U_M \angle \theta$


... AND WE ACCEPT ANGLES IN DEGREES

$U_M \angle \theta$  IS THE PHASOR REPRESENTATION FOR  $U_M \cos(\omega t + \theta)$

$$u(t) = U_M \cos(\omega t + \theta) \rightarrow U = U_M \angle \theta \Rightarrow Y = Y_M \angle \phi \rightarrow y(t) = Y_M \cos(\omega t + \phi)$$

SHORTCUT 2: DEVELOP EFFICIENT TOOLS TO DETERMINE THE PHASOR OF THE RESPONSE GIVEN THE INPUT PHASOR(S)

## Example 6

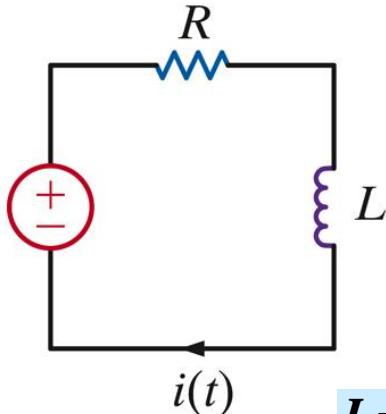

$$v(t) = V_M \cos \omega t$$

$$V = V_M \angle 0$$

$$v = V e^{j\omega t}$$

$$L \frac{di}{dt}(t) + Ri(t) = v$$

$$L(j\omega I e^{j\omega t}) + RI e^{j\omega t} = V e^{j\omega t}$$

In terms of phasors one has

$$j\omega LI + RI = V$$

$$I = \frac{V}{R + j\omega L}$$

The phasor can be obtained using only complex algebra

We will develop a phasor representation for the circuit that will eliminate the need of writing the differential equation

## Learning Extensions

**It is essential to be able to move from sinusoids to phasor representation**

$$A \cos(\omega t \pm \theta) \leftrightarrow A \angle \pm \theta$$

$$A \sin(\omega t \pm \theta) \leftrightarrow A \angle \pm \theta - 90^\circ$$

$$v(t) = 12 \cos(377t - 425^\circ) \leftrightarrow 12 \angle -425^\circ$$

$$y(t) = 18 \sin(2513t + 4.2^\circ) \leftrightarrow 18 \angle -85.8^\circ$$

Given  $f = 400 \text{ Hz}$

$$V_1 = 10 \angle 20^\circ \leftrightarrow v_1(t) = 10 \cos(800\pi t + 20^\circ)$$

$$V_2 = 12 \angle -60^\circ \leftrightarrow v_2(t) = 12 \cos(800\pi t - 60^\circ)$$

**Phasors can be combined using the rules of complex algebra**

$$(V_1 \angle \theta_1)(V_2 \angle \theta_2) = V_1 V_2 \angle (\theta_1 + \theta_2)$$

$$\frac{V_1 \angle \theta_1}{V_2 \angle \theta_2} = \frac{V_1}{V_2} \angle (\theta_1 - \theta_2)$$

# PHASOR RELATIONSHIPS FOR CIRCUIT ELEMENTS

## RESISTORS



$$v(t) = Ri(t)$$

$$V_M e^{j(\omega t + \theta)} = RI_M e^{j(\omega t + \theta)}$$


$$V_M e^{j\theta} = RI_M e^{j\theta}$$

$$V = RI$$

Phasor representation for a resistor

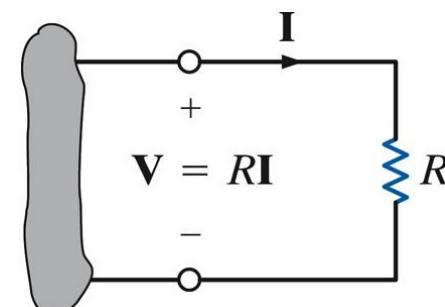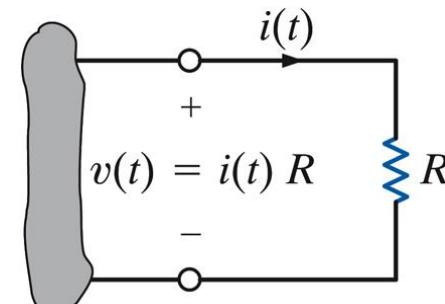


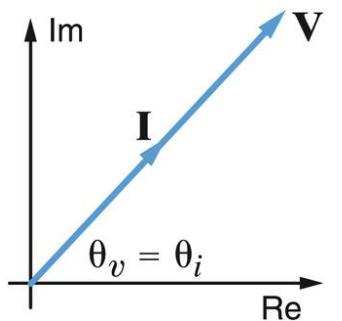Phasors are complex numbers. The resistor model has a geometric interpretation




The voltage and current phasors are colinear

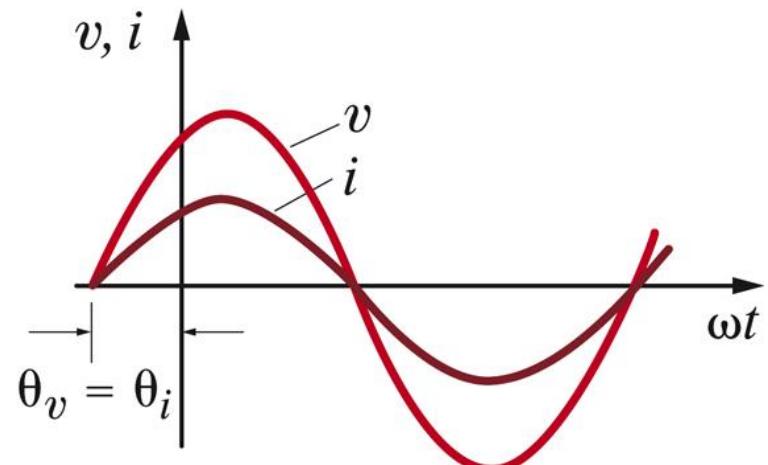In terms of the sinusoidal signals this geometric representation implies that the two sinusoids are “in phase”




## INDUCTORS

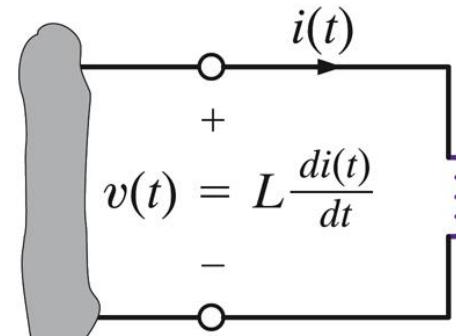

$$V = j\omega LI$$

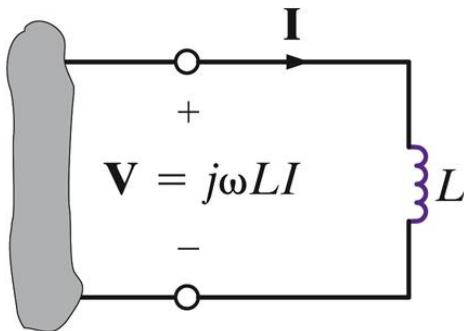
$$\begin{aligned} V_M e^{j(\omega t + \theta)} &= L \frac{d}{dt} (I_M e^{j(\omega t + \phi)}) \\ &= j\omega L I_M e^{j(\omega t + \phi)} \\ V_M e^{j\theta} &= j\omega L I_M e^{j\phi} \end{aligned}$$



The relationship between phasors is algebraic


For the geometric view use the result
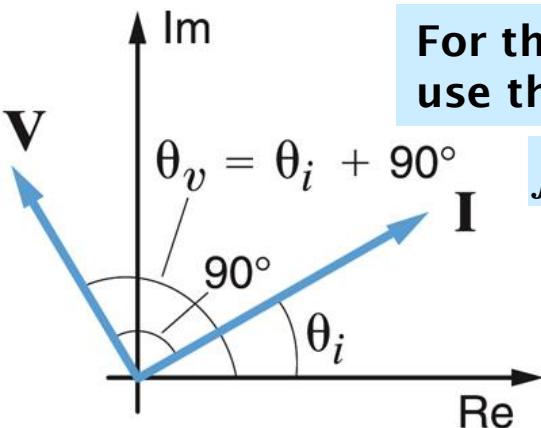
$$\begin{aligned} j &= 1 \angle 90^\circ = e^{j90^\circ} \\ V &= \omega L I \angle 90^\circ \end{aligned}$$



The voltage leads the current by 90 deg  
The current lags the voltage by 90 deg

## Relationship between sinusoids

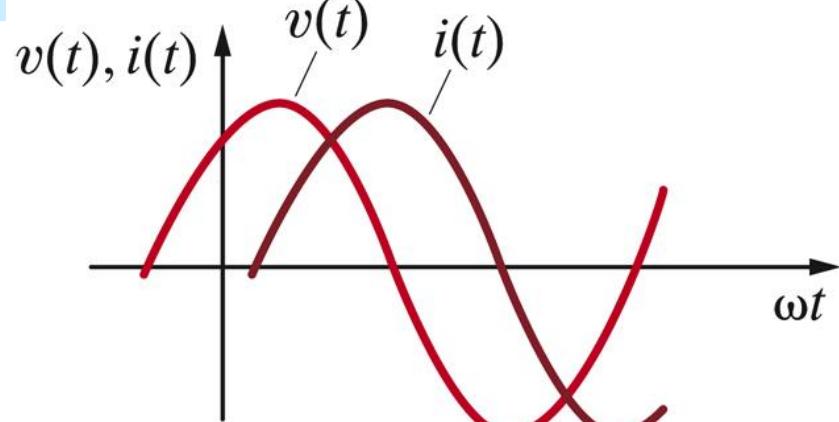

### Learning Example

$L = 20mH, v(t) = 12\cos(377t + 20^\circ)$ . Find  $i(t)$

$$\omega = 377$$

$$V = 12\angle 20^\circ$$

$$I = \frac{V}{j\omega L}$$


$$I = \frac{12}{\omega L \angle 90^\circ} (A)$$

$$I = \frac{12}{377 \times 20 \times 10^{-3}} \angle -70^\circ (A)$$


$$i(t) = \frac{12}{377 \times 20 \times 10^{-3}} \cos(377t - 70^\circ)$$

$$i(t) = 1.592 \cos(377t - 70^\circ), A$$

## CAPACITORS

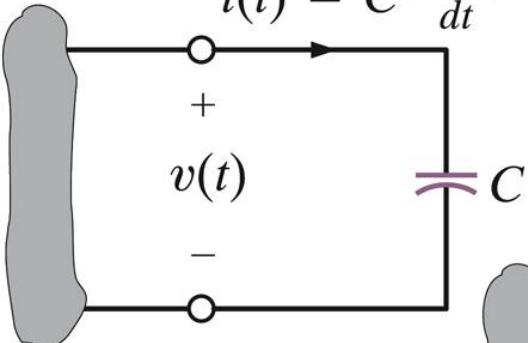

$$I = j\omega CV$$

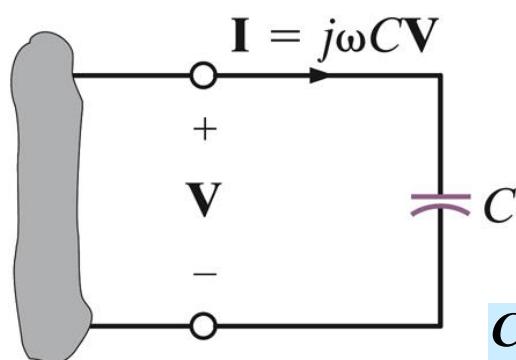


$$I = \omega CV \angle 90^\circ$$

The relationship between phasors is algebraic

In a capacitor the current leads the voltage by 90 deg


The voltage lags the current by 90 deg

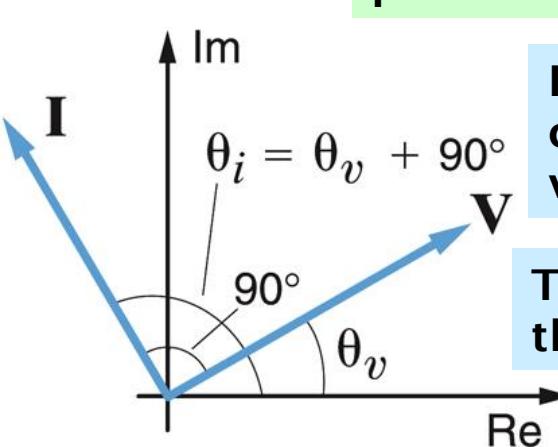

$$I_M e^{j(\omega t + \phi)} = C \frac{d}{dt} (V_M e^{j(\omega t + \theta)})$$

$$I_M e^{j\phi} = j\omega C V_M e^{j\theta}$$

## Relationship between sinusoids

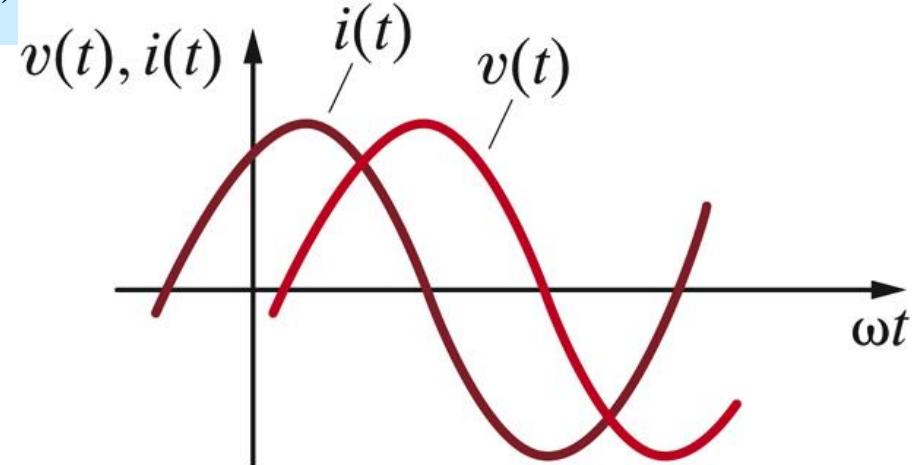

### Example 7

$$C = 100\mu F, v(t) = 100\cos(314t + 15^\circ). \text{ Find } i(t)$$

$$\omega = 314$$

$$V = 100 \angle 15^\circ$$

$$I = j\omega CV$$

$$I = 314 \times 100 \times 10^{-6} \times 100 \angle 105^\circ (\text{A})$$

$$i(t) = 3.14 \cos(314t + 105^\circ) (\text{A})$$

### Example 8

$$L = 0.05 \text{ H}, I = 4 \angle -30^\circ (\text{A}), f = 60 \text{ Hz}$$

Find the voltage across the inductor

$$\omega = 2\pi f = 120\pi$$

$$V = j\omega LI$$

$$V = 120\pi \times 0.05 \times 1 \angle 90^\circ \times 4 \angle -30^\circ$$

$$V = 24\pi \angle 60^\circ$$

$$v(t) = 24\pi \cos(120\pi t + 60^\circ)$$

### Example 9

$$C = 150 \mu F, I = 3.6 \angle -145^\circ, f = 60 \text{ Hz}$$

Find the voltage across the inductor

$$\omega = 2\pi f = 120\pi$$

$$I = j\omega CV \Rightarrow V = \frac{I}{j\omega C}$$


$$V = \frac{3.6 \angle -145^\circ}{120\pi \times 150 \times 10^{-6} \times 1 \angle 90^\circ}$$

$$V = \frac{200}{\pi} \angle -235^\circ$$

$$v(t) = \frac{200}{\pi} \cos(120\pi t - 235^\circ)$$
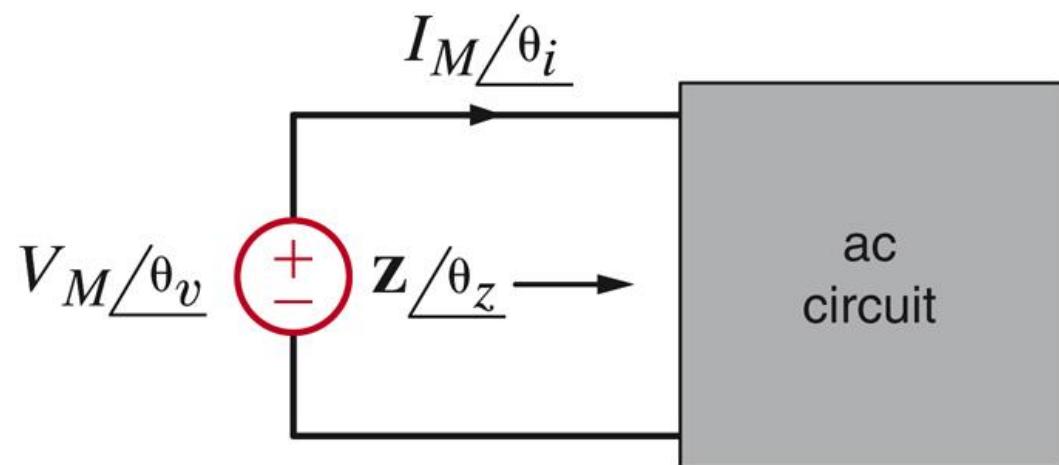
## IMPEDANCE AND ADMITTANCE

For each of the passive components the relationship between the voltage phasor and the current phasor is algebraic. We now generalize for an arbitrary 2-terminal element



$$Z(\omega) = R(\omega) + jX(\omega)$$

$R(\omega)$ =Resistive component

$X(\omega)$ =Reactive component

$$|Z| = \sqrt{R^2 + X^2}$$

$$\theta_z = \tan^{-1} \frac{X}{R}$$

### (INPUT) IMPEDANCE

$$Z = \frac{V}{I} = \frac{V_M \angle \theta_v}{I_M \angle \theta_i} = \frac{V_M}{I_M} \angle (\theta_v - \theta_i) = |Z| \angle \theta_z$$

### (DRIVING POINT IMPEDANCE)


The units of impedance are OHMS

### Element Phasor Eq. Impedance

$R$	$V = RI$	$Z = R$
$L$	$V = j\omega LI$	$Z = j\omega L$
$C$	$V = \frac{1}{j\omega C} I$	$Z = \frac{1}{j\omega C}$


Impedance is NOT a phasor but a complex number that can be written in polar or Cartesian form. In general its value depends on the frequency
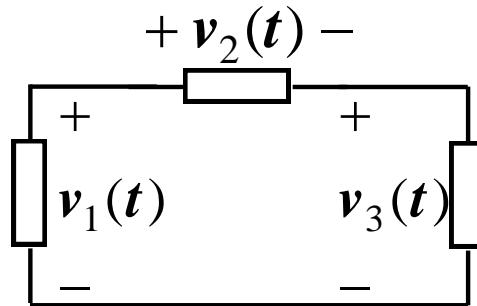
## KVL AND KCL HOLD FOR PHASOR REPRESENTATIONS



$$\text{KVL: } v_1(t) + v_2(t) + v_3(t) = 0$$
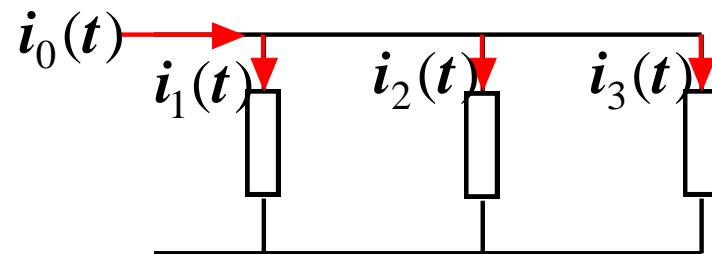
$$v_i(t) = V_{Mi} e^{j(\omega t + \theta_i)}, i = 1, 2, 3$$




$$\text{KCL: } -i_0(t) + i_1(t) + i_2(t) + i_3(t) = 0$$

$$i_k(t) = I_{Mk} e^{j(\omega t + \phi_k)}, k = 0, 1, 2, 3$$

$$\text{KVL: } (V_{M1} e^{j\theta_1} + V_{M2} e^{j\theta_2} + V_{M3} e^{j\theta_3}) e^{j\omega t} = 0$$


$$V_{M1} \angle \theta_1 + V_{M2} \angle \theta_2 + V_{M3} \angle \theta_3 = 0$$
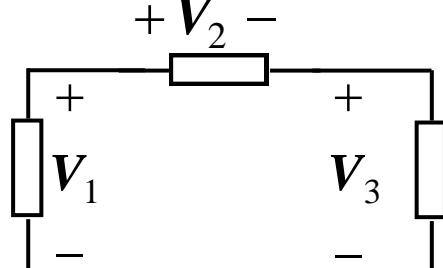
$$V_1 + V_2 + V_3 = 0 \quad \text{Phasors!}$$




In a similar way, one shows ...

$$-I_0 + I_1 + I_2 + I_3 = 0$$

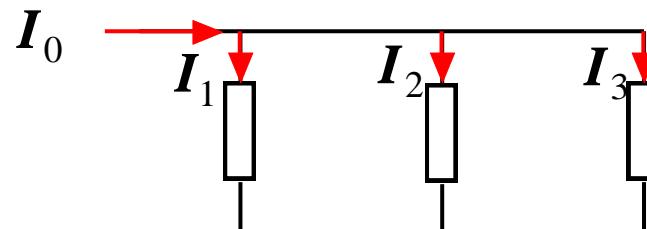


The components will be represented by their impedances and the relationships will be entirely algebraic!!

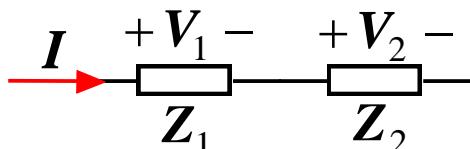
## SPECIAL APPLICATION: IMPEDANCES CAN BE COMBINED USING THE SAME RULES DEVELOPED FOR RESISTORS



$$Z_s = \sum_k Z_k$$

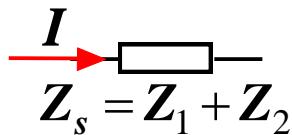

$$Z_s = Z_1 + Z_2$$

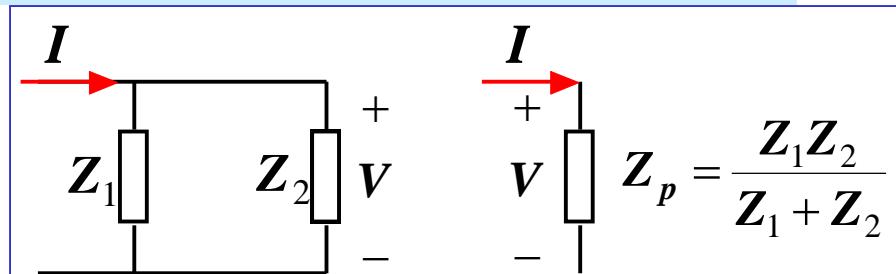


$$\frac{1}{Z_p} = \sum_k \frac{1}{Z_k}$$

$$Z_p = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

### EXAMPLE 1

$$f = 60\text{Hz}, v(t) = 50\cos(\omega t + 30^\circ)$$

Compute equivalent impedance and current

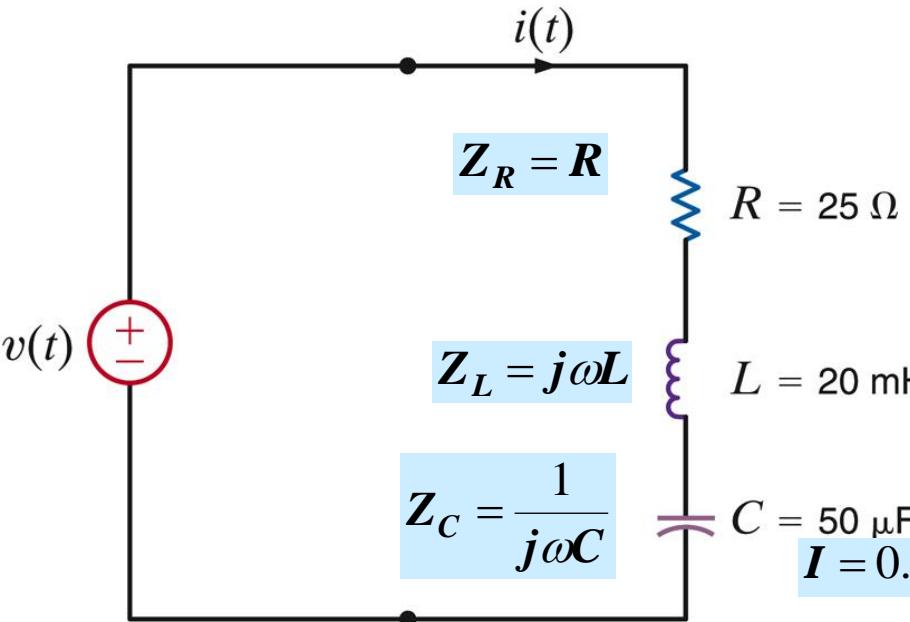

$$\omega = 120\pi, V = 50\angle 30^\circ, Z_R = 25\Omega$$


$$Z_L = j120\pi \times 20 \times 10^{-3} \Omega, Z_C = \frac{1}{j120\pi \times 50 \times 10^{-6}}$$

$$Z_L = j7.54\Omega, Z_C = -j53.05\Omega$$

$$Z_s = Z_R + Z_L + Z_C = 25 - j45.51\Omega$$

$$I = \frac{V}{Z_s} = \frac{50\angle 30^\circ}{25 - j45.51} (A) = \frac{50\angle 30^\circ}{51.93\angle -61.22^\circ} (A)$$

$$I = 0.96\angle 91.22^\circ (A) \Rightarrow i(t) = 0.96 \cos(120\pi t + 91.22^\circ) (A)$$

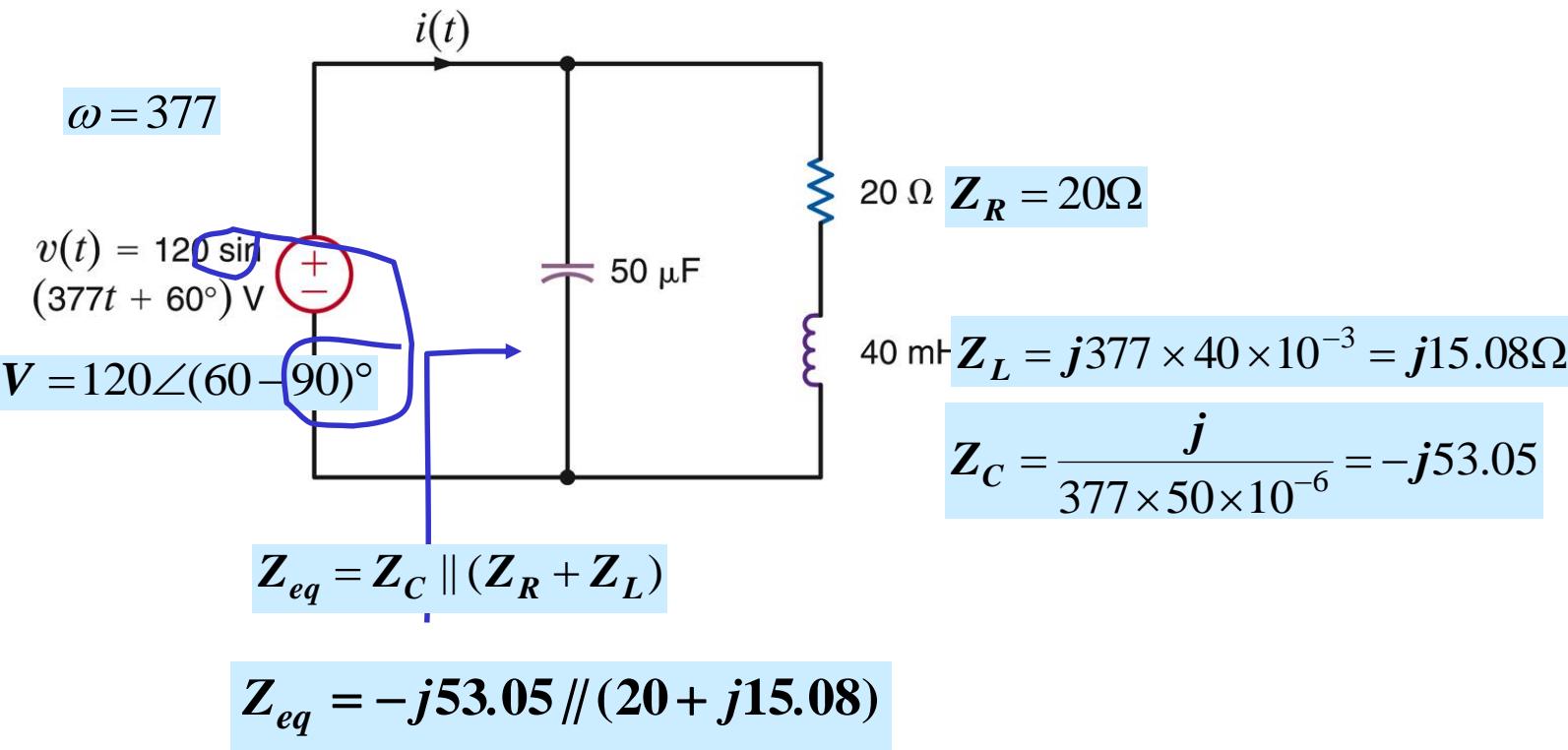**EXAMPLE 2**
**FIND  $i(t)$** 


$$\mathbf{Z}_{eq} = 30.5616 + j4.9714 = 30.963 \angle 9.239^\circ$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_{eq}} = \frac{120 \angle -30^\circ}{30.963 \angle 9.239^\circ} = 3.876 \angle -39.924^\circ (\text{A})$$

## (COMPLEX) ADMITTANCE

$$Y = \frac{1}{Z} = G + jB \text{ (Siemens)}$$

**G** = conductance

**B** = Susceptance

$$\frac{1}{Z} = \frac{1}{R+jX} \times \frac{R-jX}{R-jX} = \frac{R-jX}{R^2+X^2}$$

$$G = \frac{R}{R^2+X^2}$$

$$B = \frac{-X}{R^2+X^2}$$

Element Phasor Eq. Impedance Admittance

$$R \quad V = RI \quad Z = R$$


$$L \quad V = j\omega LI \quad Z = j\omega L$$

$$C \quad V = \frac{1}{j\omega C} I \quad Z = \frac{1}{j\omega C}$$

## Parallel Combination of Admittances

$$Y_p = \sum_k Y_k$$

$$Y_R = 0.1 S$$

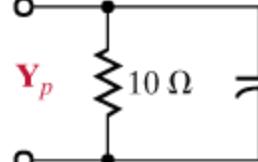


$$Y_C = \frac{1}{-j1} = j1(S)$$

$$Y_p = 0.1 + j1(S)$$

## Series Combination of Admittances

$$\frac{1}{Y_s} = \sum_k \frac{1}{Y_k}$$

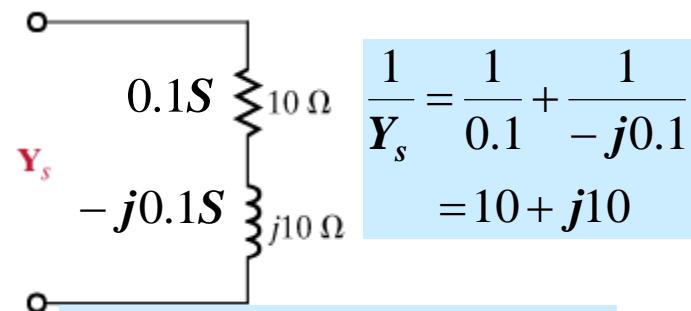

$$\begin{aligned} \frac{1}{Y_s} &= \frac{1}{0.1} + \frac{1}{-j0.1} \\ &= 10 + j10 \end{aligned}$$


$$Y_s = \frac{(0.1)(-j0.1)}{0.1 - j0.1} \times \frac{0.1 + j0.1}{0.1 + j0.1}$$

$$Y_s = \frac{1}{10 + j10} = \frac{10 - j10}{200}$$

$$Y_s = 0.05 - j0.05 S \quad 21$$

**EXAMPLE 3**

$$V_S = 60 \angle 45^\circ (V)$$

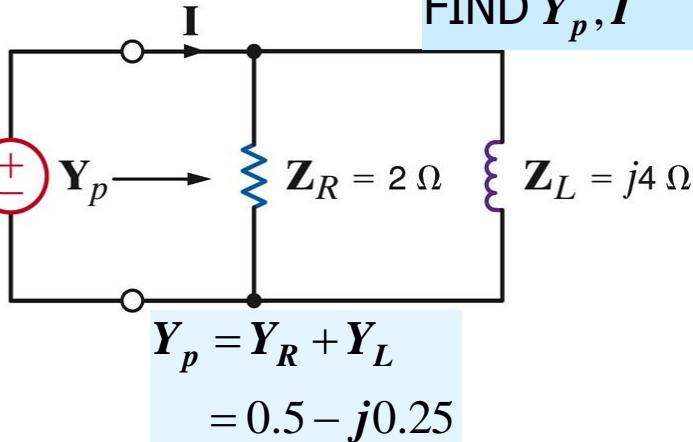**FIND  $Y_p, I$** 


$$Z_p = \frac{2 \times j4}{2 + j4} \quad Y_p = \frac{2 + j4}{j8} = 0.5 - j0.25(S)$$


$$I = Y_p V = (0.5 - j0.25) \times 60 \angle 45^\circ (A)$$

$$I = 0.559 \angle -26.565^\circ \times 60 \angle 45^\circ (A)$$

$$I = 33.54 \angle 18.435^\circ (A)$$

**EXAMPLE 4**

$$V = 10 \angle 20^\circ V$$

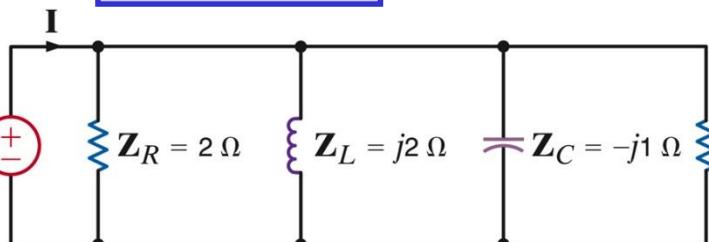

$$Y_p = 0.5 - j0.5 + j1 + 0.25 = 0.75 + j0.5(S)$$


$$Y_p = 0.9014 \angle 33.69^\circ (S)$$

$$I = Y_p V = 0.9014 \angle 33.69^\circ \times 10 \angle 20^\circ$$

$$I = 9.014 \angle 53.79^\circ (A)$$




## EXAMPLE 5

## SERIES-PARALLEL REDUCTIONS

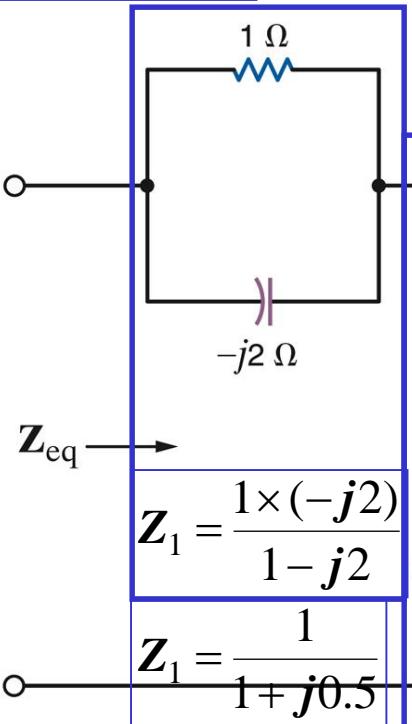

$$Z_1 = \frac{1 - j0.5}{1 + (0.5)^2}$$

$$Z_1 = 0.8 - j0.4(\Omega)$$

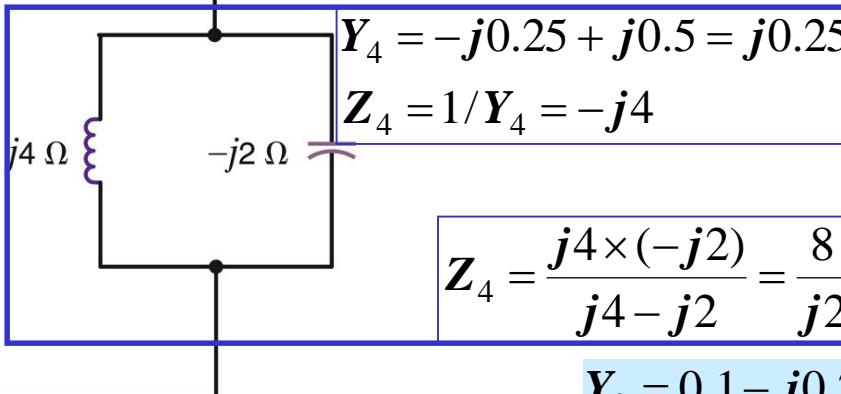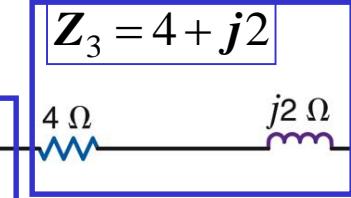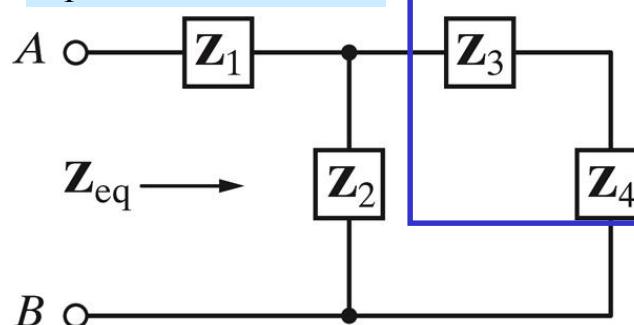

$$Y_2 = \frac{1}{2 + j4} = \frac{2 - j4}{(2)^2 + (4)^2}$$

$$Y_{34} = \frac{1}{4 - j2} = \frac{4 + j2}{20}$$

$$Y_2 = 0.1 - j0.2(S)$$

$$Y_{34} = 0.2 + j0.1$$

$$Y_{234} = 0.3 - j0.1(S)$$

$$Z_{234} = \frac{1}{Y_{234}} = \frac{1}{0.3 - j0.1} = \frac{0.3 + j0.1}{0.1}$$


$$Z_{234} = \frac{Z_2 Z_{34}}{Z_2 + Z_{34}}$$

$$= 3 + j1$$

$$Z_{eq} = Z_1 + Z_{234} = 3.8 + j0.6\Omega = 3.847 \angle 8.973^\circ$$

## EXAMPLE 6

### FIND THE IMPEDANCE $Z_T$

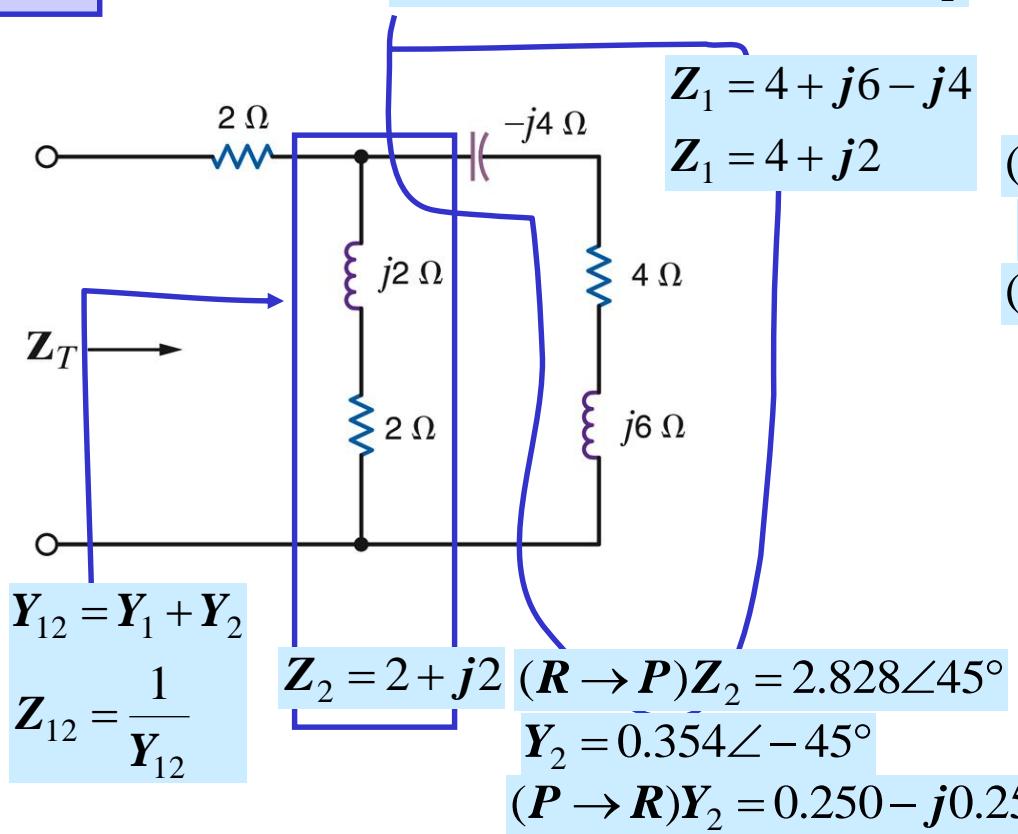

$$Y_1 = \frac{1}{4+j2} = \frac{4-j2}{(4)^2+(2)^2}$$

$$Y_2 = \frac{1}{2+j2} = \frac{2-j2}{(2)^2+(2)^2}$$

$$Z_{12} = \frac{1}{Y_{12}} = \frac{1}{0.45-j0.35} = \frac{0.45+j0.35}{0.325}$$

$$(R \rightarrow P)Z_1 = 4.472 \angle 26.565^\circ$$

$$Y_1 = 0.224 \angle -26.565^\circ$$

$$(P \rightarrow R)Y_1 = 0.200 - j0.100$$

$$Y_{12} = Y_1 + Y_2 = 0.45 - j0.35$$

$$(R \rightarrow P)Y_{12} = 0.570 \angle -37.875^\circ$$

$$Z_{12} = 1.754 \angle 37.875^\circ$$

$$(P \rightarrow R)Z_{12} = 1.384 + j1.077$$

$$Z_T = 2 + (1.384 + j1.077) = 3.383 + j1.077$$


# PHASOR DIAGRAMS

Display all relevant phasors on a common reference frame

Very useful to visualize phase relationships among variables.  
Especially if some variable, like the frequency, can change

## EXAMPLE 1
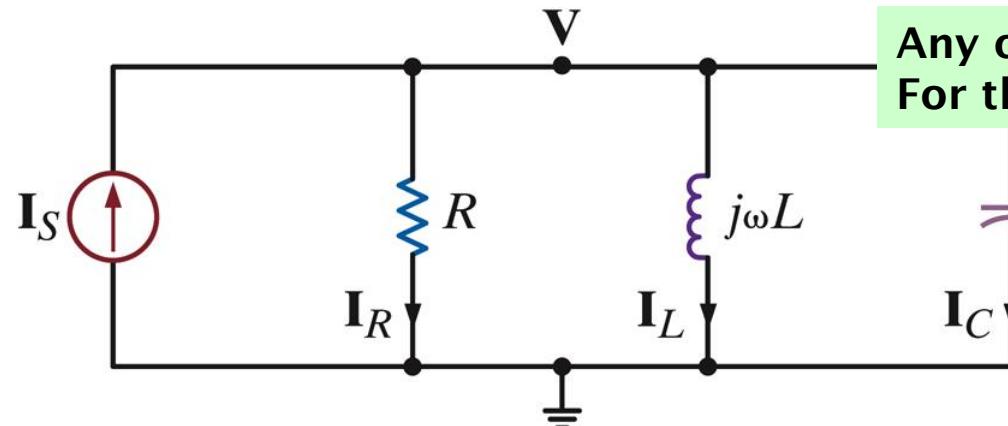
### SKETCH THE PHASOR DIAGRAM FOR THE CIRCUIT




Any one variable can be chosen as reference.  
For this case select the voltage  $V$


$$\text{KCL: } I_S = \frac{V}{R} + \frac{V}{j\omega L} + j\omega CV$$

$$I_C = j\omega CV$$


$$I_L = \frac{V}{j\omega L}$$

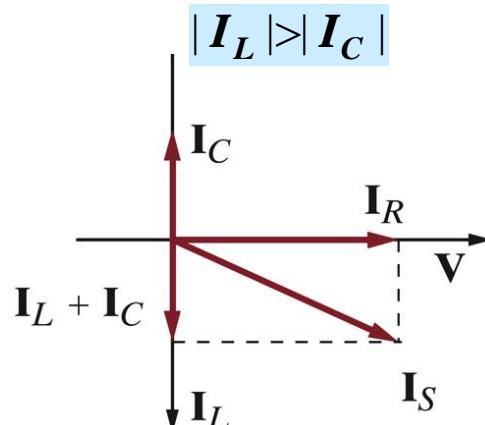

INDUCTIVE CASE

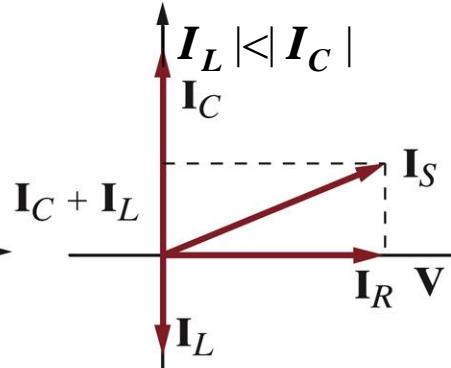


CAPACITIVE CASE

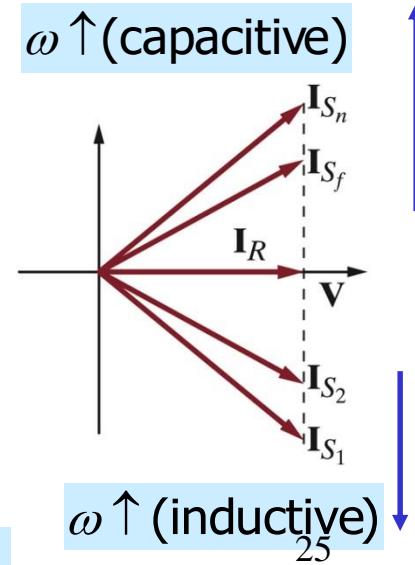


## EXAMPLE 2

## DO THE PHASOR DIAGRAM FOR THE CIRCUIT

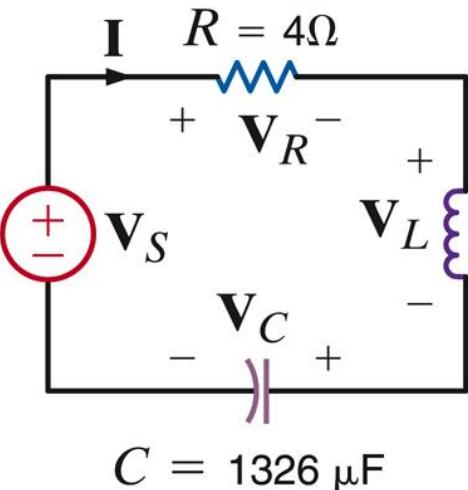

$$\omega = 377(s^{-1})$$

## 2. PUT KNOWN NUMERICAL VALUES

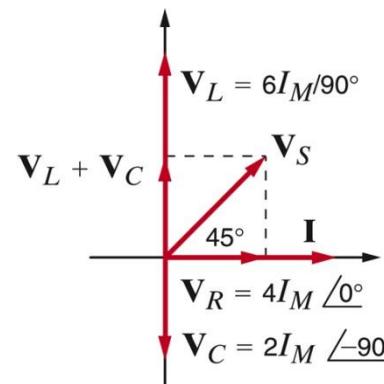

$$|\mathbf{V}_L - \mathbf{V}_C| = |\mathbf{V}_R|$$

$$Z_C = \frac{1}{j377 \times 1326 \times 10^{-6}}$$

$$Z_C = -j2 = 2\angle -90^\circ \Omega$$

$V_R = RI$

$V_L = j\omega LI$

$V_C = \frac{1}{j\omega C}I$

$V_S = V_R + V_L + V_C$

It is convenient to select the current as reference

## 1. DRAW ALL THE PHASORS


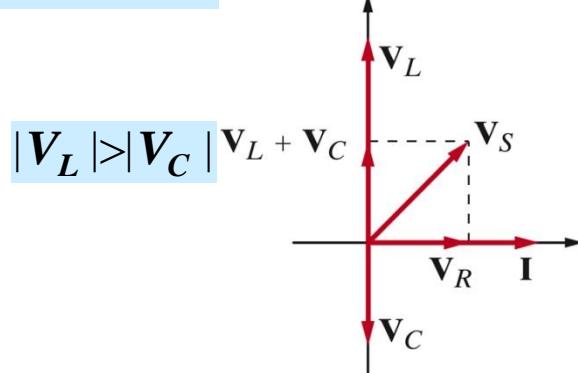


DIAGRAM WITH REFERENCE  $V_S = 12\sqrt{2}\angle 90^\circ$

$$V_L = 18\angle 135^\circ(V)$$

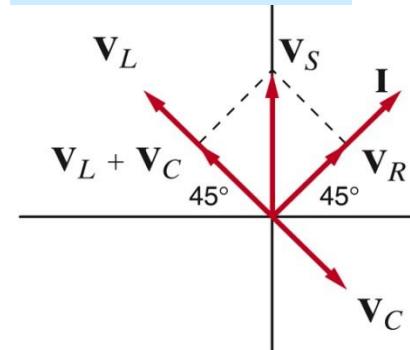

Read values from diagram!

$$\therefore I = 3\angle 45^\circ(A)$$


$$V_R = 12\angle 45^\circ(V)$$

(Pythagoras)

$$V_C = 6\angle -45^\circ$$
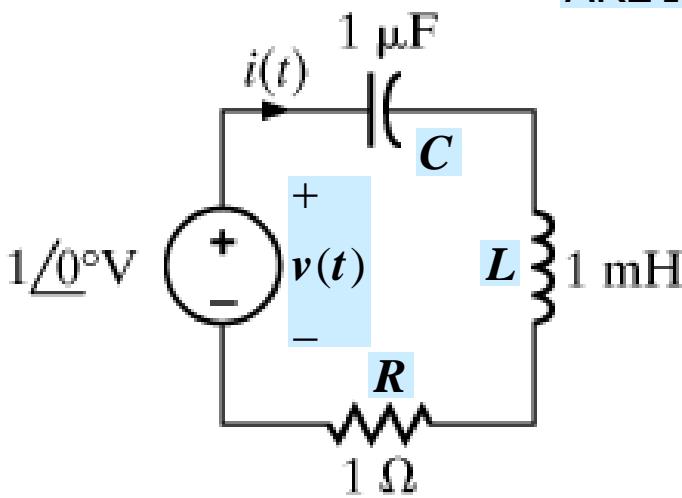
### EXAMPLE 3

FIND THE FREQUENCY AT WHICH  $v(t)$  AND  $i(t)$  ARE IN PHASE




i.e., the phasors for  $i(t), v(t)$  are co-linear

$$V = \frac{1}{j\omega C} I + j\omega L I + R I$$

Notice that I was chosen as reference

PHASOR DIAGRAM

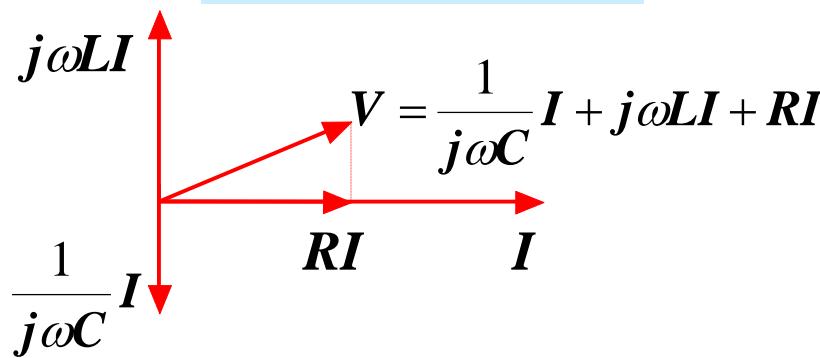

$$V \text{ and } I \text{ are co-linear iff } j\omega L + \frac{1}{j\omega C} = 0$$


$$\Rightarrow \omega^2 = \frac{1}{LC}$$

$$\omega^2 = \frac{1}{10^{-3} \times 10^{-6}} = 10^9 \Rightarrow \omega = 3.162 \times 10^4 \text{ (rad/s)}$$

$$f = \frac{\omega}{2\pi} = 5.033 \times 10^3 \text{ Hz}$$
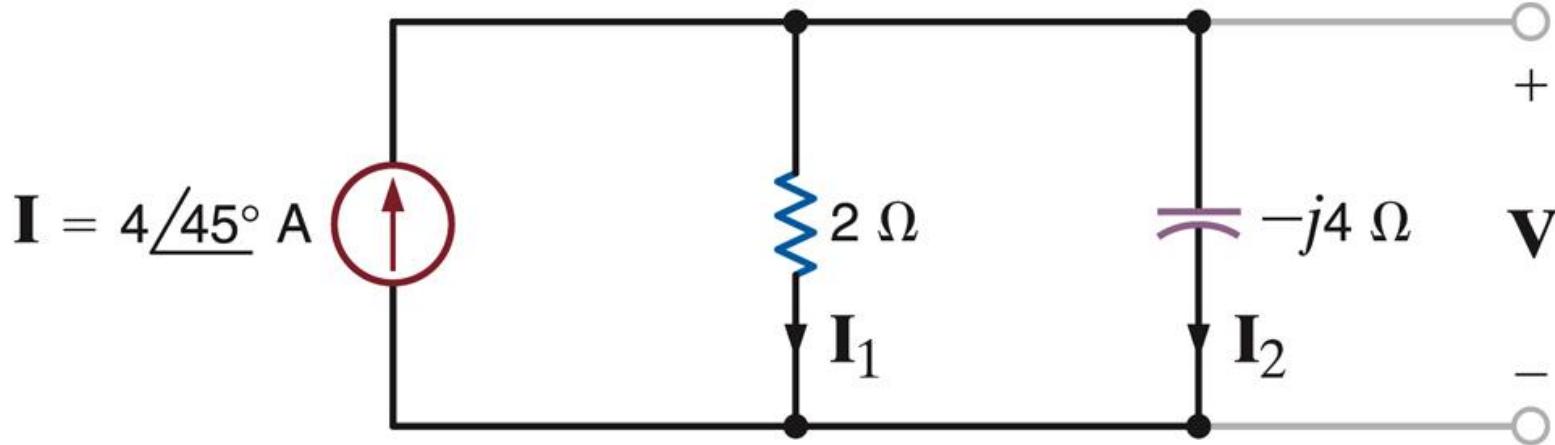
## EXAMPLE 4

Draw a phasor diagram illustrating all voltages and currents



$$\mathbf{I}_1 = \frac{-j4}{2-j4} \mathbf{I} = \frac{4\angle -90^\circ}{4.472\angle -63.435^\circ} 4\angle 45^\circ$$

Current divider


$$\mathbf{I}_1 = 3.578\angle 18.435^\circ (\text{A})$$

$$\mathbf{I}_2 = \frac{2}{2-j4} \mathbf{I} = \frac{2\angle 0^\circ}{4.472\angle -63.435^\circ} 4\angle 45^\circ$$

$$\mathbf{I}_2 = 1.789\angle 108.435^\circ \quad \text{Simpler than } \mathbf{I}_2 = \mathbf{I} - \mathbf{I}_1$$

$$\mathbf{V} = 2\mathbf{I}_1 = 7.156\angle 18.435^\circ (\text{V})$$

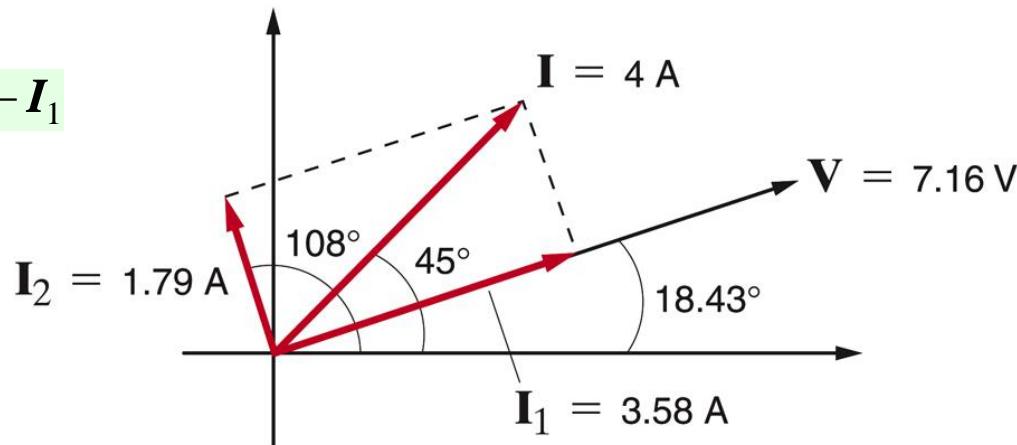DRAW PHASORS. ALL ARE KNOWN. NO NEED TO SELECT A REFERENCE



# BASIC ANALYSIS USING KIRCHHOFF'S LAWS

## PROBLEM SOLVING STRATEGY

For relatively simple circuits use

Ohm's law for AC analysis; i.e.,  $V = IZ$

The rules for combining  $Z$  and  $Y$

KCL and KVL

Current and voltage divider

For more complex circuits use

Node analysis

Loop analysis


Superposition

Source transformation

Thevenin's and Norton's theorems

**EXAMPLE 1**
**COMPUTE ALL THE VOLTAGES AND CURRENTS**

$$V_S = 24/60^\circ \text{ V}$$

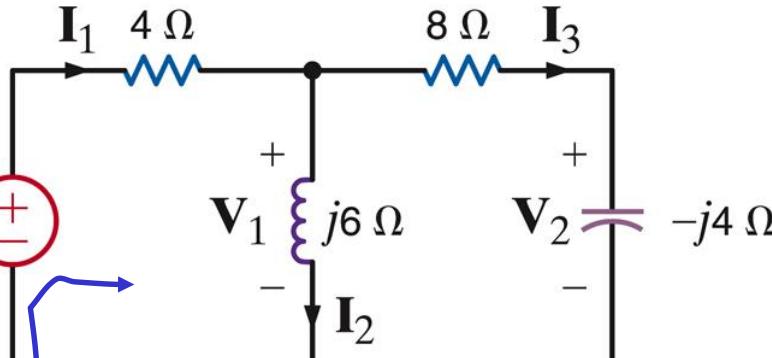

$$Z_{eq} = 4 + (j6 \parallel 8 - j4)$$

$$Z_{eq} = 4 + \frac{24 + j48}{8 + j2} = \frac{32 + j8 + 24 + j48}{8 + j2}$$

$$Z_{eq} = \frac{56 + j56}{8 + j2} = \frac{79.196 \angle 45^\circ}{8.246 \angle 14.036^\circ} = 9.604 \angle 30.964^\circ (\Omega)$$

$$I_1 = \frac{V_S}{Z_{eq}} = \frac{24 \angle 60^\circ}{9.604 \angle 30.964^\circ} = 2.498 \angle 29.036^\circ (\text{A})$$

$$I_3 = \frac{j6}{8 + j2} I_1 = \frac{6 \angle 90^\circ}{8.246 \angle 14.036^\circ} 2.498 \angle 29.036^\circ (\text{A})$$

$$I_2 = \frac{8 - j4}{8 + j2} I_1 = \frac{8.944 \angle -26.565^\circ}{8.246 \angle 14.036^\circ} 2.498 \angle 29.036^\circ (\text{A})$$


$$I_1 = 2.5 \angle 29.06^\circ \quad I_2 = 2.71 \angle -11.58^\circ \quad I_3 = 1.82 \angle 105^\circ$$

Compute  $I_1$

Use current divider for  $I_2, I_3$   
Ohm's law for  $V_1, V_2$


$$V_1 = 6 \angle 90^\circ I_2 \quad V_2 = 4 \angle -90^\circ I_3$$
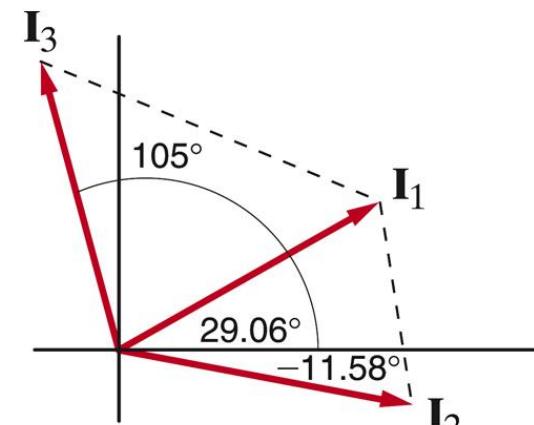
$$V_1 = 16.26 \angle 78.42^\circ (\text{V}) \\ V_2 = 7.28 \angle 15^\circ (\text{V})$$


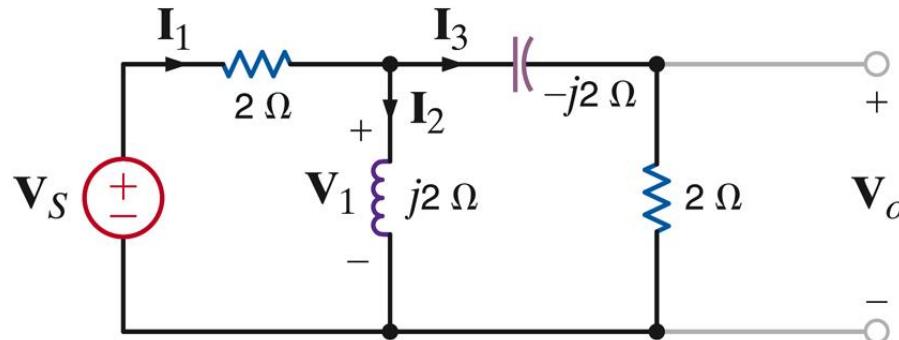
## EXAMPLE 2

IF  $V_o = 8\angle 45^\circ$ , COMPUTE  $V_s$



THE PLAN...

COMPUTE  $I_3$

COMPUTE  $V_1$

COMPUTE  $I_2, I_1$

COMPUTE  $V_s$

$$I_3 = \frac{V_o}{2} (A) = 4\angle 45^\circ (A)$$

$$V_1 = (2 - j2)I_3 = \sqrt{8}\angle -45^\circ \times 4\angle 45^\circ$$

$$V_1 = 11.314\angle 0^\circ (V)$$

$$I_2 = \frac{V_1}{j2} = \frac{11.314\angle 0^\circ}{2\angle 90^\circ} = 5.657\angle -90^\circ (A)$$

$$I_1 = I_2 + I_3 = 5.657\angle -90^\circ + 4\angle 45^\circ$$

$$I_1 = -j5.657 + (2.828 + j2.828)(A)$$

$$I_1 = 2.828 - j2.829(A)$$

$$V_s = 2I_1 + V_1 = 2(2.828 - j2.829) + 11.314\angle 0^\circ$$

$$V_s = 16.97 - j5.658(V)$$


$$V_s = 17.888\angle -18.439^\circ$$

# ANALYSIS TECHNIQUES

PURPOSE: TO REVIEW ALL CIRCUIT ANALYSIS TOOLS DEVELOPED FOR RESISTIVE CIRCUITS; I.E., NODE AND LOOP ANALYSIS, SOURCE SUPERPOSITION, SOURCE TRANSFORMATION, THEVENIN'S AND NORTON'S THEOREMS.

## EXAMPLE 3

COMPUTE  $I_0$

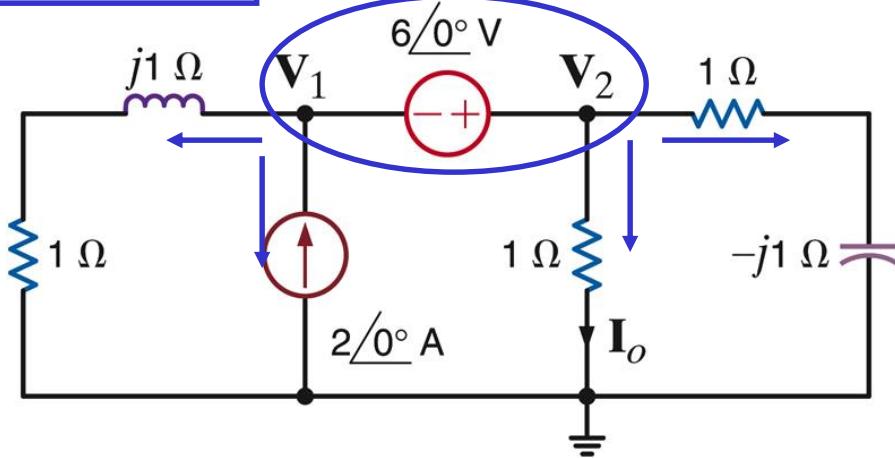

### 1. NODE ANALYSIS

$$\frac{V_1}{1+j1} - 2\angle 0^\circ + \frac{V_2}{1} + \frac{V_2}{1-j1} = 0$$

$$V_1 - V_2 = -6\angle 0^\circ$$

$$I_0 = \frac{V_2}{1}(A)$$

$$\frac{V_2 - 6\angle 0^\circ}{1+j1} - 2\angle 0^\circ + V_2 + \frac{V_2}{1-j1} = 0$$

$$V_2 \left[ \frac{1}{1+j1} + 1 + \frac{1}{1-j1} \right] = 2 + \frac{6}{1+j1}$$

$$V_2 \frac{(1-j1) + (1+j1)(1-j1) + (1+j1)}{(1+j1)(1-j1)} = \frac{2(1+j1) + 6}{1+j1}$$

$$V_2 \frac{4}{1-j} = 8 + j2$$

$$V_2 = \frac{(4+j)(1-j)}{2} = \frac{5-j3}{2}$$


$$I_0 = \left( \frac{5}{2} - j \frac{3}{2} \right) (A)$$

$$I_0 = 2.92 \angle -30.96^\circ$$

NEXT: LOOP ANALYSIS

### EXAMPLE 3

### LOOP ANALYSIS

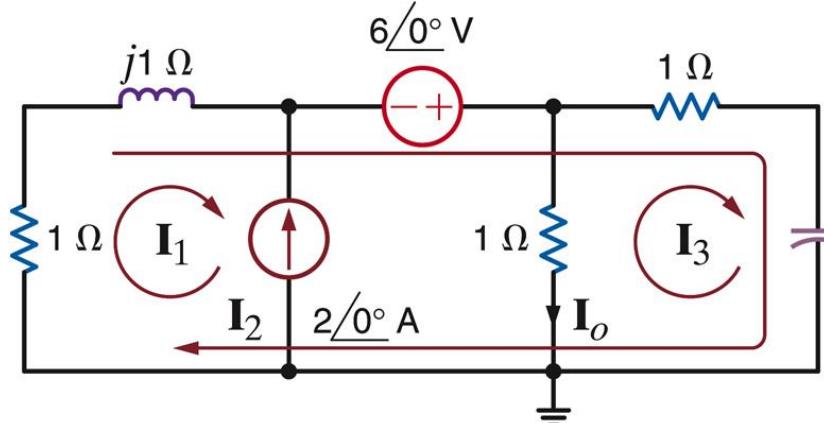

SOURCE IS NOT SHARED AND  $I_0$  IS DEFINED BY ONE LOOP CURRENT

$$\text{LOOP 1: } I_1 = -2\angle 0^\circ$$

$$I_0 = -I_3$$

$$\text{LOOP 2: } (1+j)(I_1 + I_2) - 6\angle 0^\circ + (1-j)(I_2 + I_3) = 0$$

$$\text{LOOP 3: } (1-j)(I_2 + I_3) + I_3 = 0$$

MUST FIND  $I_3$

$$2I_2 + (1-j)I_3 = 6 - (1+j)(-2)$$


$$(1-j)I_2 + (2-j)I_3 = 0$$

$$(1-j)^2 - 2(2-j)I_3 = (1-j)(8+2j)$$

$$I_3 = \frac{10-6j}{-4}$$

$$I_0 = -I_3 = -\left(-\frac{5}{2} + \frac{3}{2}j\right) = \frac{5}{2} - \frac{3}{2}j \text{ A}$$

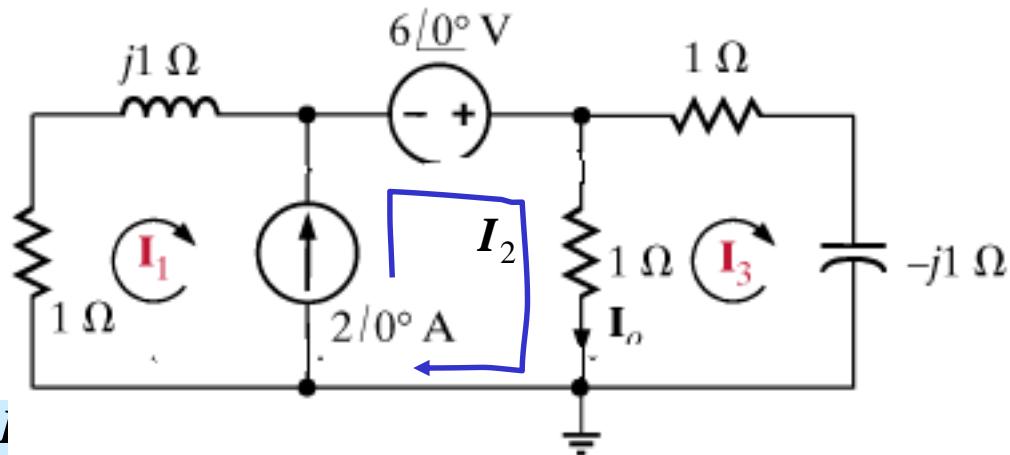ONE COULD ALSO USE THE SUPERMESH TECHNIQUE



CONSTRAINT:  $I_1 - I_2 = -2\angle 0^\circ$

SUPERMESH:  $(1+j)I_1 + 6\angle 0^\circ + (I_2 - I_3) = 0$



MESH 3:  $(I_3 - I_2) + (1-j)I_3 = 0$

$$I_0 = I_2 - I_3$$


NEXT: SOURCE SUPERPOSITION

## SOURCE SUPERPOSITION
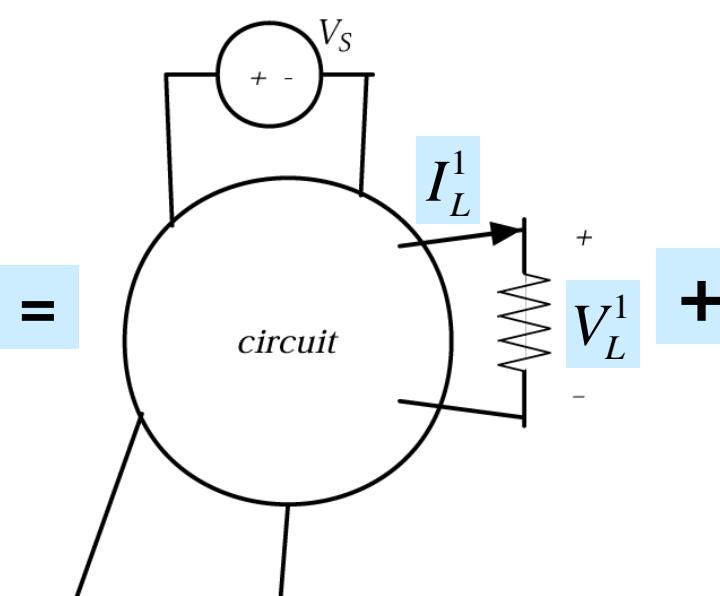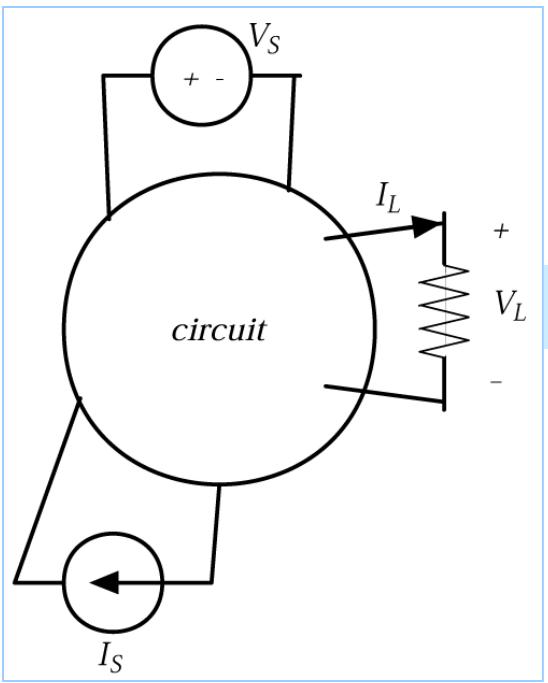
## Circuit with voltage source set to zero (SHORT CIRCUITED)



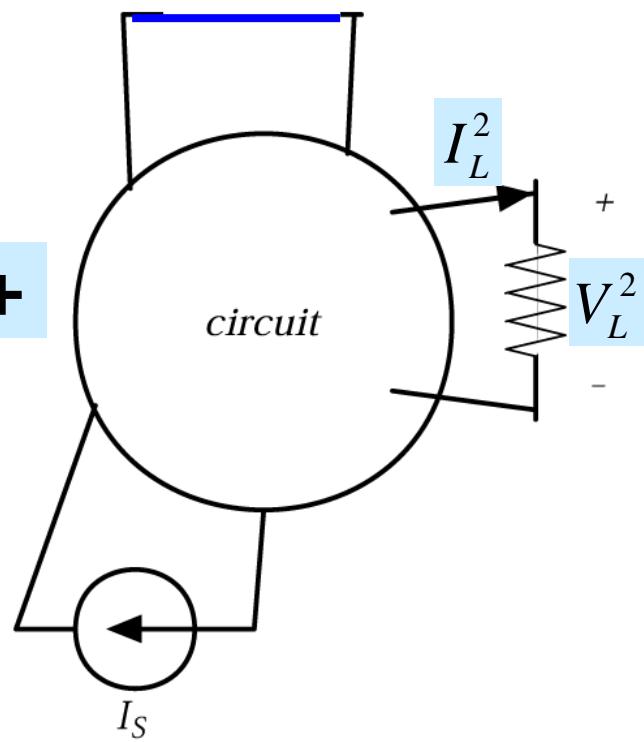**Circuit with current source set to zero(OPEN)**



**Due to the linearity of the models we must have**





$$I_L = I_L^1 + I_L^2$$

$$V_L = V_L^1 + V_L^2$$

**Principle of Source Superposition**

The approach will be useful if solving the two circuits is simpler, or more convenient, than solving a circuit with two sources

We can have any combination of sources. And we can partition any way we find convenient

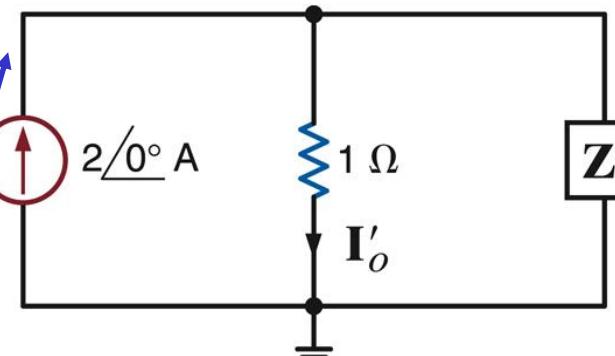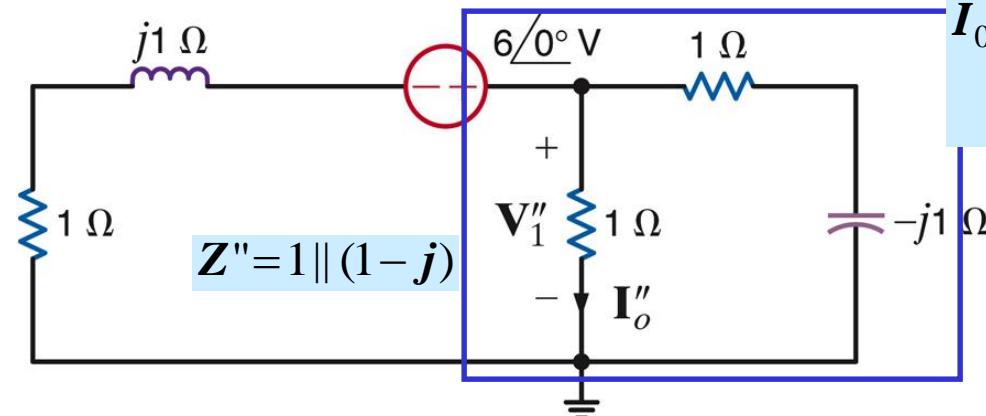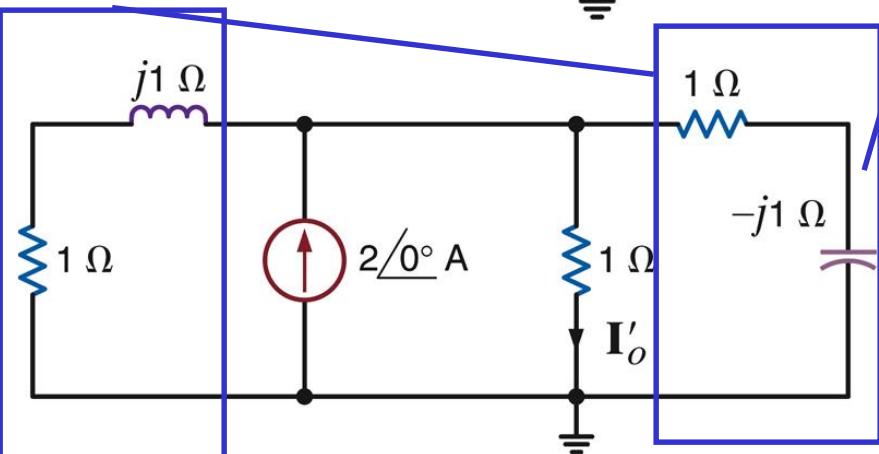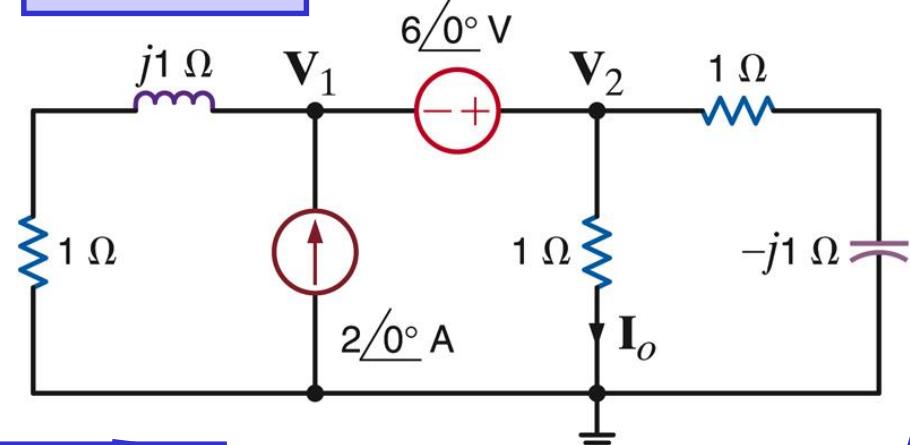**EXAMPLE 3**
**SOURCE SUPERPOSITION**


$$Z' = (1+j) \parallel (1-j) = \frac{(1+j)(1-j)}{(1+j) - (1-j)} = 1$$

COULD USE SOURCE TRANSFORMATION  
TO COMPUTE  $I''_0$

$$V''_1 = \frac{Z''}{Z'' + 1 + j} 6\angle0^\circ(V)$$

$$I''_0 = \frac{Z''}{Z'' + 1 + j} 6\angle0^\circ(A)$$

$$Z'' = \frac{1-j}{2-j}$$

$$I''_0 = \frac{1-j}{(1-j) + 3 + j} 6(A)$$

$$I''_0 = \frac{6}{4} - \frac{6}{4}j(A)$$

$$I_0 = I'_0 + I''_0 = \left(\frac{5}{2} - \frac{3}{2}j\right)(A)$$


NEXT: SOURCE TRANSFORMATION

Source transformation is a good tool to reduce complexity in a circuit ...


WHEN IT CAN BE APPLIED!!

“ideal sources” are not good models for real behavior of sources

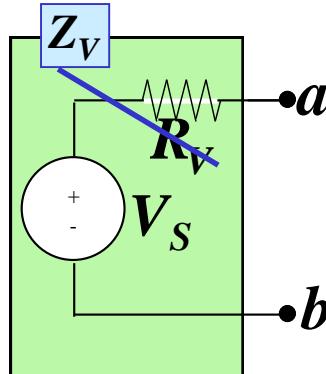A real battery does not produce infinite current when short-circuited



Improved model  
for voltage source

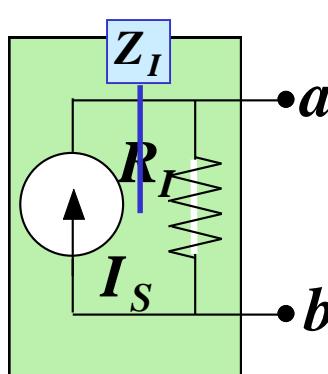




Improved model  
for current source

THE MODELS ARE EQUIVALENTS WHEN  
 $R_V = R_I = R$   
 $V_S = RI_S$

$$Z_V = Z_I = Z$$
$$V_S = ZI_S$$

Source Transformation can be used to determine the Thevenin or Norton Equivalent...


BUT THERE MAY BE MORE EFFICIENT TECHNIQUES

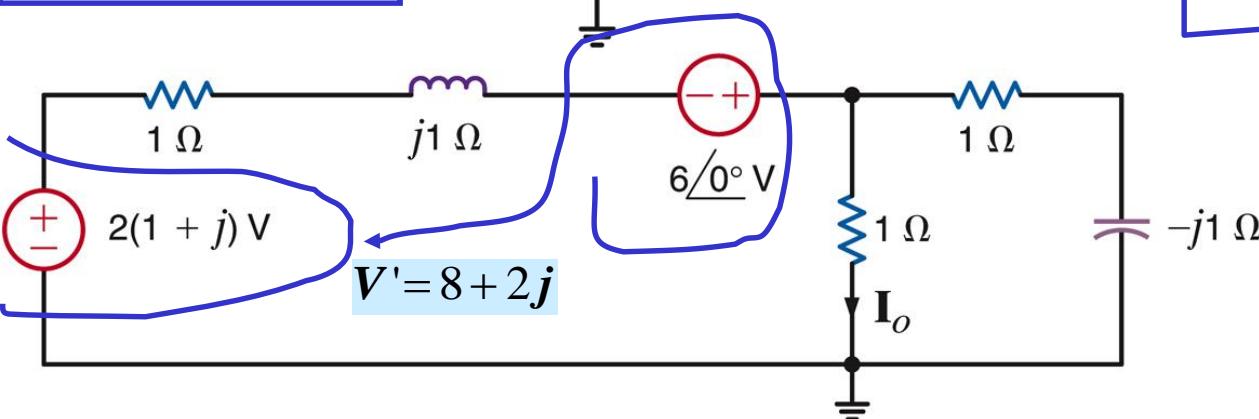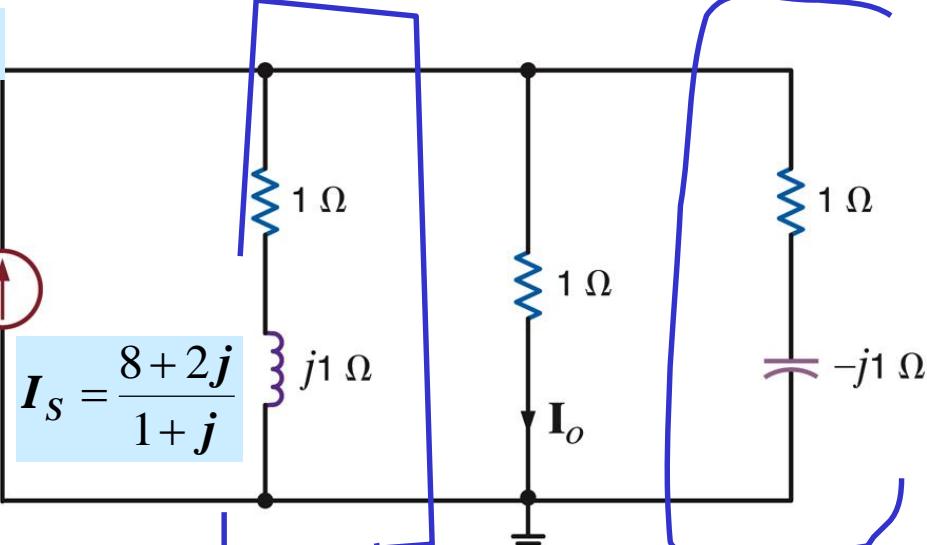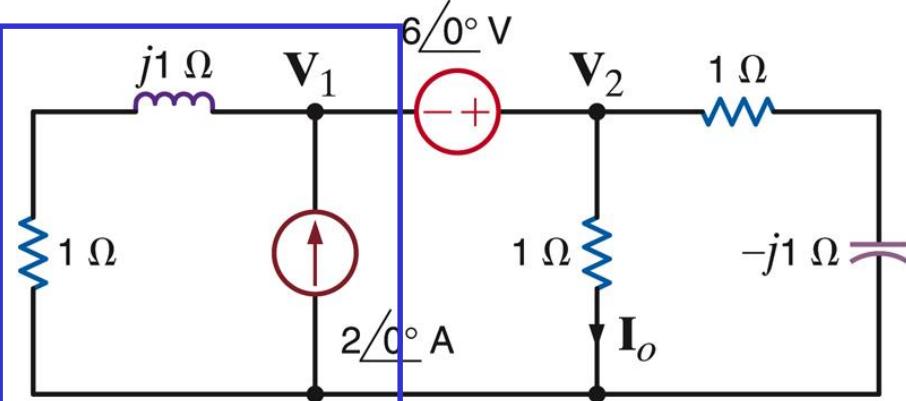**EXAMPLE 3**
**SOURCE TRANSFORMATION**


$$Z = (1+j) \parallel (1-j) = 1\Omega$$



**Now a voltage to current transformation**

**NEXT: THEVENIN**

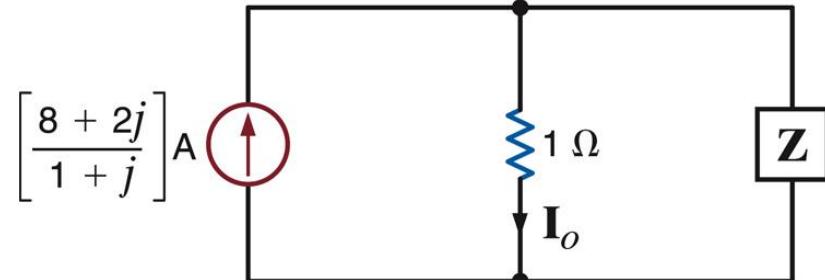

$$I_o = \frac{I_s}{2} = \frac{4+j}{1+j} = \frac{(4+j)(1-j)}{(1+j)(1-j)} = \frac{5-3j}{2}$$

# THEVENIN'S EQUIVALENCE THEOREM

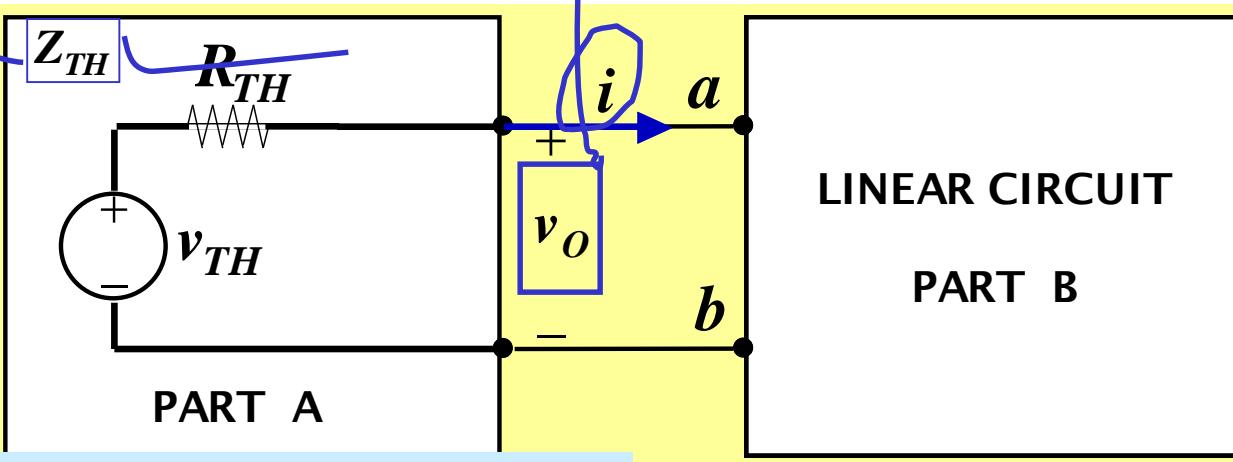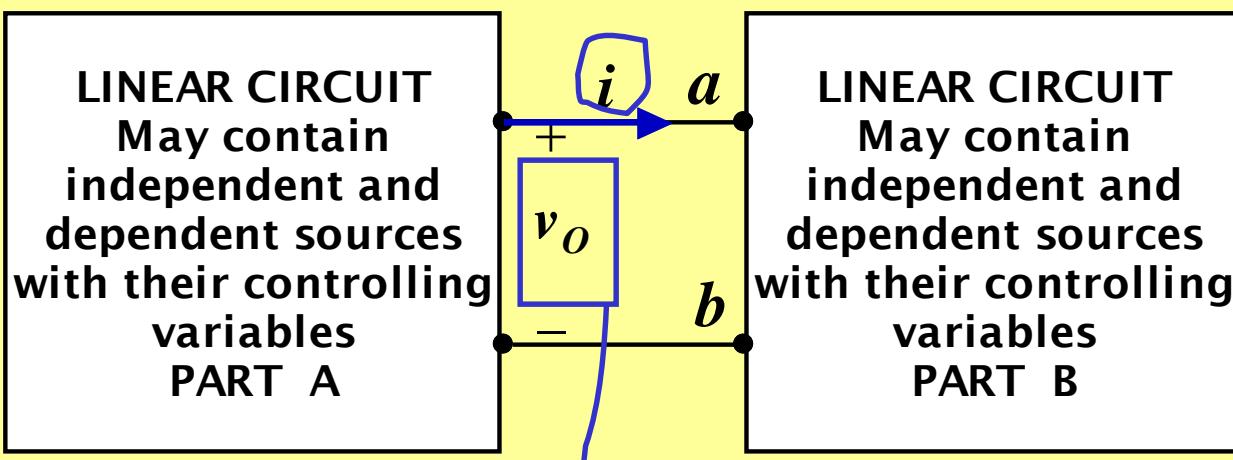

Thevenin Equivalent Circuit  
for PART A

Phasor


$v_{TH}$

$R_{TH}$

Thevenin Equivalent Source  
Thevenin Equivalent Resistance


Impedance

### EXAMPLE 3: THEVENIN ANALYSIS

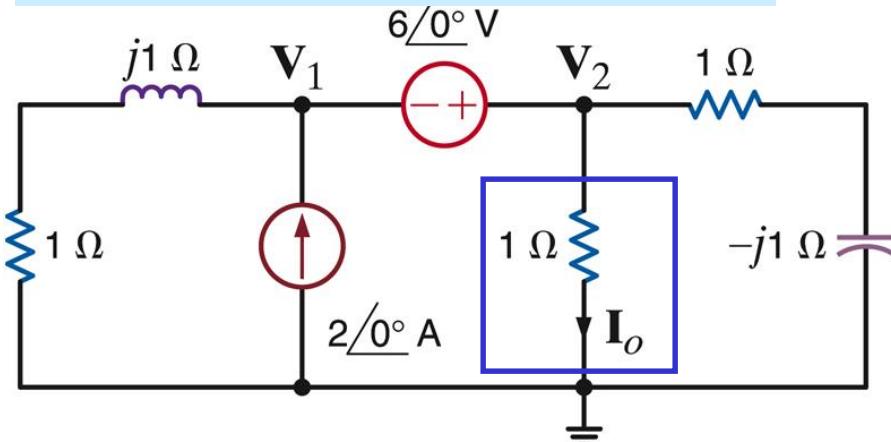

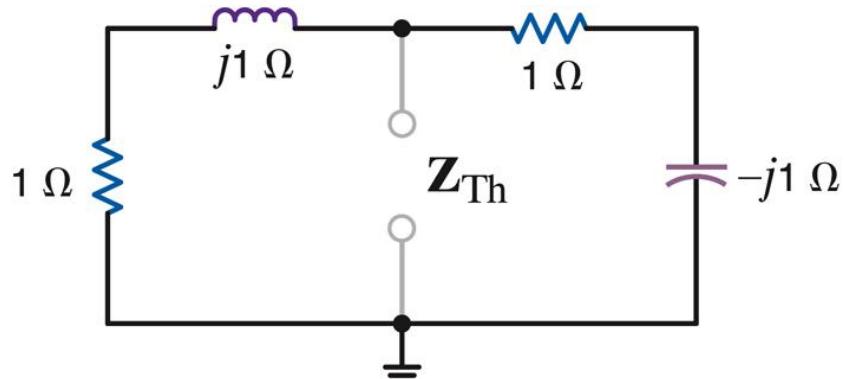
### Voltage Divider


$$V_{OC} = \frac{1-j}{(1+j)+(1-j)}(8+2j) = \frac{10-6j}{2}$$


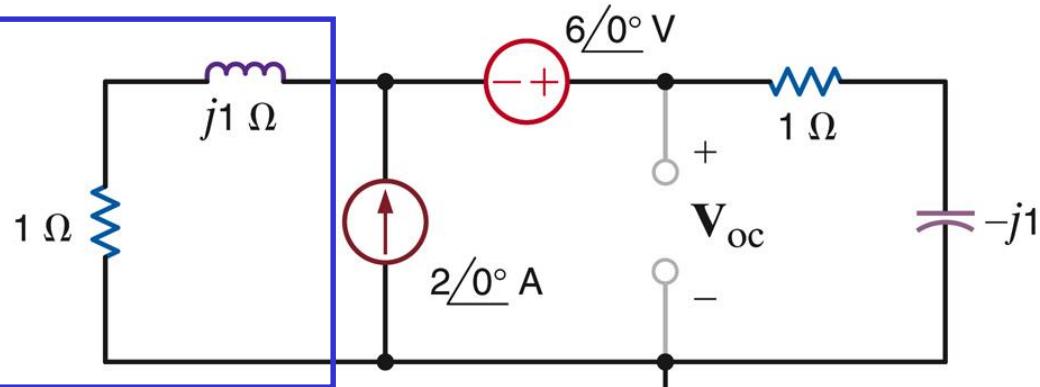
$$Z_{TH} = (1+j) \parallel (1-j) = 1\Omega$$





$$V_{oc} = (5 - 3j)\text{ V}$$

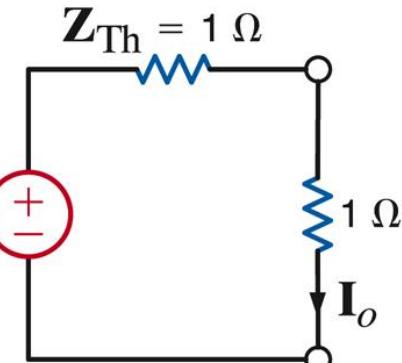

$$I_0 = \frac{5-3j}{2}(\text{A})$$

NEXT: NORTON

# NORTON'S EQUIVALENCE THEOREM

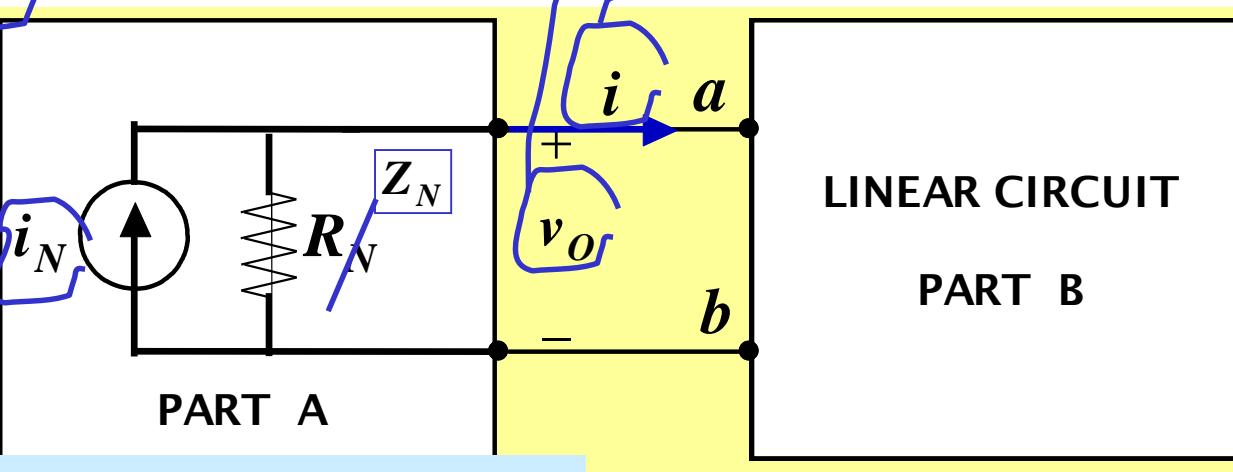
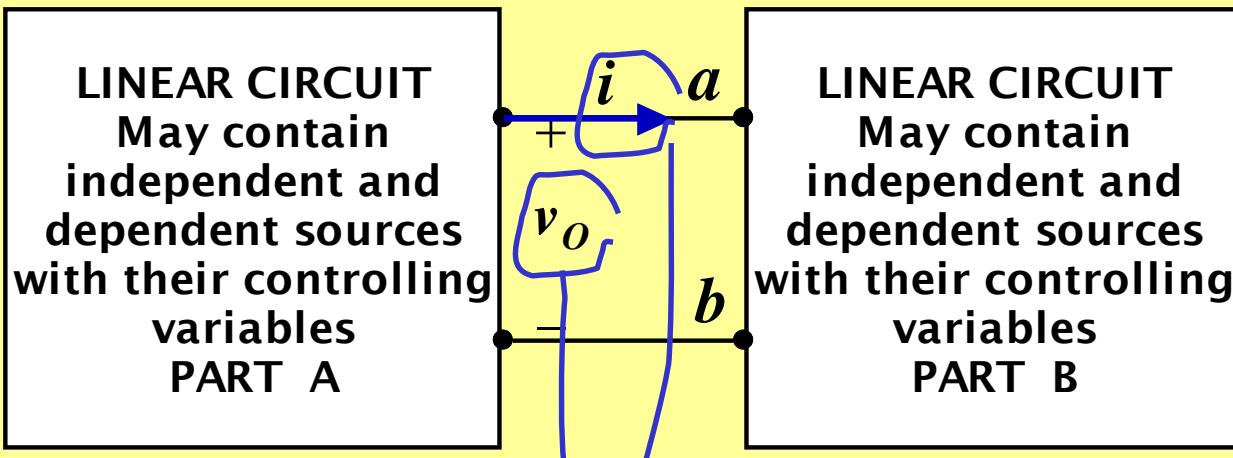


Norton Equivalent Circuit  
for PART A


$i_N$  Thevenin Equivalent Source  
 $R_N$   $Z_N$  Thevenin Equivalent Resistance

Impedance

## EXAMPLE 3: NORTON ANALYSIS

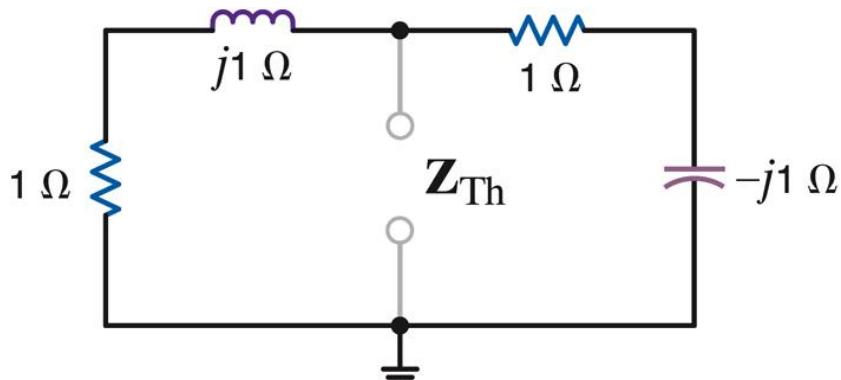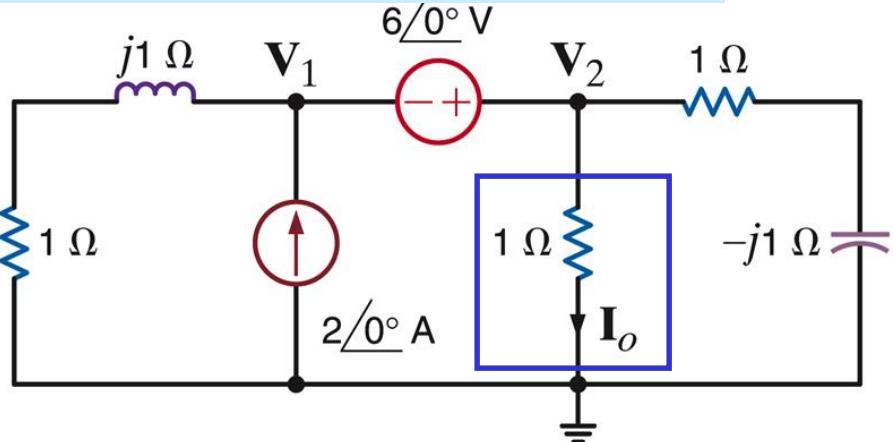
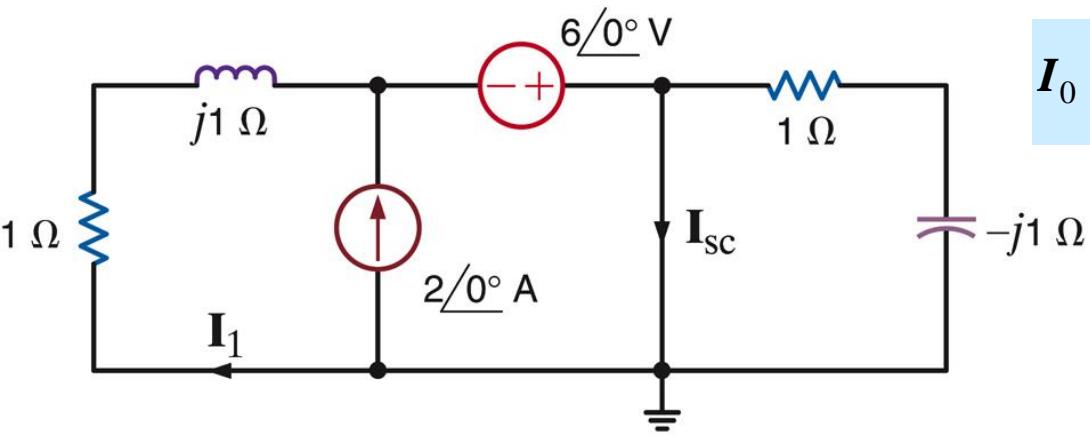
$$Z_{TH} = (1+j) \parallel (1-j) = 1\Omega$$




$$I_0 = \frac{I_{sc}}{2} = \frac{4+j}{1-j} = \frac{(4+j)(1-j)}{(1+j)(1-j)} = \frac{5-3j}{2}$$

Possible techniques: loops, source transformation, superposition

BY SUPERPOSITION

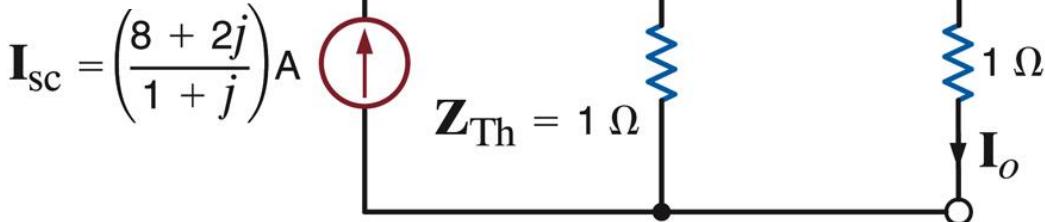
$$I_{sc} = 2\angle0^\circ + \frac{6\angle0^\circ}{1+j} = \frac{8+2j}{1+j} (A)$$




## EXAMPLE 4
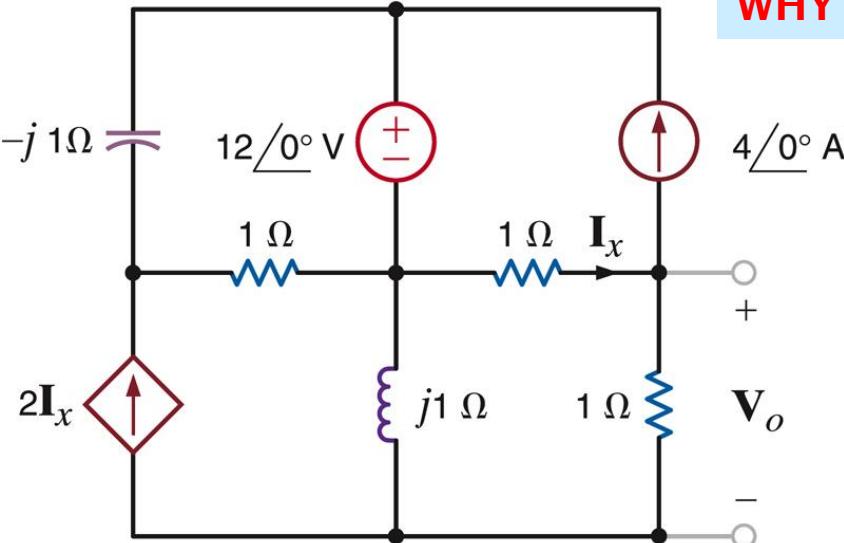
## FIND $V_0$ USING NODES, LOOPS, THEVENIN, NORTON

WHY SKIP SUPERPOSITION AND TRANSFORMATION?



NODES

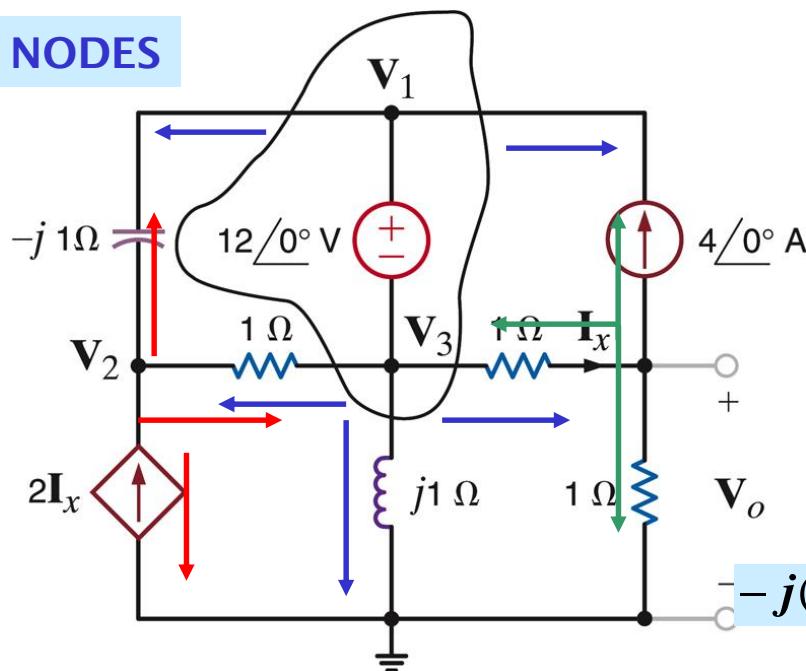

Notice choice of ground

Supernode constraint:  $V_1 - V_3 = 12\angle 0^\circ$

KCL @ Supernode

$$-4\angle 0^\circ + \frac{V_3 - V_0}{1} + \frac{V_3 - V_2}{1} + \frac{V_1 - V_2}{-j} + \frac{V_3}{j} = 0$$

KCL@ $V_2$

$$\frac{V_2 - V_1}{-j} - 2I_x + \frac{V_2 - V_3}{1} = 0$$

KCL@ $V_0$

$$\frac{V_0}{1} + \frac{V_0 - V_3}{1} + 4\angle 0^\circ = 0 \Rightarrow V_3 = 2V_0 + 4$$

Controlling variable

$$I_x = \frac{V_3 - V_0}{1}$$

$$V_1 = V_3 + 12$$

$$V_1 = 2V_0 + 16$$


$$V_3 - V_0 = V_0 + 4$$

$$j(V_2 - 2V_0 - 16) - 2(V_0 + 4) + (V_2 - 2V_0 - 4) + (V_0 + 4) - j(2V_0 + 4) = 4$$


$$\text{Adding: } V_0 = -\frac{8 + 4j}{1 + 2j}$$

## EXAMPLE 4

## LOOP ANALYSIS

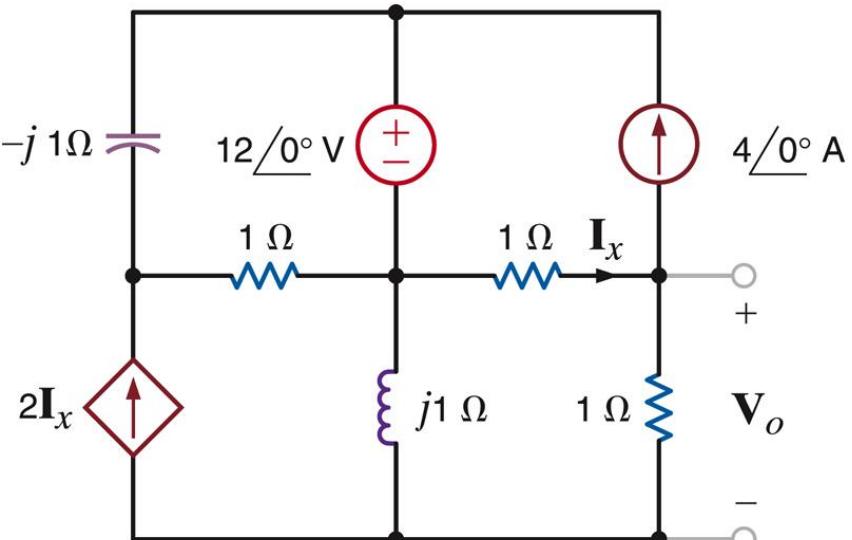

MESH CURRENTS ARE ACCEPTABLE

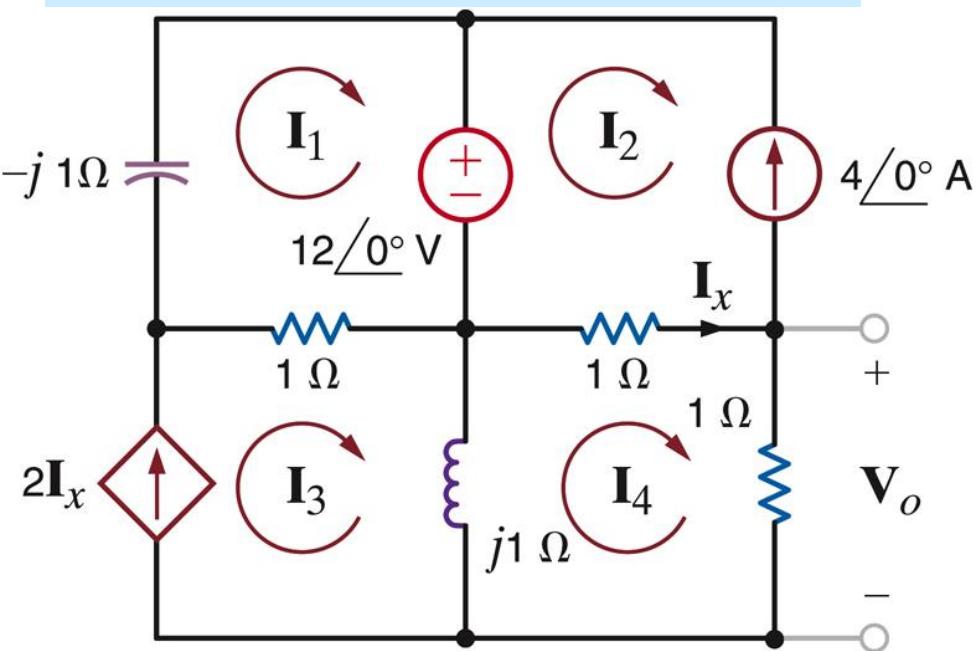

## MESH CURRENTS DETERMINED BY SOURCES

$$I_2 = -4\angle 0^\circ$$

$$I_3 = 2I_x$$

$$\Rightarrow I_3 = 2(I_4 + 4)$$

MESH 1:

$$-jI_1 + 12\angle 0^\circ + 1(I_1 - I_3) = 0$$

MESH 4:

$$1(I_4 - I_2) + 1 \times I_4 + j(I_4 - I_3) = 0$$



CONTROLLING VARIABLE:  $I_x = I_4 - I_2$

VARIABLE OF INTEREST:  $V_o = 1 \times I_4(V)$



$$I_4 + 4 + I_4 + j(I_4 - 2(I_4 + 4)) = 0$$

$$(2 - j)I_4 = -(4 - 8j) \Rightarrow I_4 = -\frac{4 - 8j}{2 - j} \times \frac{j}{j}$$

$$V_o = -\frac{8 + 4j}{1 + 2j}$$

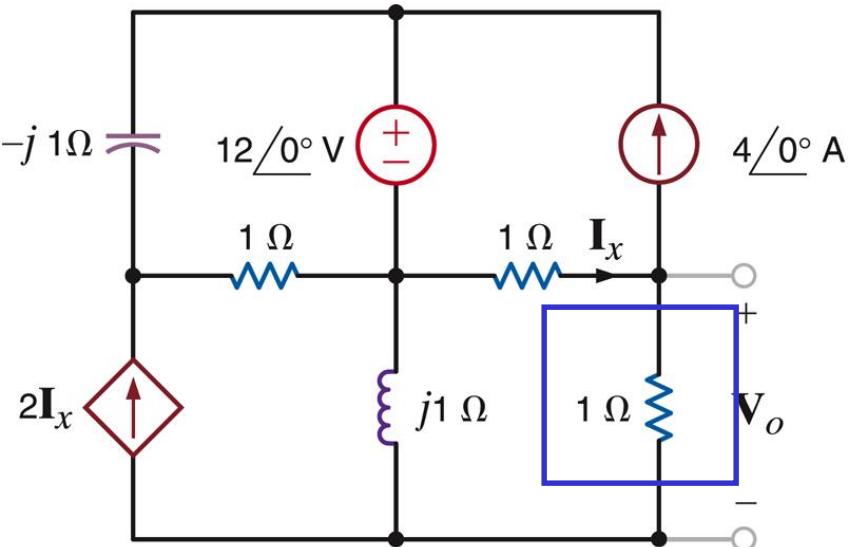
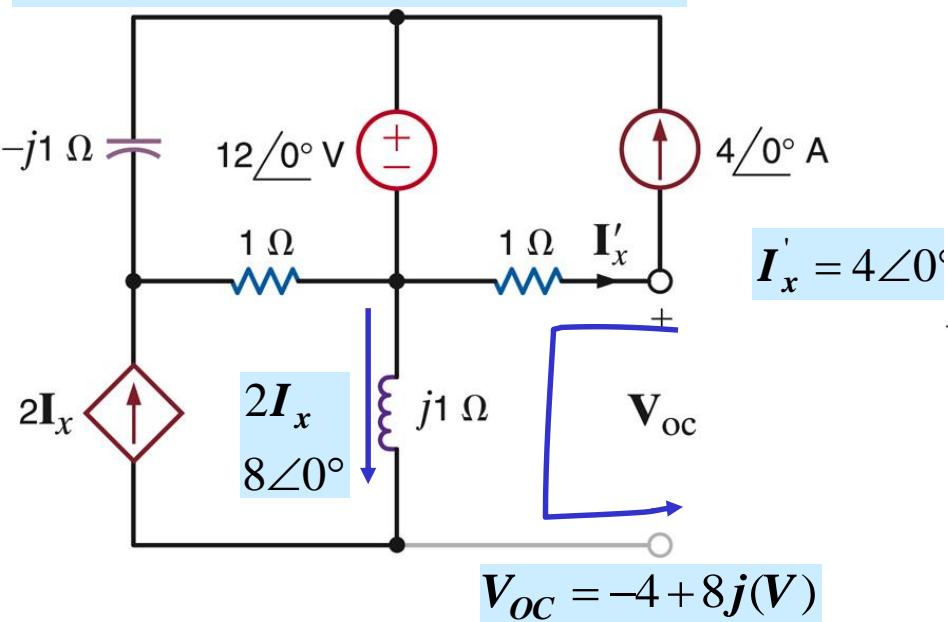
**EXAMPLE 4**
**THEVENIN**

**FOR OPEN CIRCUIT VOLTAGE**

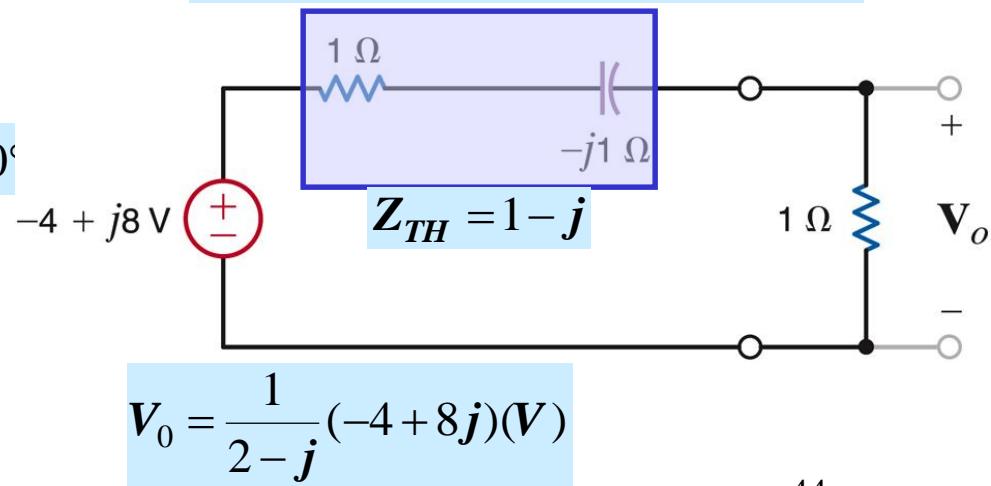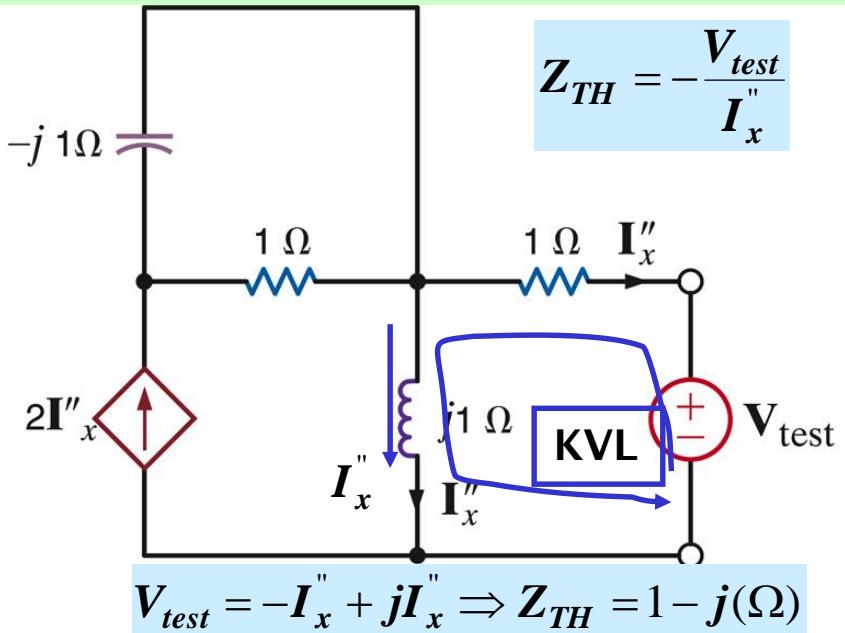**Alternative procedure to compute Thevenin impedance:**

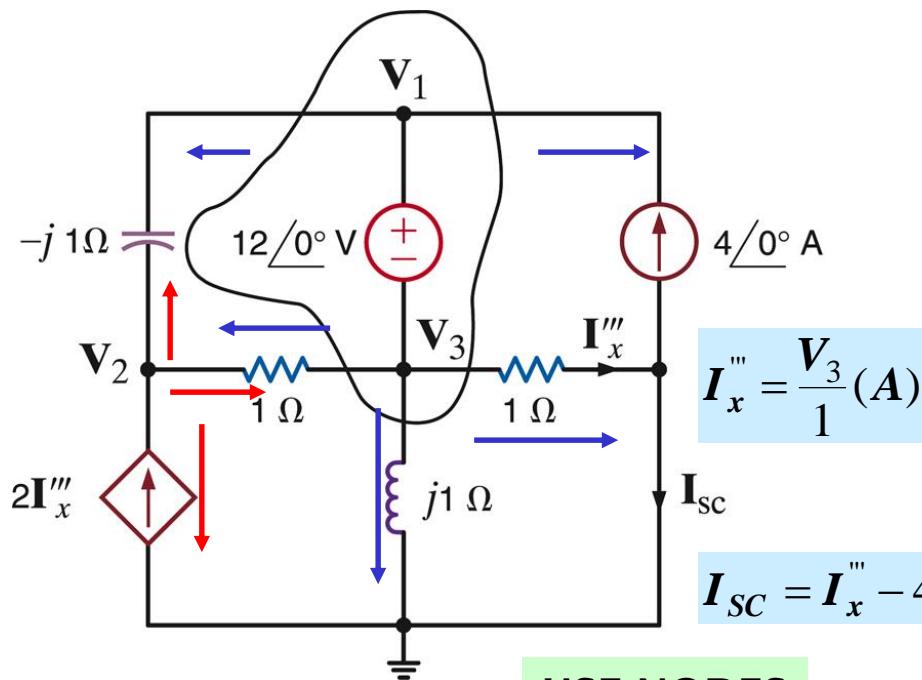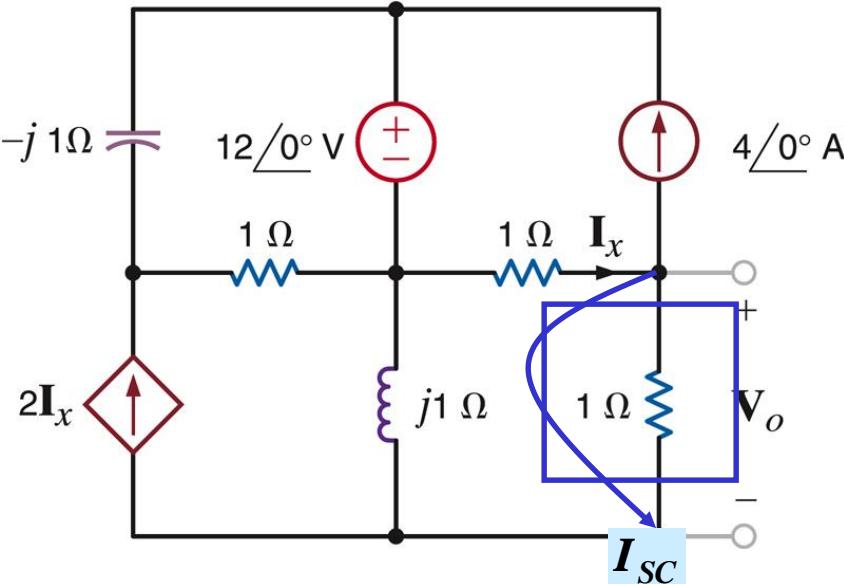1. Set to zero all INDEPENDENT sources
2. Apply an external probe



## EXAMPLE 4

## NORTON



## Supernode constraint

$$V_1 - V_3 = 12\angle 0^\circ \Rightarrow V_1 = V_3 + 12$$

KCL@ Supernode

$$\frac{V_3}{1} + \frac{V_3}{j} + \frac{V_3 - V_2}{1} + \frac{V_1 - V_2}{-j} - 4\angle 0^\circ = 0 / \times j$$

$$\text{KCL@ } V_2 : -2I_x''' + \frac{V_2 - V_3}{1} + \frac{V_2 - V_1}{-j} = 0 / \times (-j)$$

Controlling Variable:  $I_x''' = \frac{V_3}{1}$

$$2jV_3 - j(V_2 - V_3) + (V_2 - V_3 - 12) = 0$$

$$(1-j)V_2 - (1-3j)V_3 = 12$$


$$(1+j)V_3 + jV_3 - jV_2 - (V_3 + 12) + V_2 = 4j$$

$$(1-j)V_2 + 2jV_3 = 12 + 4j$$

$$(1-j)V_3 = 4j \Rightarrow V_3 = \frac{4j}{1-j} \Rightarrow I_{SC} = \frac{-4+8j}{1-j}$$

$$I_{SC} = \frac{(-4+8j)j}{(1-j)j} = -\frac{8+4j}{1+j}$$

Now we can draw the Norton Equivalent circuit ...

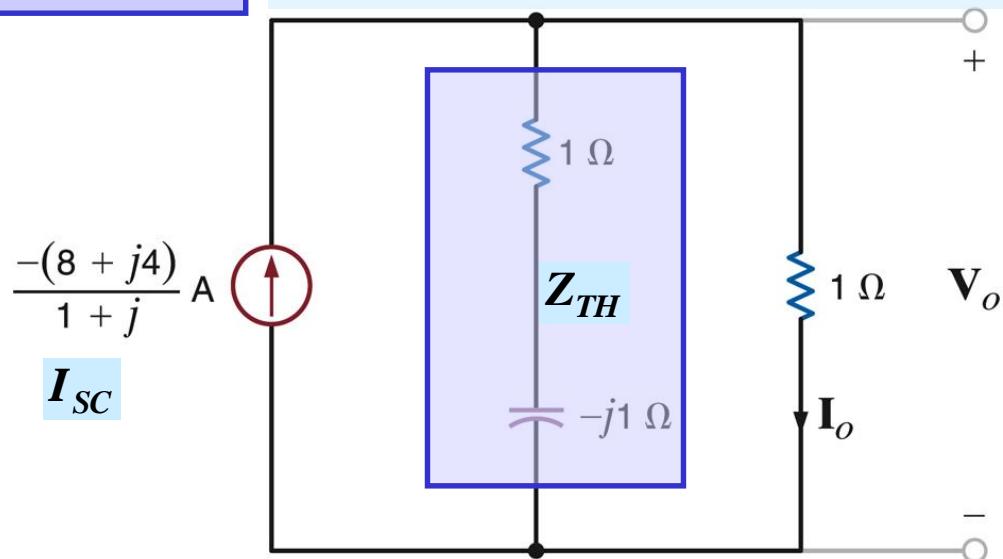**EXAMPLE 4****NORTON'S EQUIVALENT CIRCUIT**

$$V_0 = (1)I_0(V) = \frac{1-j}{2-j} \left( -\frac{8+4j}{1+j} \right) (V) \quad \text{Current Divider}$$

**EXAMPLE 4** **EQUIVALENCE OF SOLUTIONS****Using Norton's method**

$$V_0 = -\frac{12-4j}{3+j} = -\frac{(8+4j)(1-j)}{(1+2j)(1-j)}$$

**Using Thevenin's**


$$V_0 = \frac{-4+8j}{2-j} \times \frac{j}{j}$$

**Using Node and Loop methods**

$$V_0 = -\frac{8+4j}{1+2j}$$

## EXAMPLE 5

### USE NODAL ANALYSIS

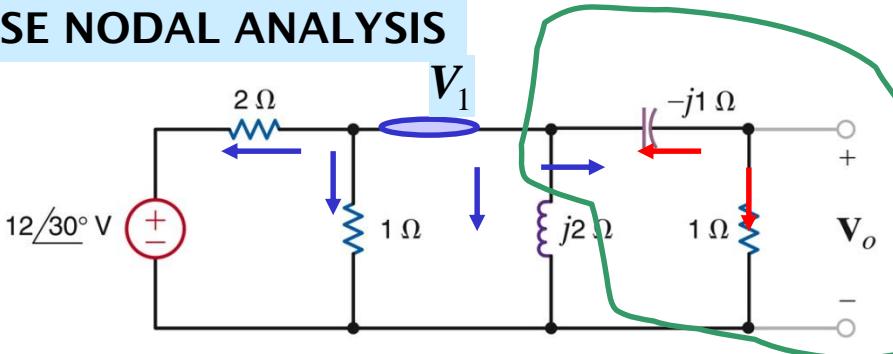

$$\frac{V_1 - 12\angle 30^\circ}{2} + \frac{V_1}{1} + \frac{V_1}{j2} + \frac{V_1 - V_0}{-j} = 0 \quad / \times 2j$$

$$\frac{V_0 - V_1}{-j} + \frac{V_0}{1} = 0 \Rightarrow V_1 = (1-j)V_0$$

$$j(V_1 - 12\angle 30^\circ) + 2jV_1 + V_1 - 2(V_1 - V_0) = 0$$

$$2V_0 + (1 - 2 + 2j + j)(1-j)V_0 = j12\angle 30^\circ$$

$$(2 + (-1 + 3j)(1-j))V_0 = 1\angle 90^\circ \times 12\angle 30^\circ$$

$$V_0 = \frac{12\angle 120^\circ}{4 + 4j} = \frac{12\angle 120^\circ}{5.66\angle 45^\circ} = 2.12\angle 75^\circ (V)$$


### COMPUTE $V_0$

### USE THEVENIN

$$Z_{TH} = 2 \parallel 1 \parallel j2 = \frac{4j}{\frac{2}{3} + j2} = \frac{4j}{2 + 6j} = \frac{4j(2 - 6j)}{40}$$

$$V_{OC} = \frac{1 \parallel j2}{2 + (1 \parallel j2)} 12\angle 30^\circ = \frac{j2}{2(1 + 2j) + 2j} 12\angle 30^\circ$$

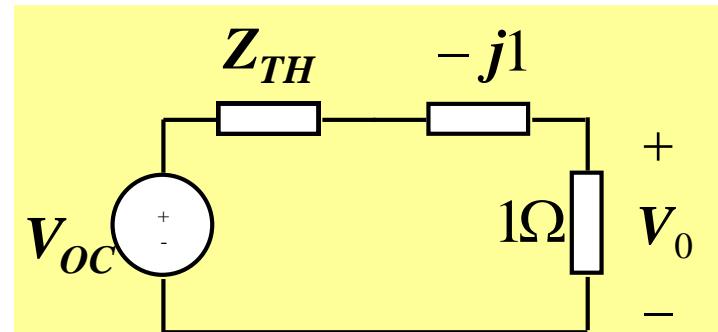
$$V_{OC} = \frac{24\angle 120^\circ}{2 + 6j} = \frac{12\angle 120^\circ}{1 + 3j}$$



$$V_0 = \frac{1}{Z_{TH} + 1 - j} V_{OC}$$

## EXAMPLE 6

## COMPUTE $V_0$ USING MESH ANALYSIS

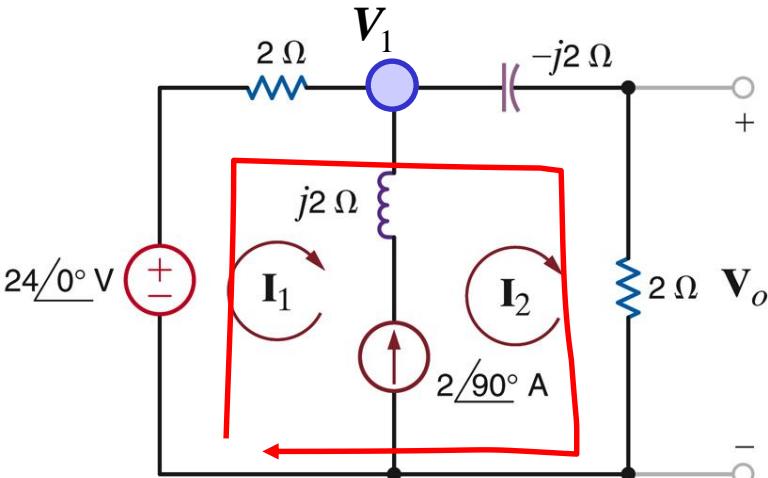

**CONSTRAINT**

$$-I_1 + I_2 = 2\angle 90^\circ \Rightarrow I_1 = I_2 - 2j$$

**SUPERMESH**

$$-24\angle 0^\circ + 2I_1 - 2jI_2 + 2I_2 = 0$$

$$2(I_2 - 2j) + (2 - 2j)I_2 = 24 \Rightarrow (4 - 2j)I_2 = 24 + 4j$$

$$V_0 = 2I_2 = \frac{24 + 4j}{2 - j} = \frac{24.33\angle 9.46^\circ}{2.24\angle -26.57^\circ} = 10.86\angle 36.03^\circ$$

### USING NODES

$$\frac{V_1 - 24\angle 0^\circ}{2} - 2\angle 90^\circ + \frac{V_1}{2 - 2j} = 0$$

$$V_0 = \frac{2}{2 - 2j} V_1$$

### USING SOURCE SUPERPOSITION



$$V_0^V = \frac{2}{2 + 2 - 2j} 24\angle 0^\circ$$

$$V_0^I = 2 \times \frac{2}{4 - 2j} 2\angle 90^\circ$$


$$V_0 = V_0^V + V_0^I$$

## EXAMPLE 7

COMPUTE  $V_0$

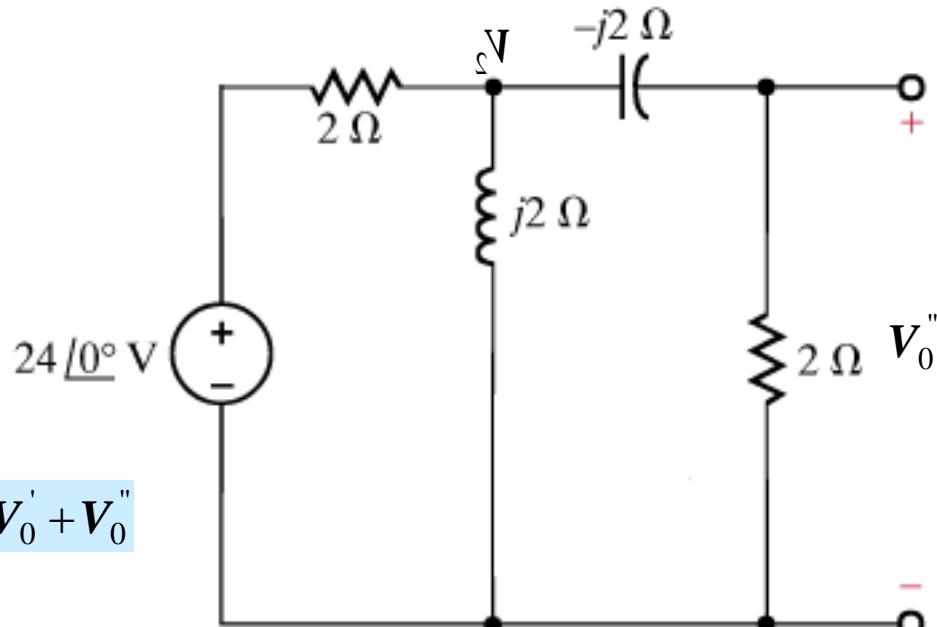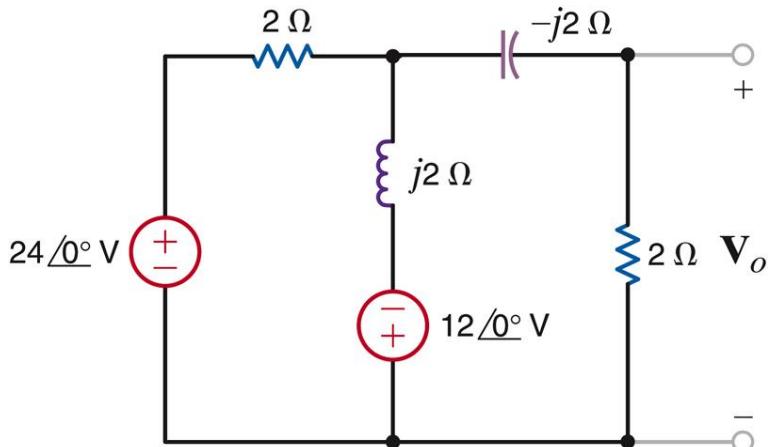

USING SUPERPOSITION

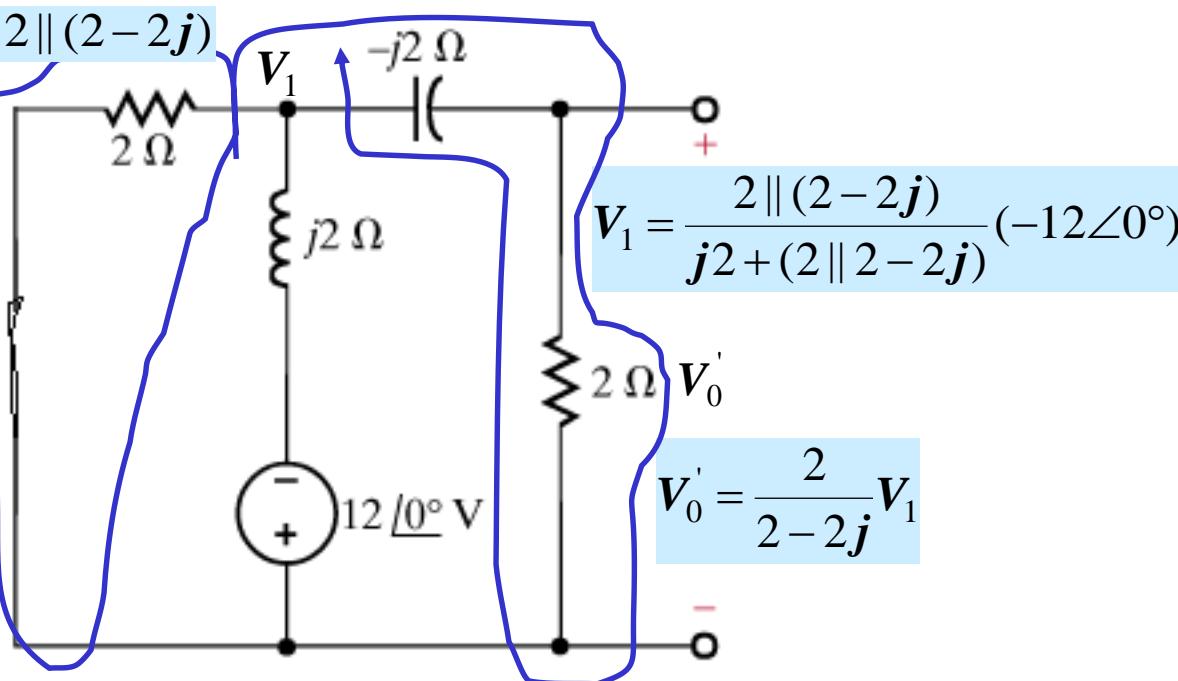

$$V_2 = \frac{(2j) \parallel (2 - 2j)}{2 + (2j \parallel 2 - 2j)} 24\angle 0^\circ$$



$$V_0'' = \frac{2}{2 - 2j} V_2$$

$$V_1 = \frac{2 \parallel (2 - 2j)}{j2 + (2 \parallel 2 - 2j)} (-12\angle 0^\circ)$$

$$V_0' = \frac{2}{2 - 2j} V_1$$

## EXAMPLE 7


## USE SOURCE TRANSFORMATION

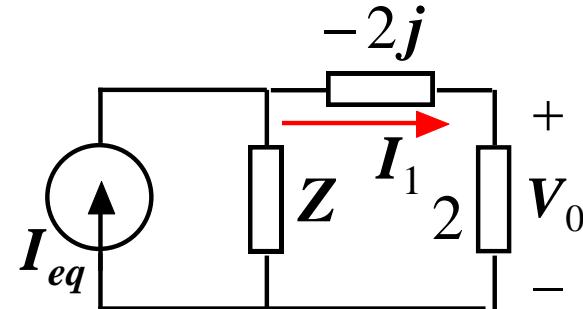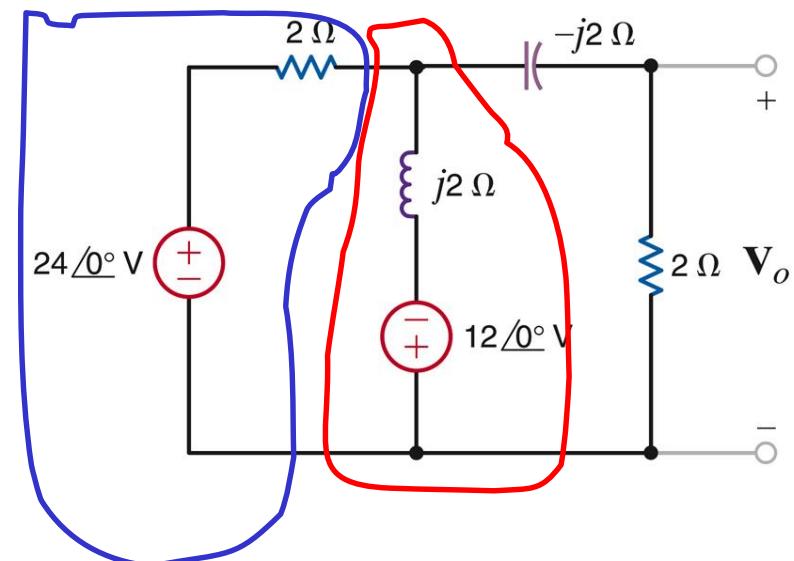

$$I_{eq} = 12\angle 0^\circ - 6\angle -90^\circ = 12 + 6j$$




$$I_1 = \frac{Z}{Z + 2 - 2j} I_{eq}$$

$$V_0 = 2I_1$$

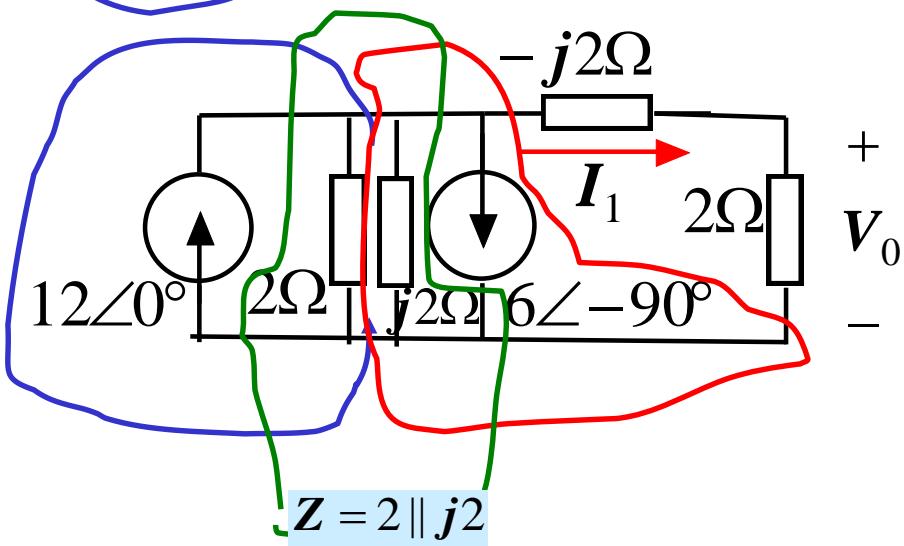

## EXAMPLE 7


## USE NORTON'S THEOREM

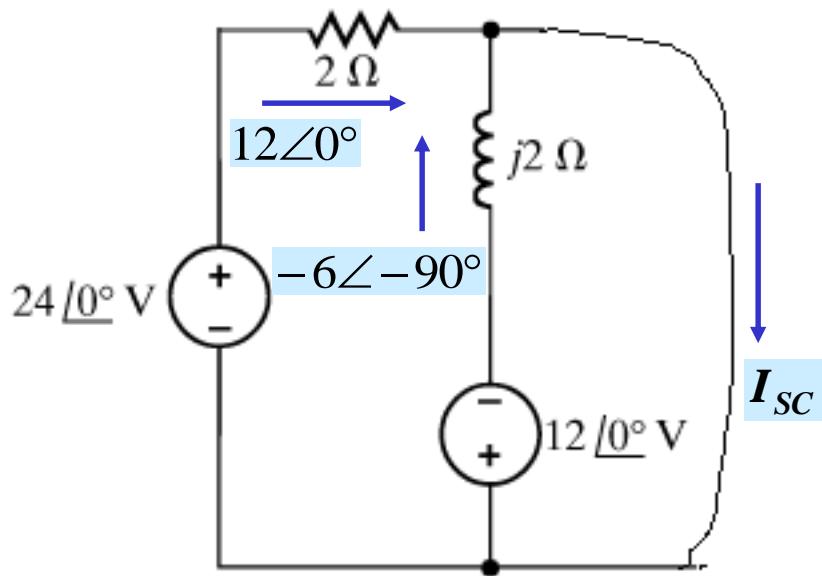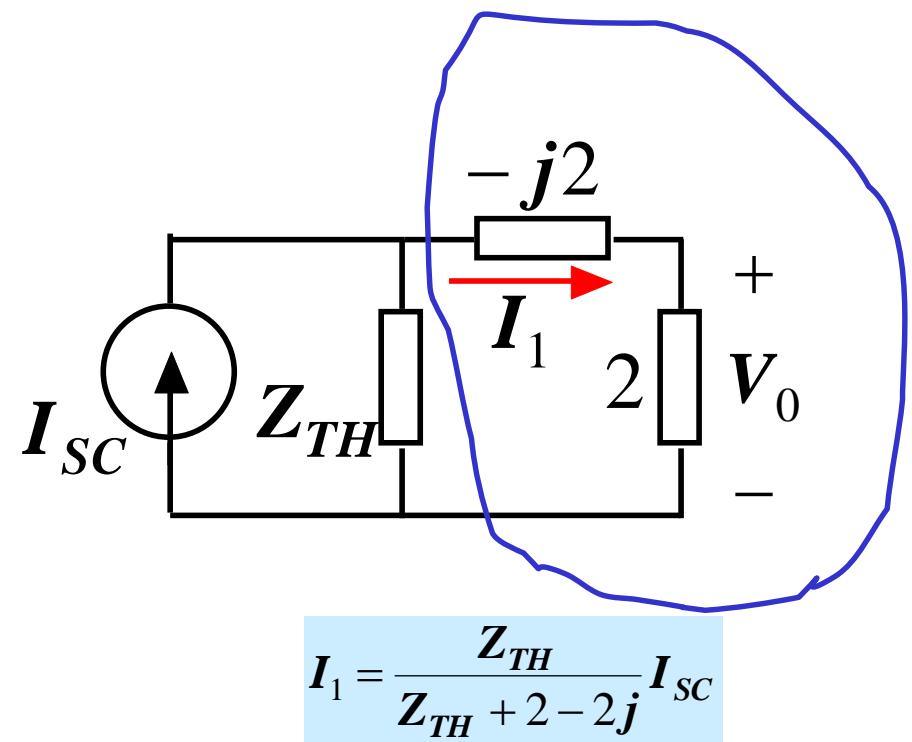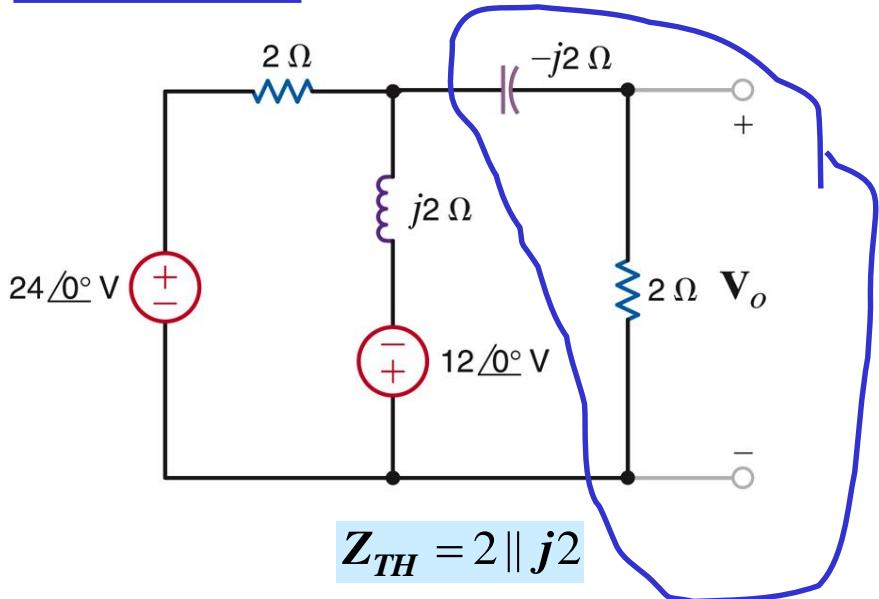





$$V_0 = 2I_1$$

## EXAMPLE 8
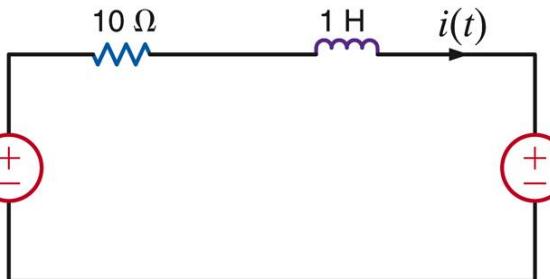
### Find the current $i(t)$ in steady state



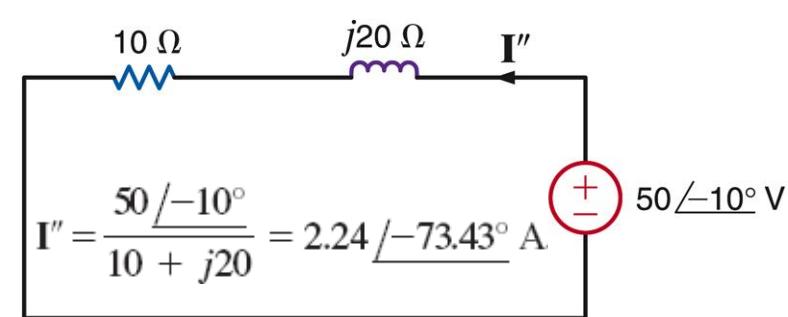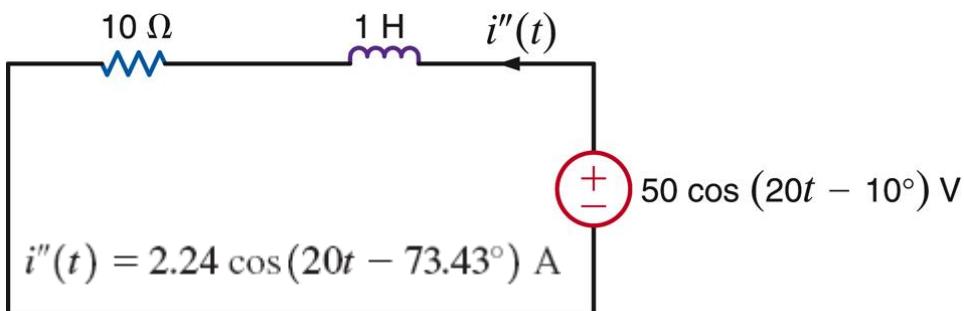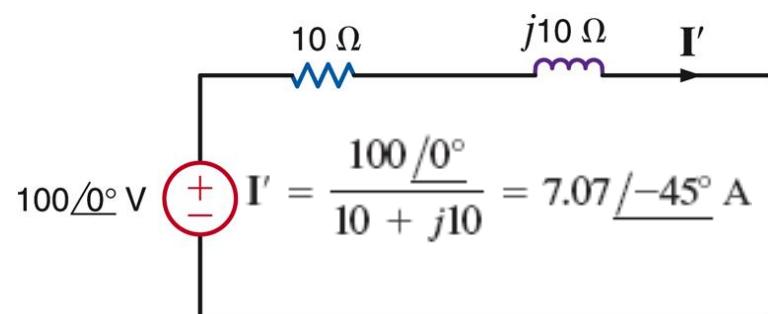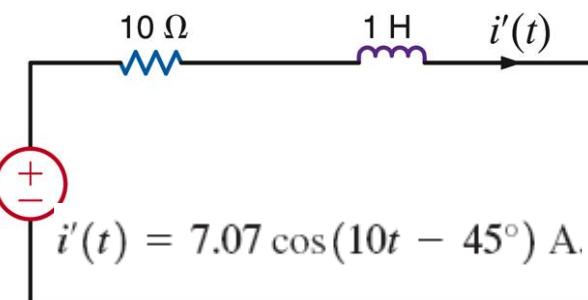The sources have different frequencies!  
For phasor analysis MUST use source superposition



### SOURCE 2: FREQUENCY 20r/s

$$i'(t) - i''(t) = 7.07 \cos(10t - 45^\circ) - 2.24 \cos(20t - 73.43^\circ) \text{ A}$$

### Principle of superposition

## USING MATLAB

MATLAB recognizes complex numbers in rectangular representation. It does NOT recognize Phasors

Unless previously re-defined, MATLAB recognizes “i” or “j” as imaginary units

```
» z2=3+4j  
  
z2 =  
  
    3.0000 + 4.0000i  
  
» z1=4+6i  
  
z1 =  
  
    4.0000 + 6.0000i
```


In its output MATLAB always uses “i” for the imaginary unit

Phasors  $\leftrightarrow$  Rectangular  $z = 10\angle 45^\circ$

```
» a=45; % angle in degrees  
» ar=a*pi/180, %convert degrees to radians  
ar =  
    0.7854  
» m=10; %define magnitude  
» x=m*cos(ar); %real part  
x =  
    7.0711  
» y=m*sin(ar); %imaginary part  
y =  
    7.0711  
» z=x+i*y  
z =  
    7.0711 + 7.0711i  
z = 7.0711 + 7.0711i;  
» mp=abs(z); %compute magnitude  
mp =  
    10  
» arr=angle(z); %compute angle in RADIANS  
arr =  
0.7854  
» adeg=arr*180/pi; %convert to degrees  
adeg =  
    45  
x=real(z)  
x=  
    7.0711  
y=imag(z)  
y=  
    7.0711
```

## EXAMPLE 1

## COMPUTE ALL NODE VOLTAGES

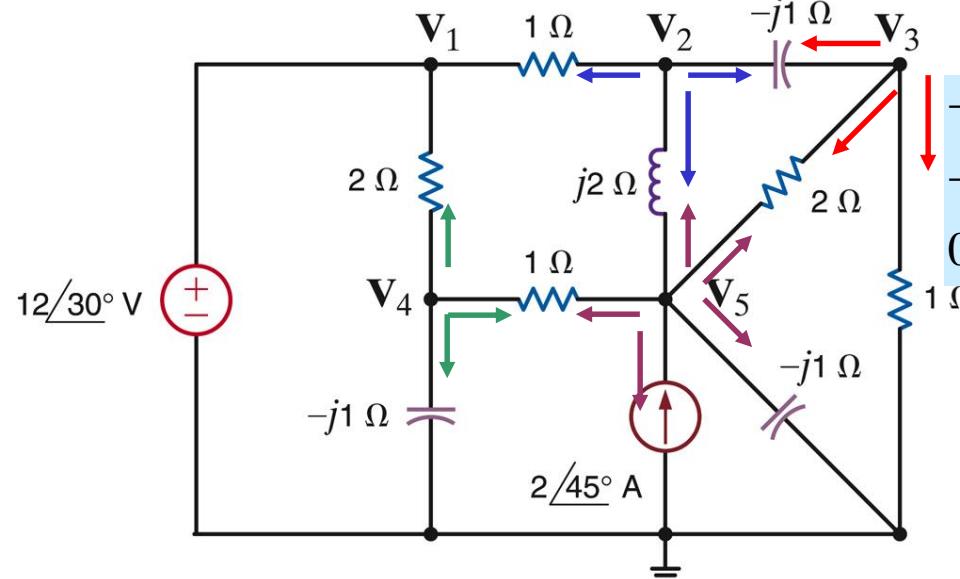

$$V_1 = 12\angle 30^\circ$$

$$-V_1 + (1 + j - 0.5j)V_2 - jV_3 - 0.5jV_5 = 0$$

$$-jV_2 + (j + 0.5 + 1)V_3 - 0.5V_5 = 0$$

$$-0.5V_1 + (0.5 + 1 + j)V_4 - V_5 = 0$$

$$0.5jV_2 - 0.5V_3 - V_4 + (1 - 0.5j + 0.5 + j)V_5 = 2\angle 45^\circ$$

$$V_1 = 12\angle 30^\circ$$

$$\frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{-j1} + \frac{V_2 - V_5}{j2} = 0$$

$$\frac{V_3 - V_2}{-j1} + \frac{V_3 - V_5}{2} + \frac{V_3}{1} = 0$$

$$\frac{V_4 - V_1}{2} + \frac{V_4 - V_5}{1} + \frac{V_4}{-j1} = 0$$

$$-2\angle 45^\circ + \frac{V_5 - V_4}{1} + \frac{V_5 - V_2}{j2} + \frac{V_5 - V_3}{2} + \frac{V_5}{-j1} = 0$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ -1 & 1+j0.5 & -j1 & 0 & j0.5 \\ 0 & -j1 & 1.5+j1 & 0 & -0.5 \\ -0.5 & 0 & 0 & 1.5+j1 & -1 \\ 0 & j0.5 & -0.5 & -1 & 1.5+j0.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} = \begin{bmatrix} 12\angle 30^\circ \\ 0 \\ 0 \\ 0 \\ 2\angle 45^\circ \end{bmatrix}$$

$$YV = I_R$$

$$V = Y^{-1}I_R$$

## EXAMPLE 1

```
%example8p18
%define the RHS vector.
ir=zeros(5,1); %initialize and define non zero values
ir(1)=12*cos(30*pi/180)+j*12*sin(30*pi/180);
ir(5)=2*cos(pi/4)+j*2*sin(pi/4), %echo the vector
%now define the matrix
y=[1,0,0,0,0; %first row
   -1,1+0.5j,-j,0,0.5j; %second row
   0,-j,1.5+j,0,-0.5; %third row
   -0.5,0,0,1.5+j,-1; %fourth row
   0,0.5i,-0.5,-1,1.5+0.5i] %last row and do echo
v=y\ir %solve equations and echo the answer
```

### Echo of Answer

v =

```
10.3923 + 6.0000i
7.0766 + 2.1580i
1.4038 + 2.5561i
3.7661 - 2.9621i
3.4151 - 3.6771i
```

### Echo of RHS

```
ir =
10.3923 + 6.0000i
```

0

0

0

```
1.4142 + 1.4142i
```

```
y =
Columns 1 through 4
```

1.0000

0

0

0

-1.0000

1.0000 + 0.5000i

0 - 1.0000i

0

0

0 - 1.0000i

1.5000 + 1.0000i

0

-0.5000

0

0

1.5000 + 1.0000i

0

0 + 0.5000i

-0.5000

-1.0000

Column 5

0

### Echo of Matrix

0 + 0.5000i


-0.5000

-1.0000


1.5000 + 0.5000i

## EXAMPLE 2

## FIND THE CURRENT $I_o$

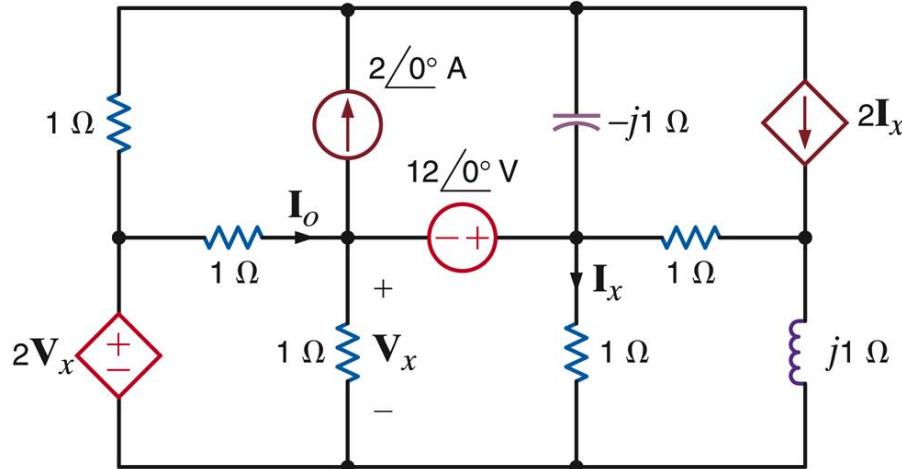

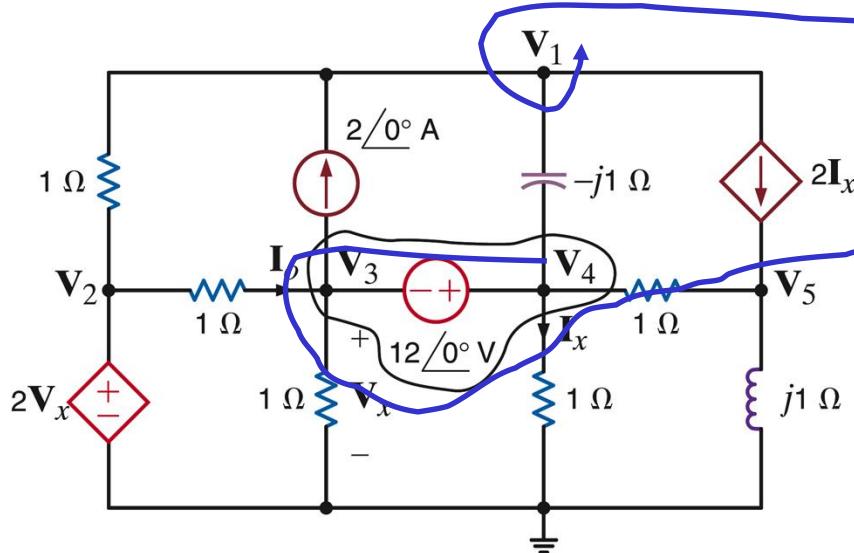6 meshes and two current sources  
5 non-reference nodes and two voltage sources... slight advantage for nodes



$$\frac{V_1 - V_2}{1} - 2 + \frac{V_1 - V_4}{-j} + 2I_x = 0$$

$$V_2 = 2V_x$$

$$V_4 - V_3 = 12$$

$$2 + \frac{V_3 - V_2}{1} + \frac{V_3}{1} + \frac{V_4}{1} + \frac{V_4 - V_5}{1} + \frac{V_4 - V_1}{-j} = 0$$

$$\frac{V_5 - V_4}{1} + \frac{V_5}{j} = 2I_x$$

$$V_x = V_3$$

$$I_x = \frac{V_4}{1}$$

## EXAMPLE 2

### NODE EQUATIONS

$$\frac{V_1 - V_2}{1} - 2 + \frac{V_1 - V_4}{-j} + 2I_x = 0$$

$$V_2 = 2V_x$$

$$V_4 - V_3 = 12$$

$$2 + \frac{V_3 - V_2}{1} + \frac{V_3}{1} + \frac{V_4}{1} + \frac{V_4 - V_5}{1} + \frac{V_4 - V_1}{-j} = 0$$

$$\frac{V_5 - V_4}{1} + \frac{V_5}{j} = 2I_x$$

$$V_x = V_3$$

$$I_x = \frac{V_4}{1}$$

### MATRIX FORM

$$\begin{bmatrix} 1+j & -1 & 0 & 2-j & 0 \\ 0 & 1 & -2 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ -j & -1 & 2 & 2+j & -1 \\ 0 & 0 & 0 & -3 & 1-j \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 12 \\ -2 \\ 0 \end{bmatrix}$$

```
>> Y = [1+j*1 -1 0 2-j*1; 0 1 -2 0 0; 0 0 -1 1 0;
       -j*1 -1 2 2+j*1 -1; 0 0 0 -3 1-j*1]
```

```
Y =
```

```
Columns 1 through 4
```

1.0000	+1.0000i	-1.0000	0	2.0000	-1.0000i
0		1.0000	-2.0000	0	
0		0	-1.0000	1.0000	
0	-1.0000i	-1.0000	2.0000	2.0000	+1.0000i
0		0	0	-3.0000	

```
Column 5
```

0
0
0

```
-1.0000
1.0000 -1.0000i
```

```
>> I = [2; 0; 12; -2; 0]
```

```
I =
-2
0
12
-2
0
```

```
>> V = inv(Y) * I
```

```
V =
-5.5000 +4.5000i
-26.0000 -24.0000i
-13.0000 -12.0000i
-1.0000 -12.0000i
16.5000 -19.5000i
```

## MATLAB COMMANDS


## LINEAR EQUATION


$$\begin{bmatrix} 1+j & -1 & 0 & 2-j & 0 \\ 0 & 1 & -2 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 \\ -j & -1 & 2 & 2+j & -1 \\ 0 & 0 & 0 & -3 & 1-j \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 12 \\ -2 \\ 0 \end{bmatrix}$$
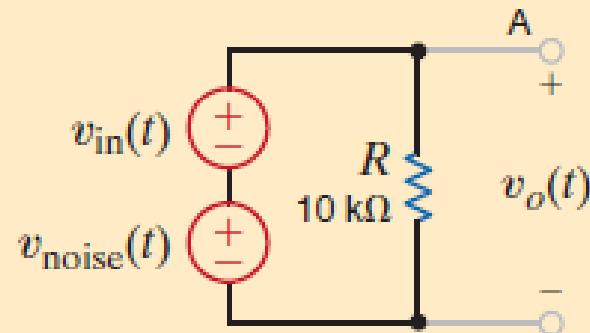
## ANSWER


$$\begin{aligned} I_o &= (V_2 - V_3)/1 \\ &= -13 - j12 \text{ A} \end{aligned}$$

The network in Fig. 8.28 models an unfortunate situation that is all too common. Node A, which is the voltage  $v_{in}(t)$  at the output of a temperature sensor, has “picked-up” a high-frequency voltage,  $v_{noise}(t)$ , caused by a nearby AM radio station. The noise frequency is 700 kHz. In this particular scenario, the sensor voltage, like temperature, tends to vary slowly. Our task then is to modify the circuit to reduce the noise at the output without disturbing the desired signal,  $v_{in}(t)$ .




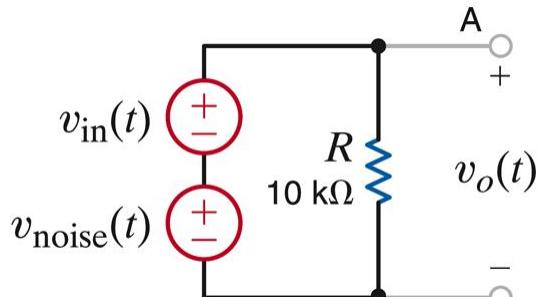

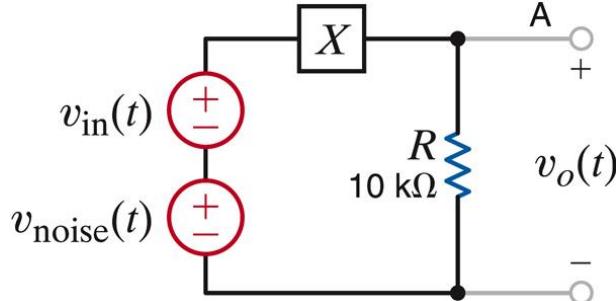Noise has much higher frequency (700kHz) than signal.  
Find a way to 'block' high frequencies



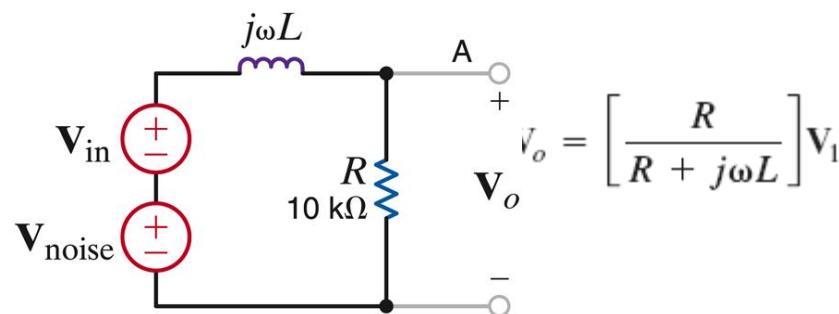Impedance  $X$  should have low (zero) value at low frequencies and very high at noise frequency



Reduce amplitude of noise by 10

$$\left| \frac{R}{R + j\omega L} \right| = \frac{1}{10} \quad \text{at } f = 700 \text{ mHz}$$

$$L = 22.6 \text{ mH}$$


A sinusoidal signal,  $v_1(t) = 2.5 \cos(\omega t)$  when added to a dc level of  $V_2 = 2.5$  V, provides a 0- to 5-V clock signal used to control a microprocessor. If the oscillation frequency of the signal is to be 1 GHz, let us design the appropriate circuit.

## LEARNING BY DESIGN

## PASSIVE SUMMING CIRCUIT - BIAS T NETWORK

$$v_o(t) = 2.5 + 2.5 \cos \omega t, \quad \omega = 2\pi f; f = 1\text{GHz}$$

### PROPOSED SOLUTION

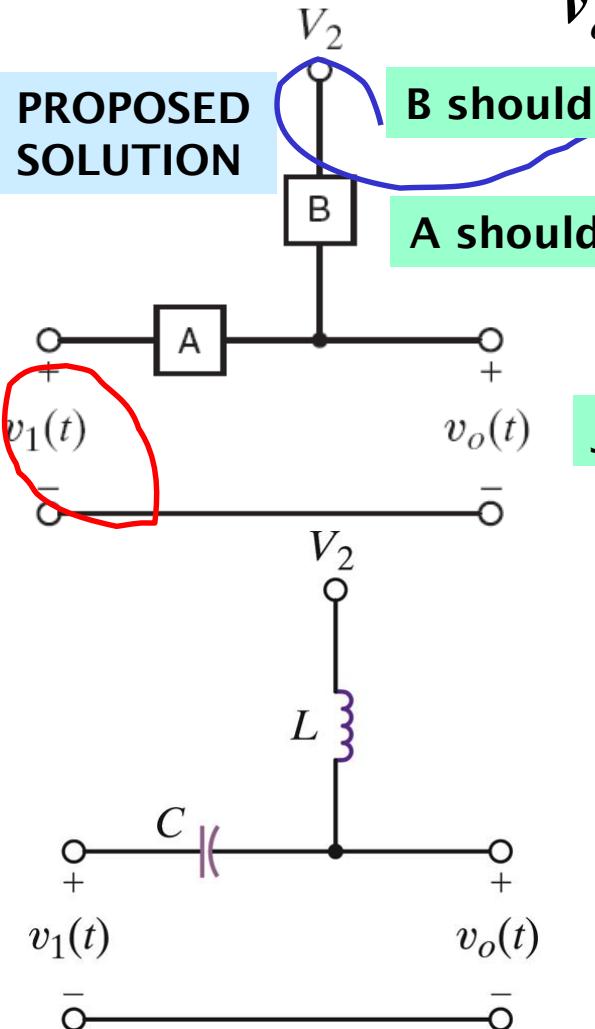

B should have zero impedance for DC and block high frequencies

A should block DC and have very low impedance at 1GHz

AT DC THE CAPACITOR IS ALWAYS OPEN CIRCUIT  
BUT AT 1GHz ONE WOULD NEED INFINITE INDUCTANCE.

JUST MAKE THE IMPEDANCES VERY DIFFERENT

PROPOSE  $\omega C = 1; L\omega = 10k\Omega; \omega = 2\pi \times 10^9$

$$C = \frac{1}{\omega X_C} = \frac{1}{2\pi \times 10^9} = 159 \text{ pF}$$

$$L = \frac{X_L}{\omega} = 1.59 \mu\text{H}$$

$$v_o(t) = 2.5 + 2.50025 \cos[2\pi 10^9 t]$$

# HOMEWORK I

- 8.4** Determine the phase angles by which  $v_1(t)$  leads  $i_1(t)$  and  $v_1(t)$  leads  $i_2(t)$ , where

$$v_1(t) = 4 \sin(377t + 25^\circ) \text{ V}$$

$$i_1(t) = 0.05 \cos(377t - 20^\circ) \text{ A}$$

$$i_2(t) = -0.1 \sin(377t + 45^\circ) \text{ A}$$

- 8.5** Calculate the current in the capacitor shown in Fig. P8.5 if the voltage input is

(a)  $v_1(t) = 10 \cos(377t - 30^\circ) \text{ V}$ .

(b)  $v_2(t) = 12 \sin(377t + 60^\circ) \text{ V}$ .

Give the answers in both the time and frequency domains.

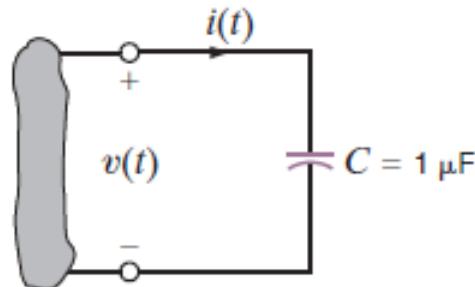


Figure P8.5

- 8.8** Find the equivalent admittance for the circuit in Fig. P8.8, if  $\omega = 10$  radians/second.

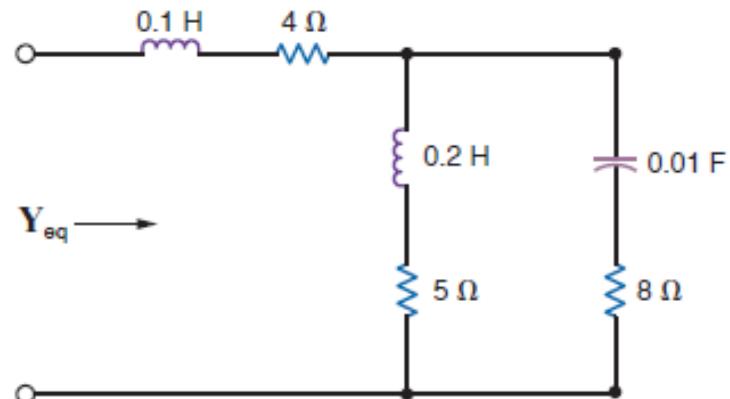


Figure P8.8

- 8.11** Find  $Z$  in the network in Fig. P8.11.

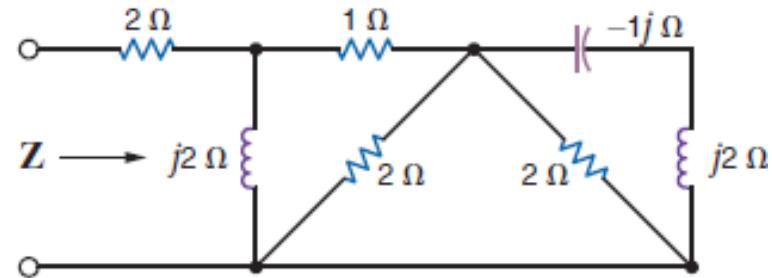


Figure P8.11

# HOMEWORK I

-  **8.18** The impedance of the network in Fig. P8.18 is found to be purely real at  $f = 400$  Hz. What is the value of  $C$ ?

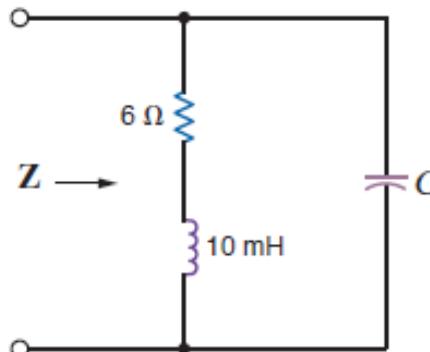


Figure P8.18

- 8.27** Find  $v_x(t)$  and  $v_R(t)$  in the circuit in Fig. P8.27 if  $v(t) = 50 \cos 10t$  V.

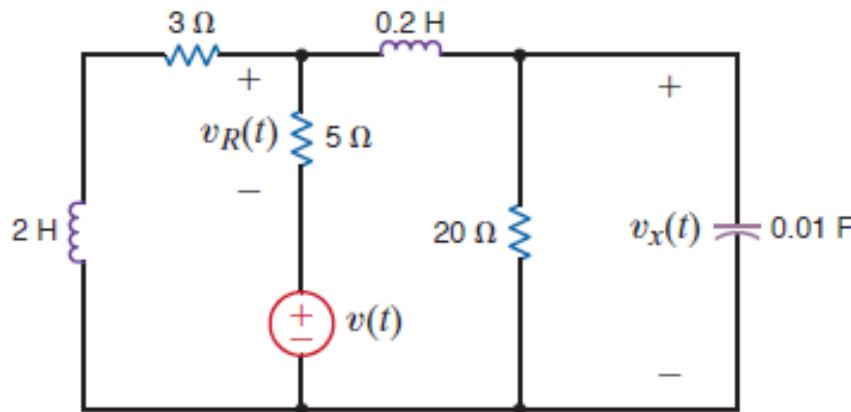


Figure P8.27

- 8.23** In the diagram in Fig. P8.23,  $v(t) = 50 \cos(10t + 10^\circ)$  V and  $i(t) = 25 \cos(10t + 41^\circ)$  A. Is the impedance of the BOX inductive or capacitive? Explain your answer.

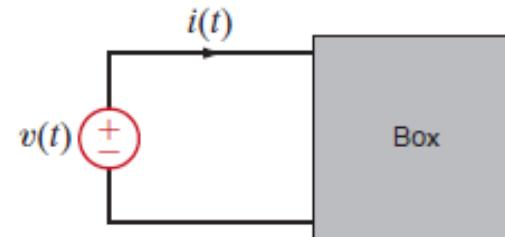


Figure P8.23

- 8.40** Find the voltage  $V_o$  shown in Fig. P8.40.

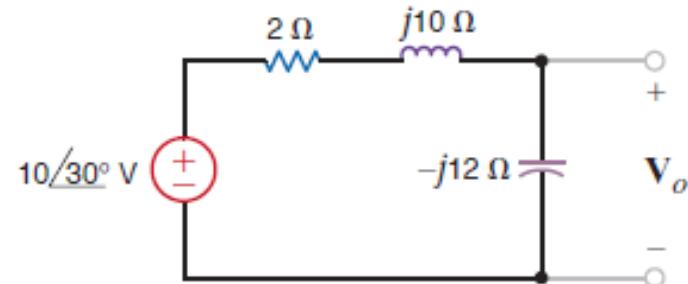


Figure P8.40

# HOMEWORK I

**8.51** Using nodal analysis, find  $\mathbf{I}_o$  in the circuit in Fig. P8.51.

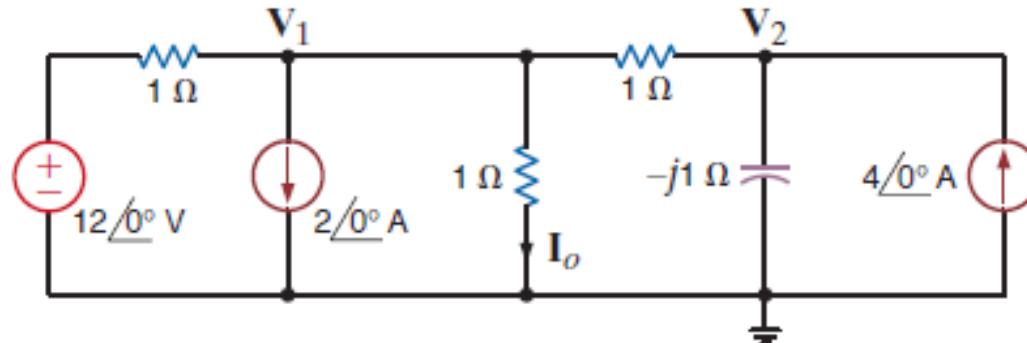


Figure P8.51

**8.53** Find  $\mathbf{V}_o$  in the network in Fig. P8.53 using nodal analysis.

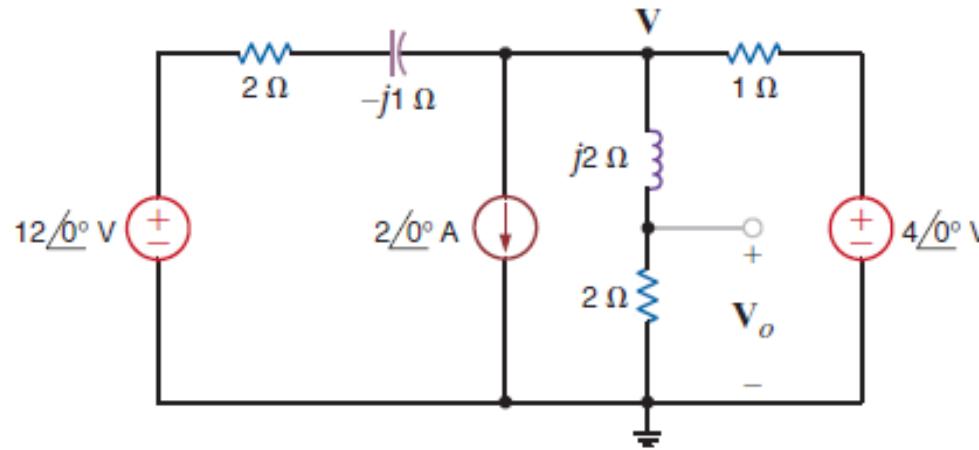


Figure P8.53

# HOMEWORK I

**8.71** Use loop analysis, to find  $V_o$  in the circuit in Fig. P8.71.

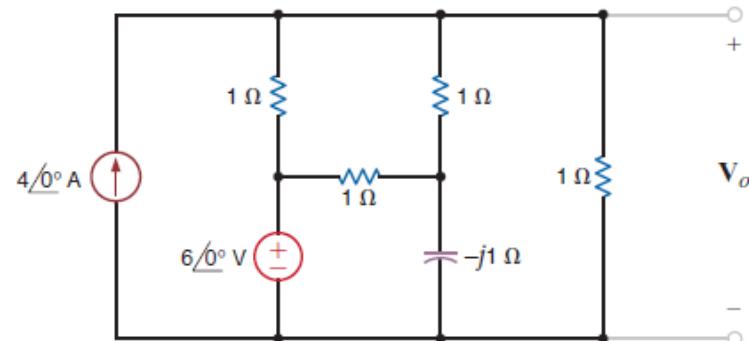


Figure P8.71

**8.74** Use mesh analysis to find  $V_o$  in the circuit in Fig. P8.74.

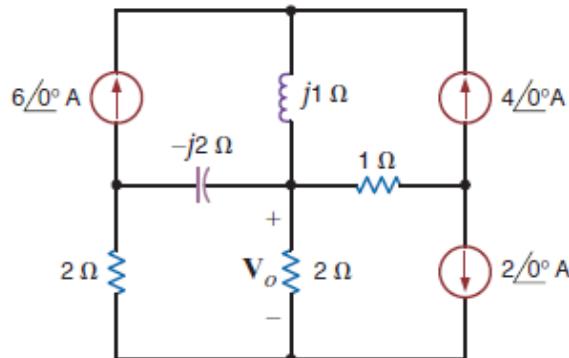


Figure P8.74

**8.90** Use superposition to find  $V_o$  in the circuit in Fig. P8.90.

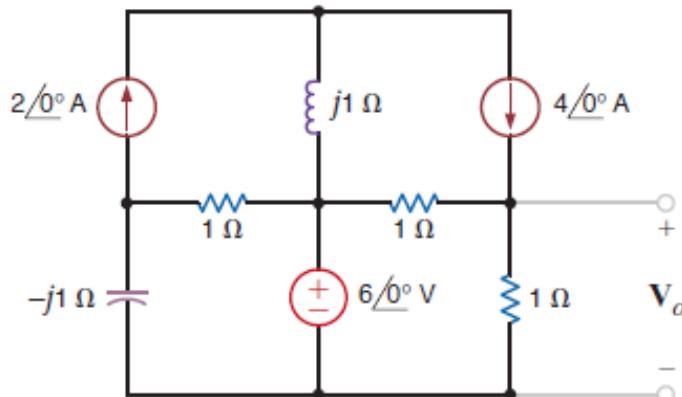


Figure P8.90

**8.97** Use source transformation to find  $V_o$  in the circuit in Fig. P8.97.

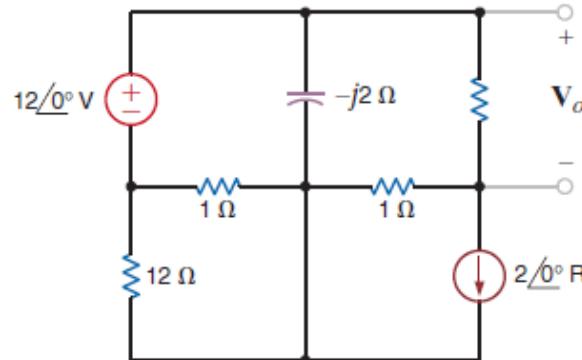


Figure P8.97

# HOMEWORK I

- 8.105** Use Thévenin's theorem to find  $V_o$  in the circuit in Fig. P8.105.

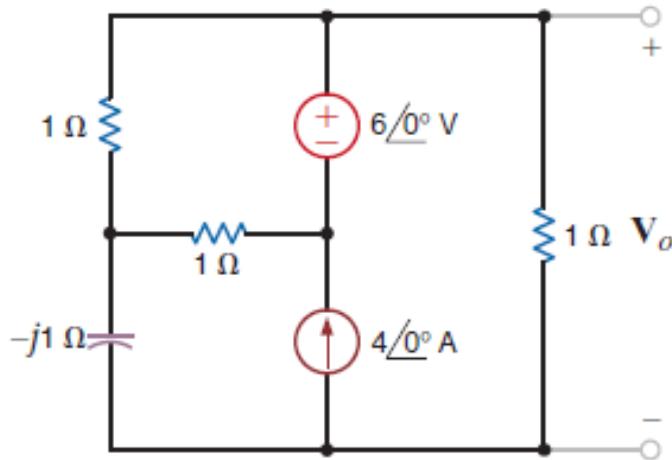


Figure P8.105

- 8.114** Find  $I_o$  in the network in Fig. P8.114 using Norton's theorem.

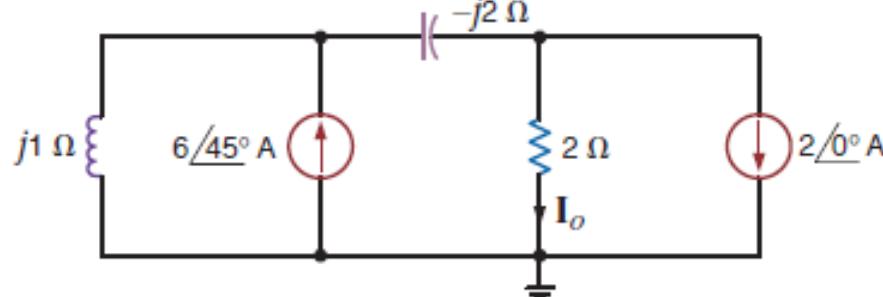


Figure P8.114

- 8.112** Find the Thévenin's equivalent for the network in Fig. P8.112 at terminals A–B.

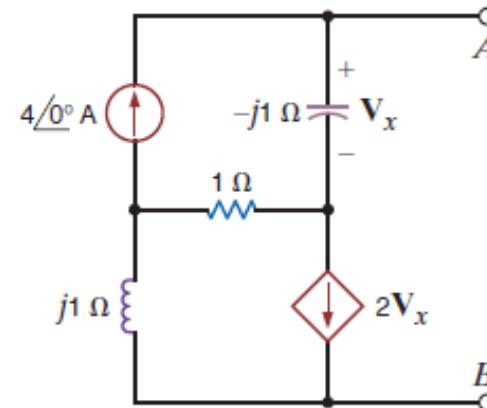


Figure P8.112

- 8.128** Apply Norton's theorem to find  $V_o$  in the network in Fig. P8.128.

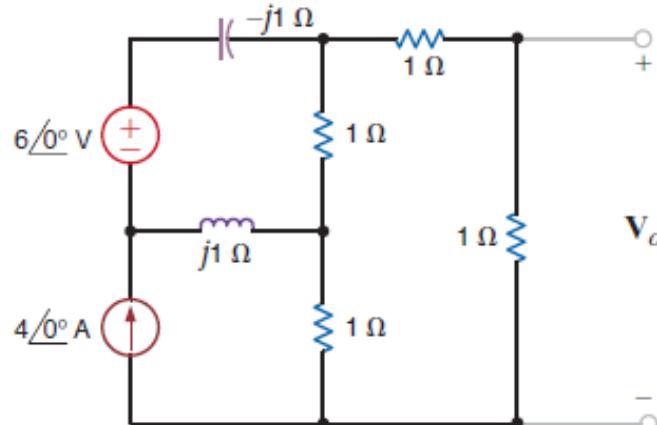


Figure P8.128