

EEE 472 POWER SYSTEM ANALYSIS II

Symmetrical Fault Analysis (Balanced 3-Phase Faults)

Z_{bus} Method


Prof. Dr. Saffet AYASUN

Department of Electrical and Electronics Engineering

Gazi University

Fault Analysis Using Impedance Matrix

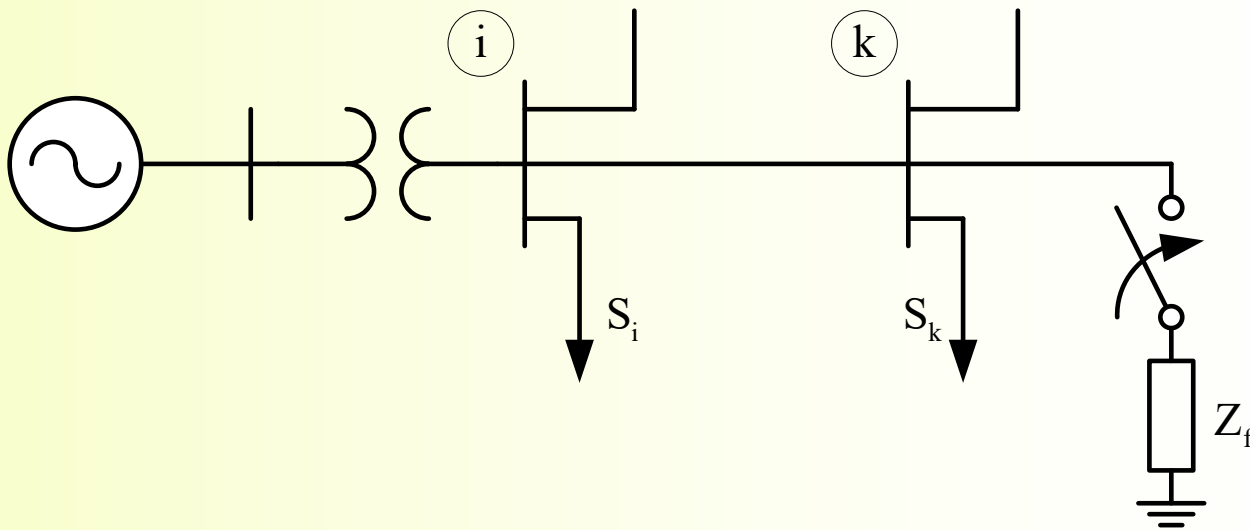- In a large network, an impedance matrix is readily available
- Matrix algebra formation
 - Seek a matrix where the diagonal elements represent the source impedance for the buses
- Consider the following system



- Balanced operation is assumed

Fault Analysis Using Impedance Matrix

- Place the prefault voltages into a vector


$$V_{bus}(0) = \begin{bmatrix} V_1(0) & \cdots & V_k(0) & \cdots & V_n(0) \end{bmatrix}^T$$

- Replace the loads by a constant impedance model using the prefault bus voltages

$$Z_i = \frac{|V_i(0)|^2}{S_i^*}$$

- The voltage change (ΔV) is determined by placing a fault voltage at the faulted bus with all the other sources short-circuited

Fault Analysis Using Impedance Matrix

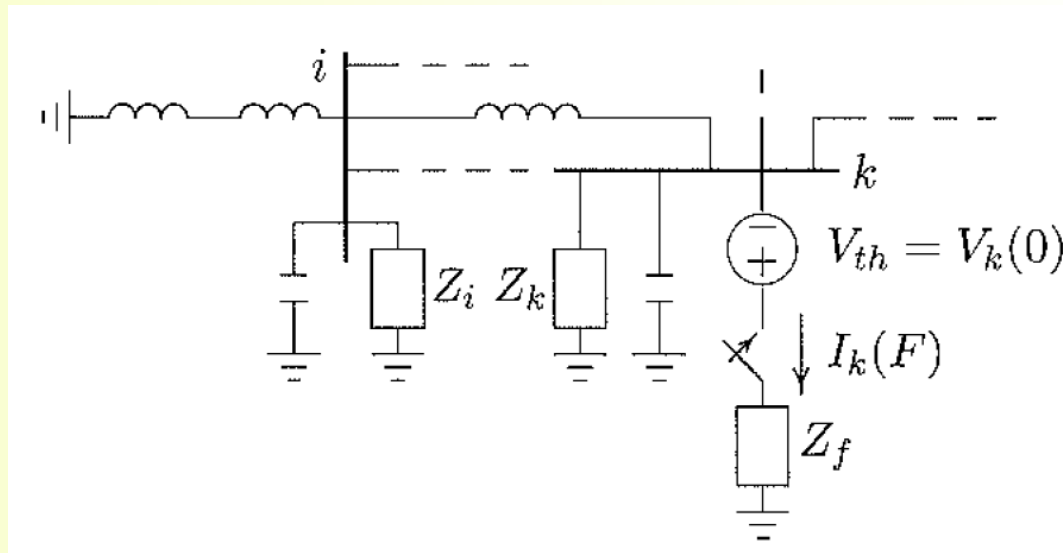

- **Superposition:** the fault voltages are calculated from the prefault voltages

$$\mathbf{V}_{\text{bus}}^f = \mathbf{V}_{\text{bus}}(0) + \Delta \mathbf{V}_{\text{bus}}$$

where bus voltage changes caused by the faulty

$$\Delta \mathbf{V}_{\text{bus}} = [\Delta V_1 \quad \cdots \quad \Delta V_k \quad \cdots \quad \Delta V_n]^T$$

Fault Analysis Using Impedance Matrix

- The change in bus voltages can be calculated from the network matrix

$$\begin{bmatrix} 0 \\ \vdots \\ -I_k(F) \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{11} & \cdots & Y_{1k} & \cdots & Y_{1n} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ Y_{k1} & \cdots & Y_{kk} & \cdots & Y_{kn} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ Y_{n1} & \cdots & Y_{nk} & \cdots & Y_{nn} \end{bmatrix} \begin{bmatrix} \Delta V_1 \\ \vdots \\ \Delta V_k \\ \vdots \\ \Delta V_n \end{bmatrix}$$

$$\mathbf{I}_{bus}(F) = \mathbf{Y}_{bus} \Delta \mathbf{V}_{bus}$$

Fault Analysis Using Impedance Matrix

- Solving for bus voltage changes

$$\Delta \mathbf{V}_{bus} = \mathbf{Z}_{bus} \mathbf{I}_{bus}(F)$$

$$\mathbf{Z}_{bus} = \mathbf{Y}_{bus}^{-1}$$

- The bus voltages during the fault:

$$\mathbf{V}_{bus}(F) = \mathbf{V}_{bus}(0) + \mathbf{Z}_{bus} \mathbf{I}_{bus}(F)$$

Fault Analysis Using Impedance Matrix

$$\begin{bmatrix} V_1(F) \\ \vdots \\ V_k(F) \\ \vdots \\ V_n(F) \end{bmatrix} = \begin{bmatrix} V_1(0) \\ \vdots \\ V_k(0) \\ \vdots \\ V_n(0) \end{bmatrix} + \begin{bmatrix} Z_{11} & \cdots & Z_{1k} & \cdots & Z_{1n} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ Z_{k1} & \cdots & Z_{kk} & \cdots & Z_{kn} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ Z_{n1} & \cdots & Z_{nk} & \cdots & Z_{nn} \end{bmatrix} \begin{bmatrix} 0 \\ \vdots \\ -I_k(F) \\ \vdots \\ 0 \end{bmatrix}$$

$$V_k(F) = V_k(0) - Z_{kk}I_k(F)$$

$$V_k(F) = Z_f I_k(F)$$


$$I_k(F) = \frac{V_k(0)}{Z_{kk} + Z_f}$$

Fault Analysis Using Impedance Matrix

- The bus voltage during the fault at bus i becomes

$$V_i(F) = V_i(0) - Z_{ik}I_k(F)$$


$$I_k(F) = \frac{V_k(0)}{Z_{kk} + Z_f}$$

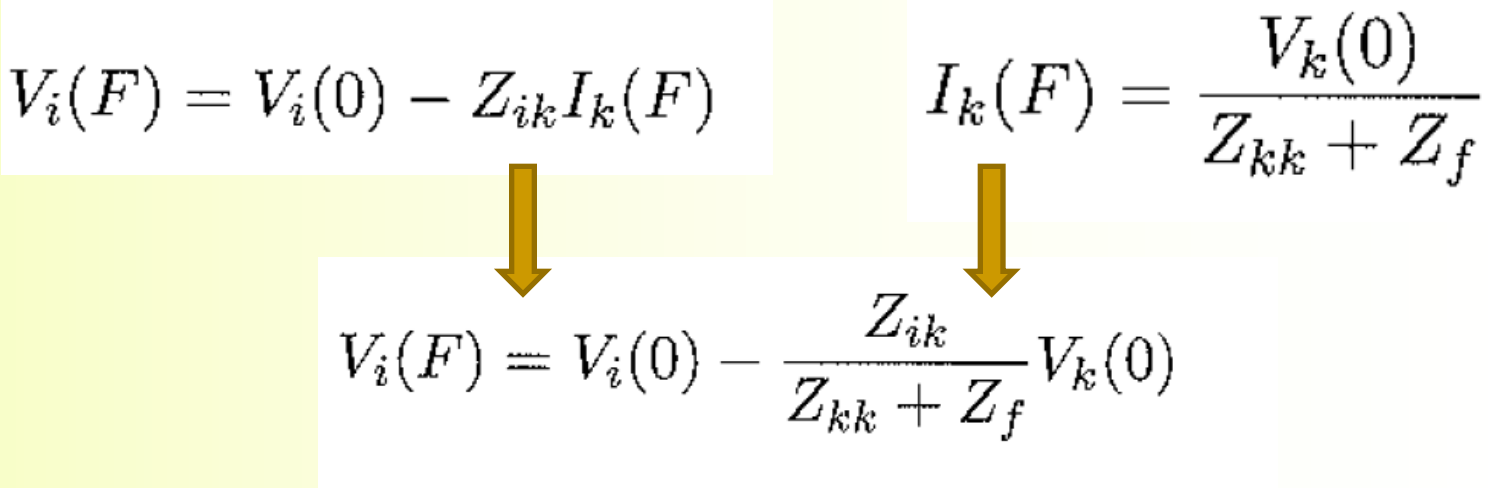
$$V_i(F) = V_i(0) - \frac{Z_{ik}}{Z_{kk} + Z_f} V_k(0)$$

- Note that for bolted fault $Z_f = 0$ and $V_k(F) = 0$
- With the knowledge of bus voltages during the fault, we can calculate the current in all the lines. For the line connecting bus i and j with impedance z_{ij} , the short-circuit current in this line


$$I_{ij}(F) = \frac{V_i(F) - V_j(F)}{z_{ij}}$$

Example 1

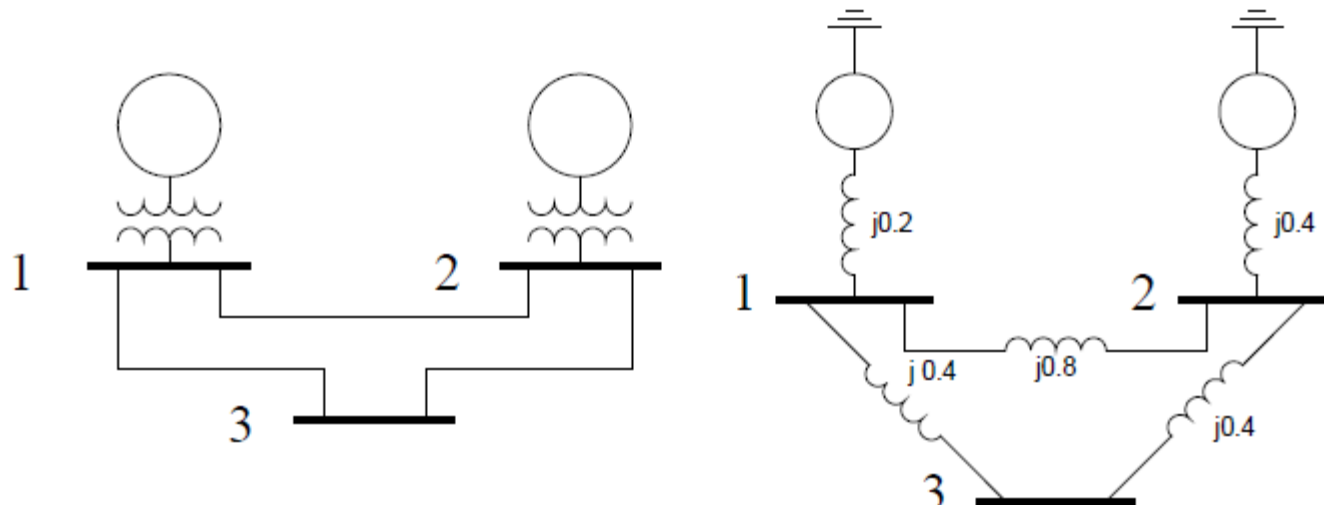


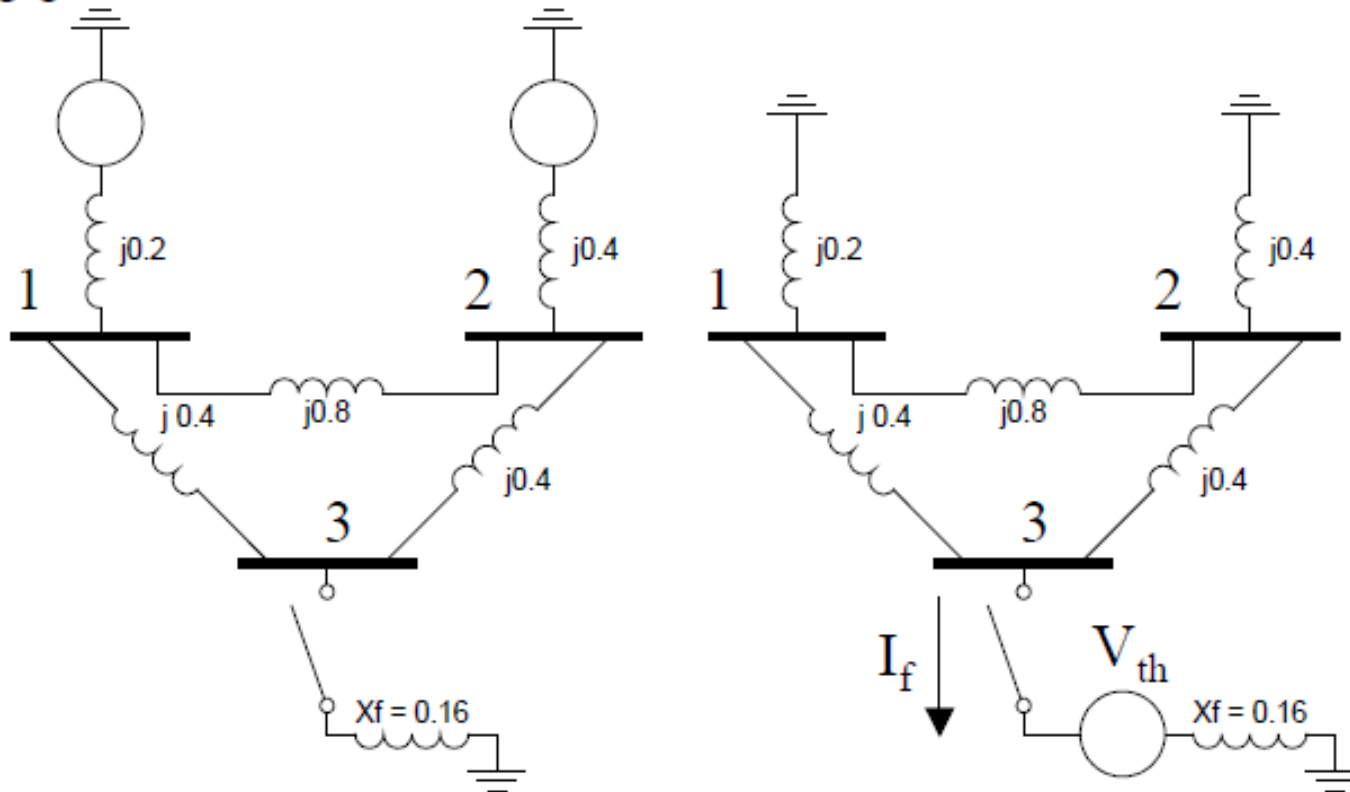Example 1 (cont'd)

- 3-phase fault with $Z_f = j0.16$ on bus 3
- bus 3



Example 1 (cont'd)

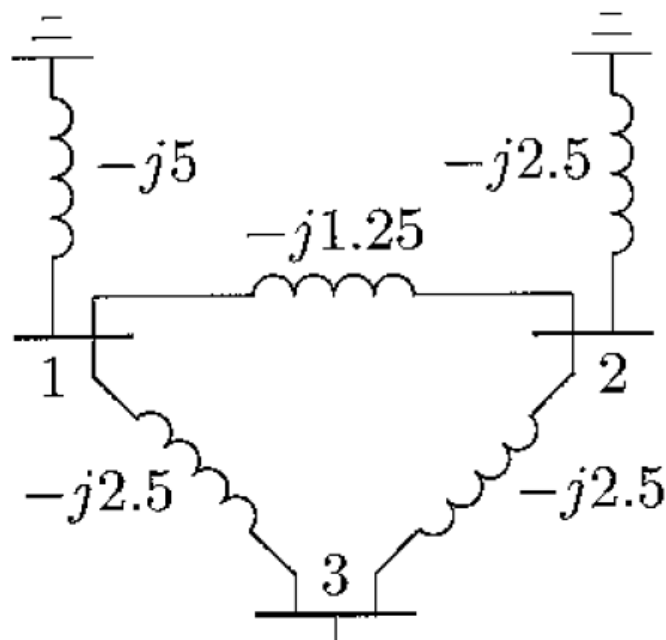

$$Y_{bus} = \begin{bmatrix} -j8.75 & j1.25 & j2.50 \\ j1.25 & -j6.25 & j2.50 \\ j2.50 & j2.50 & -j5.00 \end{bmatrix}$$

$$Z_{bus} = \begin{bmatrix} j0.16 & j0.08 & j0.12 \\ j0.08 & j0.24 & j0.16 \\ j0.12 & j0.16 & j0.34 \end{bmatrix}$$

$$I_3(F) = \frac{V_3(0)}{Z_{33} + Z_f} = \frac{1.0}{j0.34 + j0.16} = -j2.0 \text{ pu}$$

$$V_1(F) = V_1(0) - Z_{13}I_3(F) = 1.0 - (j0.12)(-j2.0) = 0.76 \text{ pu}$$

$$V_2(F) = V_2(0) - Z_{23}I_3(F) = 1.0 - (j0.16)(-j2.0) = 0.68 \text{ pu}$$

$$V_3(F) = V_3(0) - Z_{33}I_3(F) = 1.0 - (j0.34)(-j2.0) = 0.32 \text{ pu}$$


$$I_{12}(F) = \frac{V_1(F) - V_2(F)}{z_{12}} = \frac{0.76 - 0.68}{j0.8} = -j0.1 \text{ pu}$$

$$I_{13}(F) = \frac{V_1(F) - V_3(F)}{z_{13}} = \frac{0.76 - 0.32}{j0.4} = -j1.1 \text{ pu}$$

$$I_{23}(F) = \frac{V_2(F) - V_3(F)}{z_{23}} = \frac{0.68 - 0.32}{j0.4} = -j0.9 \text{ pu}$$

Example 2

- A 3-phase fault occurs at bus 2

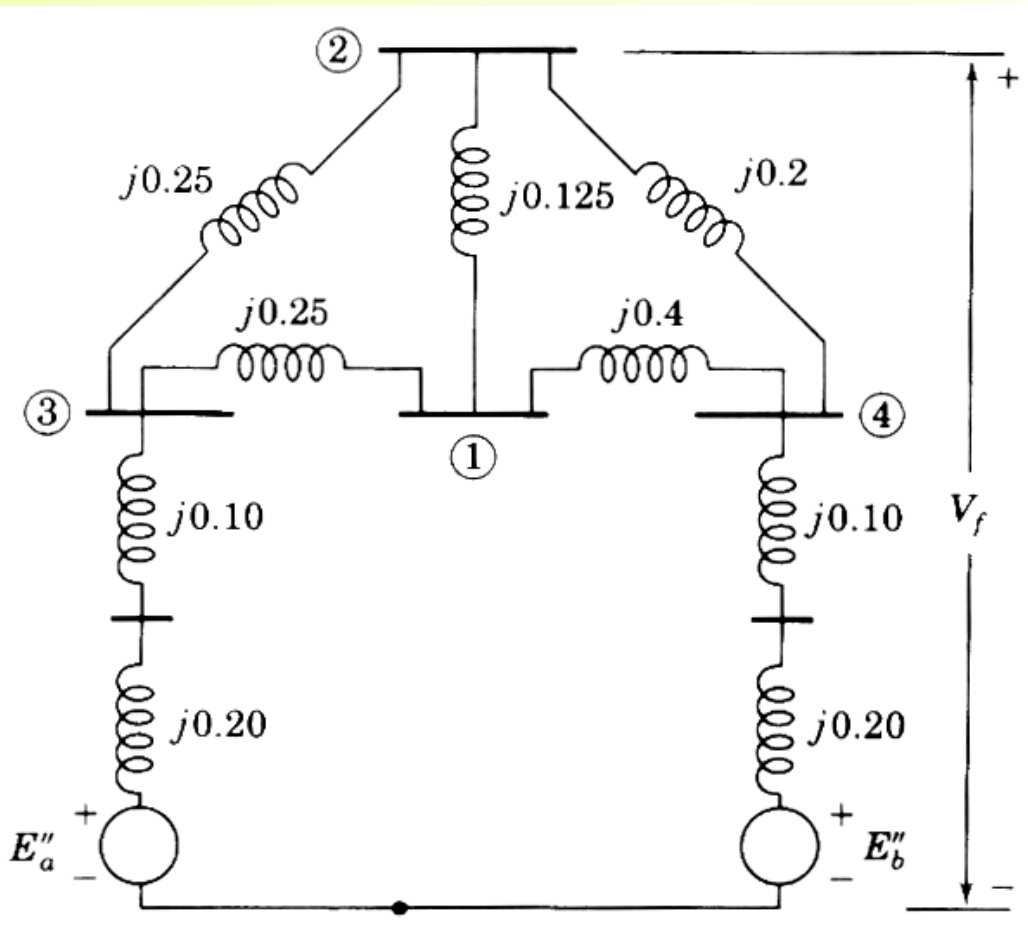

[Zbus]

$$j \begin{bmatrix} .2436 & .1938 & .1544 & .1456 \\ .2295 & .1494 & .1506 & \\ .1954 & .1046 & & \\ .1954 & & & \end{bmatrix}$$

$$V_f = 1.0 \angle 0 \text{ p.u.}$$

Example 2-Solution

- Fault current

$$I_f = V_f / Z_{22} = 1.0 / j0.2295 = -j4.3573 \text{ p.u.}$$

- Voltages during fault

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 1 - j0.1938 / j0.2295 \\ 0 \\ 1 - j0.1494 / j0.2295 \\ 1 - j0.1506 / j0.2295 \end{bmatrix} = \begin{bmatrix} 0.1556 \\ 0 \\ 0.3490 \\ 0.3438 \end{bmatrix}$$

- Fault currents contributed to bus 2


- From bus 1 $I_{f1} = V_1 / Z_{b1} = 0.1556 / j0.125 = -j1.2448 \text{ p.u.}$

- From bus 3 $I_{f3} = V_3 / Z_{b3} = 0.3490 / j0.25 = -j1.3960 \text{ p.u.}$


- From bus 4 $I_{f4} = V_4 / Z_{b4} = 0.3438 / j0.20 = -j1.7190 \text{ p.u.}$

Example 3

3. A three-phase fault occurs at the receiving end of the transmission line. By ignoring the pre-fault loading conditions, find the fault current using Z-bus method. (Choose $V_B=30$ kV of the generator voltage and $S_B = 100$ MVA) (25 pts)

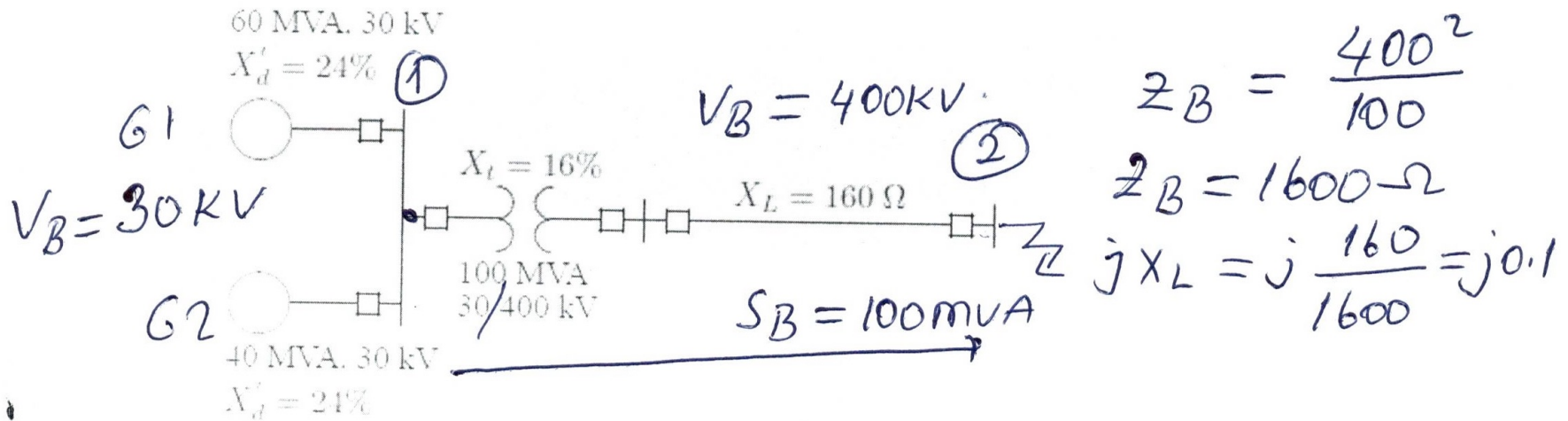

Example 3-Solution

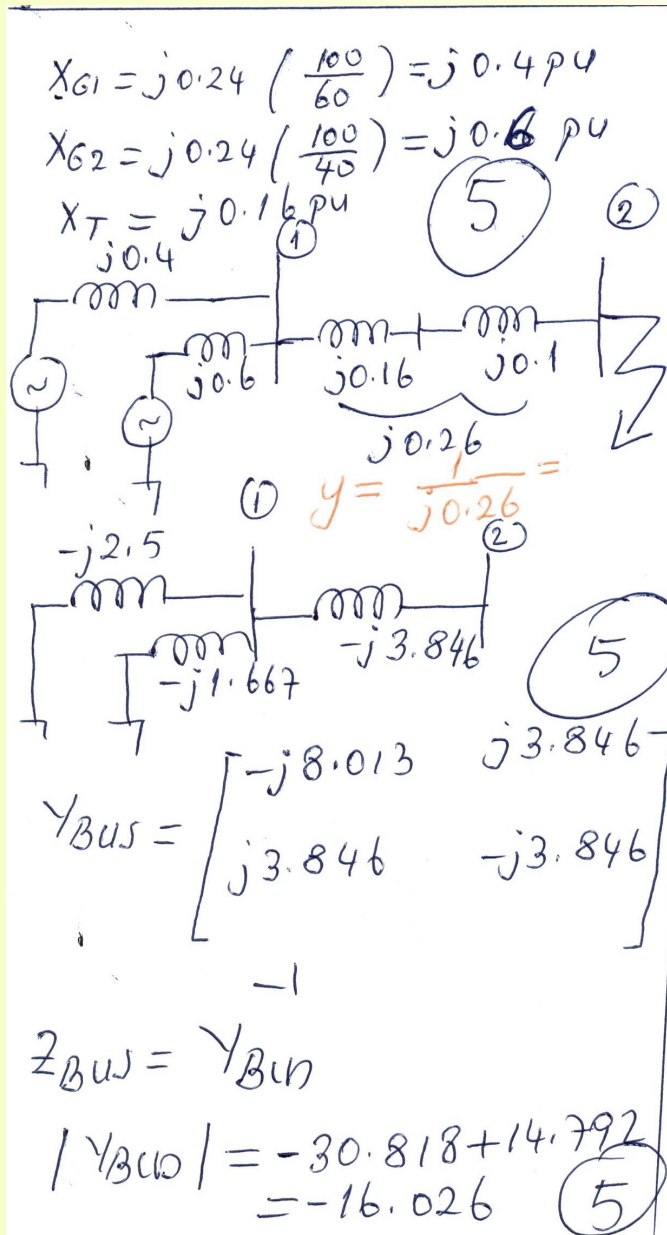

$Z_{Bus} = \frac{1}{-16.026} \begin{bmatrix} -j3.846 & j3.846 \\ -j3.846 & -j8.013 \end{bmatrix}$

$Z_{Bus} = \begin{bmatrix} j0.24 & j0.24 \\ j0.24 & j0.5 \end{bmatrix}$

$Z_{22} = j0.5 \text{ pu}$


$I_f = \frac{1.0}{j0.5} = -j2.0 \text{ pu}$

$I_B = \frac{100 \times 10^6}{\sqrt{3} (400 \times 10^3)} = 144.34 \text{ A}$

$I_f = (-j2.0 \text{ pu}) / (144.34)$
 $= -j288.68 \text{ A}$

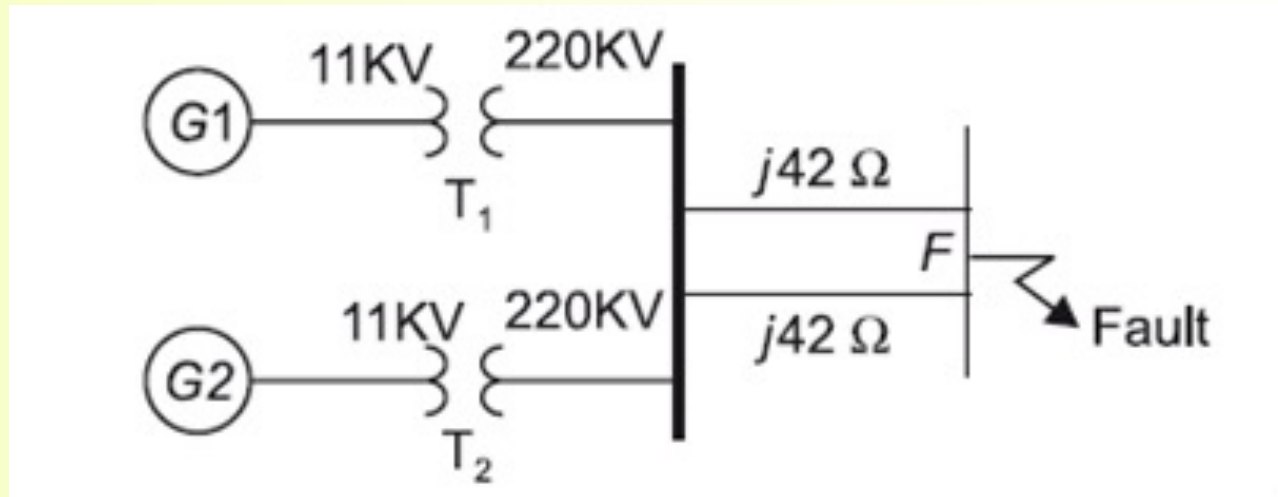Example 4

The figure given below shows a generating station feeding a 220 kV system. Determine total fault current and fault current supplied by each generator for a three-phase fault at the receiving end of the line.



$$G1 : 11 \text{ KV}, 100 \text{ MVA}, x'_{g1} = j0.15$$

$$G2 : 11 \text{ KV}, 75 \text{ MVA}, x'_{g2} = j0.125$$

$$T1 : 100 \text{ MVA}, x_{T1} = j0.10, 11/220 \text{ KV}$$

$$T2 : 75 \text{ MVA}, x_{T2} = j0.08, 11/220 \text{ KV}$$

Example 4 Solution

Let $S_B = 100 \text{ MVA}$, $V_B = 11 \text{ kV}$

$X_{G1} = j0.15 \text{ pu}$


$X_{G2} = j0.125 \left(\frac{100}{75} \right) = j0.167 \text{ pu}$

$X_{T1} = j0.10 \text{ pu}$

$X_{T2} = j0.08 \left(\frac{100}{75} \right) = j0.107 \text{ pu}$

$Z_B = \frac{V_B^2}{S_B} = \frac{220^2}{100} = 484 \Omega$

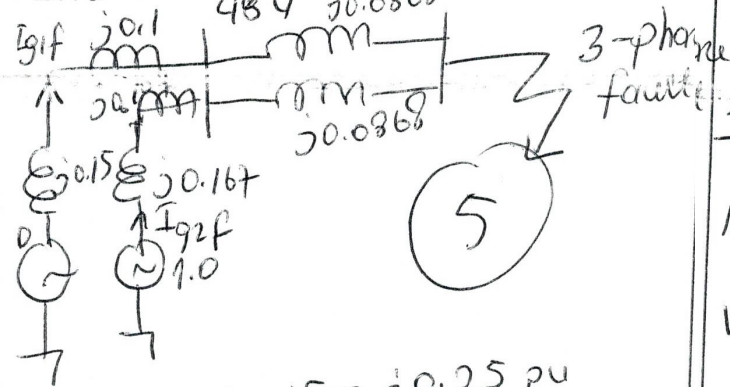$X_{\text{Line}} = \frac{j42}{484} = j0.0868 \text{ pu}$



$X_1 = j0.1 + j0.15 = j0.25 \text{ pu}$

$Y_1 = \frac{1}{X_1} = -j4 \text{ pu}$

$X_2 = j0.167 + j0.107 = j0.274 \text{ pu}$

$Y_2 = \frac{1}{X_2} = -j3.65 \text{ pu}$

$X_3 = j0.0868 // j0.0868$
 $= j0.0434 \text{ pu}$

$Y_3 = \frac{1}{X_3} = -j23.041 \text{ pu}$

$Y_{Bus} = \begin{bmatrix} -j30.69 & j23.041 \\ j23.041 & -j23.041 \end{bmatrix}$

$Z_{Bus} = Y_{Bus}^{-1} = \begin{bmatrix} j0.131 & j0.131 \\ j0.131 & j0.174 \end{bmatrix}$

The fault current:

$I_f = \frac{V_f}{Z_{22}} = \frac{1.0}{j0.174} = -j5.75 \text{ pu}$

$I_B = \frac{100 \times 10^6}{\sqrt{3} \times 220 \times 10^3} = 262.43 \text{ A}$

$|I_f| = 5.75 \times 262.43 = 1508.98 \text{ A}$

$V_1' = 1 - \frac{Z_{12}}{Z_{22}} = 1 - \frac{j0.131}{j0.174} = 0.247$

$V_2' = 0$
 $I_{G1f} = \frac{1 - 0.247}{j0.25} = -j3.012 \text{ pu}$


$I_{G2f} = \frac{1 - 0.247}{j0.274} = -j2.748 \text{ pu}$

$I_B = \frac{100 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 5248.6 \text{ A}$

$|I_{G2f}| = 14.423 \text{ kA}$
 $I_{\text{Total}} = 3.012 \times 5248 = 15.8 \text{ kA}$

Example 5

- For the three-bus system given below, a three-phase fault occurs at bus # 3. By ignoring the pre-fault loading conditions and using the Z-bus (bus impedance) method, compute the followings:
 - Fault current **(15)**
 - Bus voltages during the fault **(10)**
 - Fault currents of lines and generators**(10)**

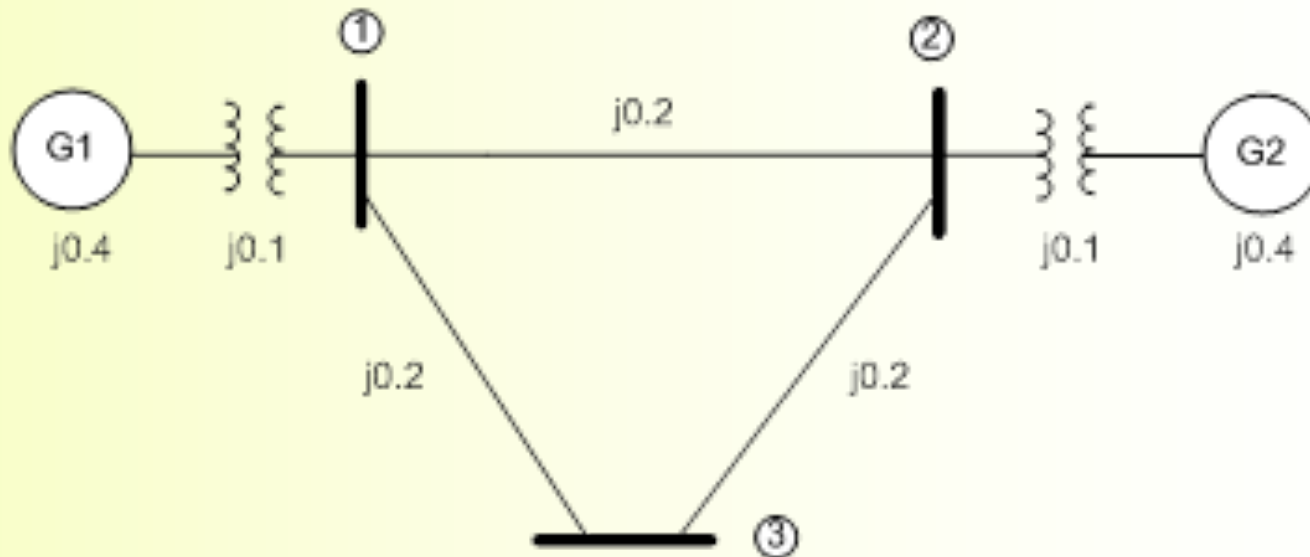


Example 5-Solution

$$Y_B = \begin{bmatrix} -j12 & j5 & j5 \\ j5 & -j12 & j5 \\ j5 & j5 & -j10 \end{bmatrix}$$

$$Z_B = Y_B^{-1} = \begin{bmatrix} j0.2793 & j0.2206 & j0.25 \\ j0.2206 & j0.2793 & j0.25 \\ j0.25 & j0.25 & j0.35 \end{bmatrix}$$

a) Fault current

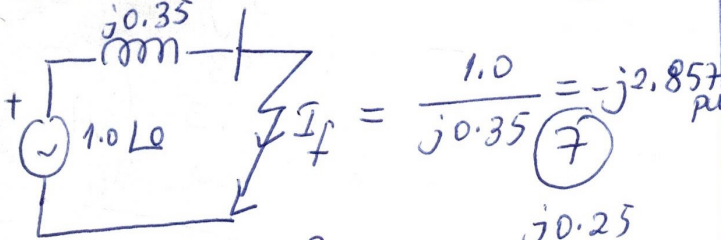

$$b) V_1' = 1 - \frac{Z_{13}}{Z_{33}} = 1 - \frac{j0.25}{j0.35}$$

$$V_1' = 0.2857 \text{ pu}$$

$$V_2' = 1 - \frac{Z_{22}}{Z_{33}} = 1 - \frac{j0.25}{j0.35}$$

$$V_2' = 0.2857 \text{ pu}$$

$$V_3' = 0 \text{ pu}$$

c) Lines and generator fault currents:

Ignoring pre-fault loading condition:

$$I_{G1} = \frac{1.0 - 0.2857}{j0.5} = -j1.4286 \text{ pu}$$

$$I_{G2} = \frac{1.0 - 0.2857}{+j0.5} = -j1.4286 \text{ pu}$$


$$I_{12} = \frac{0.2857 - 0.2857}{j0.2} = 0 \text{ pu}$$

$$I_B = \frac{0.2857 - 0}{j0.2} = -j1.4285 \text{ pu}$$


$$I_{23} = \frac{0.2857 - 0}{j0.2} = -j1.4285 \text{ pu}$$

Example 6

The two-bus system below provides power to the motor when the voltage of the bus 1 is $V_1 = 0.9 \angle 0^\circ$ pu and the generator current is $I_G = 1.0 \angle 36.87^\circ$ pu. A three-phase fault occurs at bus 2. **Using the Z-bus matrix (bus impedance matrix)** find the fault current, the contribution of the generator and the motor to the fault current and bus voltages during the fault (35 p)

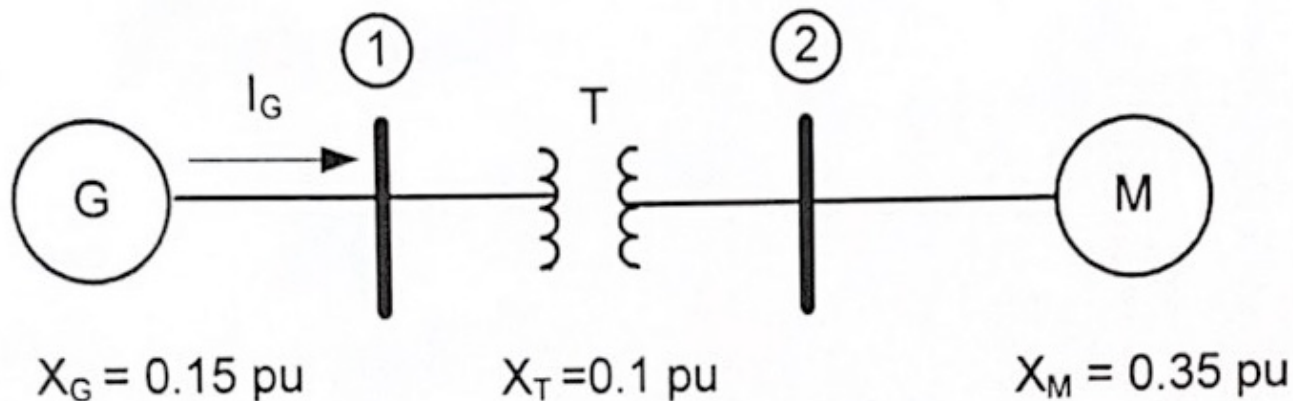

Example 6-Solution

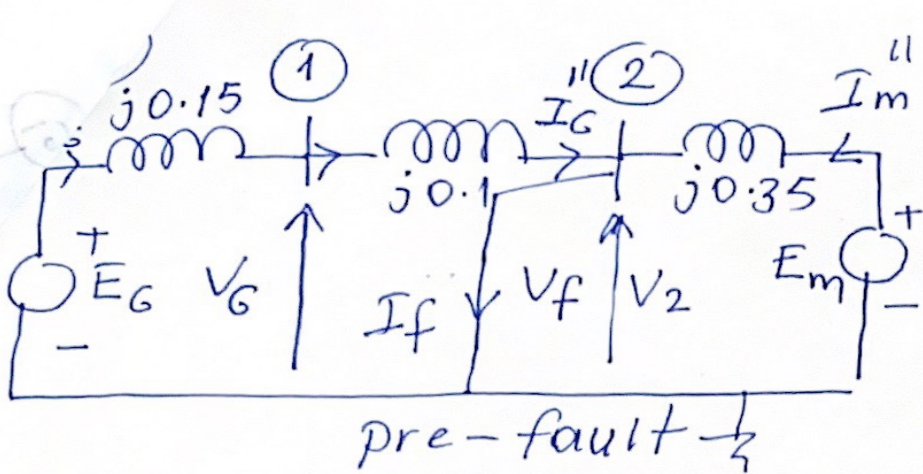

Pre-fault load conditions:

$$V_G = V_1 = 0.9 \angle 0^\circ$$


$$I_G = 1.0 \angle 36.87^\circ \text{ pu}$$

The voltage at bus (2) before the fault:

$$V_2 = V_f = V_G - jX_T I_G$$

$$V_f = 0.9 \angle 0^\circ - (j0.1)(1.0 \angle 36.87^\circ)$$
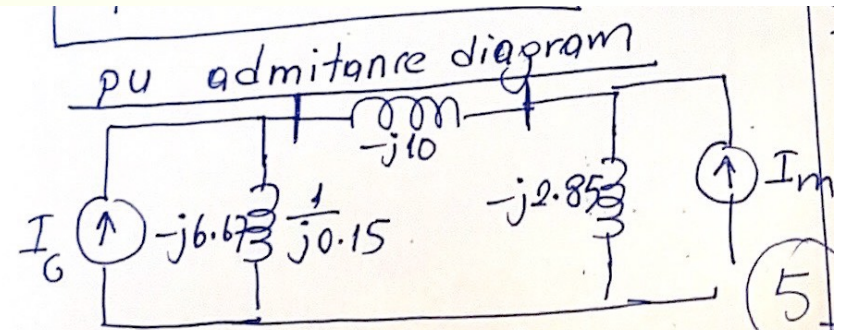
$$V_f = 0.963 \angle -4.76^\circ \text{ pu}$$



Bus admittance matrix:

$$Y_{Bus} = \begin{bmatrix} -j16.67 & j10 \\ j10 & -j12.85 \end{bmatrix}$$

$$Z_{Bus} = [Y_{Bus}]^{-1} = \begin{bmatrix} j0.112 & j0.087 \\ j0.087 & j0.146 \end{bmatrix}$$

Example 6-Solution

The fault current

$$I_f'' = \frac{V_f}{Z_{22}} = \frac{0.963 \angle -4.76^\circ}{j0.146}$$

$$I_f'' = 6.596 \angle -94.76^\circ \text{ pu}$$

Bus voltage during fault:

$$V_2' = 0$$

$$V_1' = V_1 - I_f'' Z_{12}$$

$$V_1' = 0.9 \angle 0^\circ - (6.596 \angle -94.76^\circ) \cdot (j0.087)$$

$$V_1' = 0.331 \angle 8.25^\circ \text{ pu}$$

The contribution of the generator and the motor to the fault current:

$$I_G'' = \frac{V_1' - V_2'}{Z_{1-2}}$$

$$I_G'' = \frac{0.331 \angle 8.25^\circ - 0}{j0.1}$$

$$I_G'' = 3.31 \angle -81.75^\circ \text{ pu}$$

$$I_f'' = I_G'' + I_m''$$


$$I_m'' = I_f'' - I_G''$$

$$I_m'' = 6.596 \angle -94.76^\circ - 3.31 \angle -81.75^\circ$$

$$I_m'' = -1.022 - j3.298$$

$$I_m'' = 3.45 \angle -113.72^\circ \text{ pu}$$


Example 7

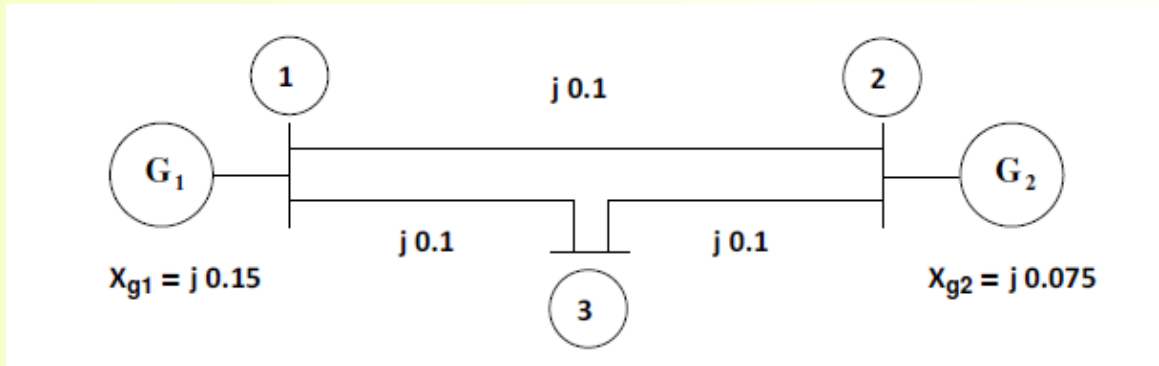

A three-bus power system is shown above. The p.u. impedances are on a base of 50 MVA and 12 kV. A three-phase symmetrical short circuit occurs at bus 3 with no fault impedance. Using Z-bus matrix method and ignoring pre-fault loading conditions:

- Compute the short-circuit current (20)
- Bus voltages during fault (5)
- Contributions of generators to the short-circuit current (5)

Example 7-Solution

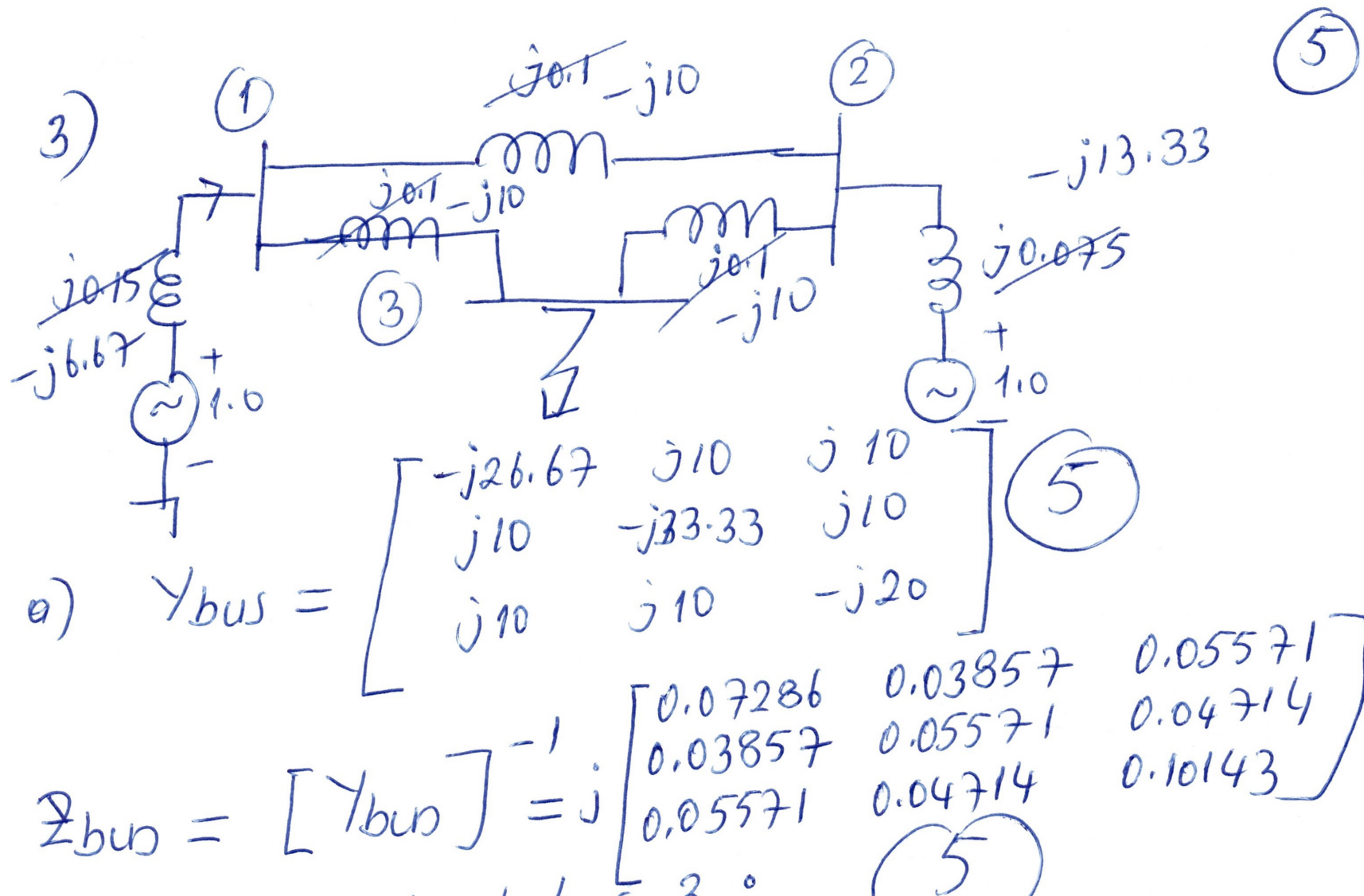

Example 7-Solution (cont'nd)

short circuit at bus 3 :

$$I_{3f} = \frac{1}{j0.10143} = -j9.86 \text{ pu}$$

$$\text{Base current } I_B = \frac{50 \times 10^6}{\sqrt{3} (12 \times 10^3)} = 2405.6 \text{ A}$$

(10)

$$\text{Fault current } I_{3f} = (-j9.86)(2405.6) = -j23.72 \text{ kA}$$

$$b) V_1 = 1.0 - \frac{Z_{13}}{Z_{33}} = 1.0 - \frac{j0.05571}{j0.10143} = 0.451 \text{ pu}$$

(5)

$$V_2 = 1.0 - \frac{Z_{23}}{Z_{33}} = 1.0 - \frac{j0.04714}{j0.10143} = 0.535 \text{ pu}$$

$$V_3 = 0 \text{ pu}$$

$$c) I_{G1} = \frac{1 - 0.451}{j0.15} = -j3.66 \text{ pu or}$$

$$I_{G1} = (-j3.66)(2405.6) = -j8.804 \text{ kA}$$

(5)

$$I_{G2} = \frac{1 - 0.535}{j0.075} = -j6.2 \text{ pu}$$

$$I_{G2} = (-j6.2)(2405.6) = -j14.91 \text{ kA}$$