

EEE472 POWER SYSTEM ANALYSIS II


BUS ADMITANCE MATRIX

Prof. Dr. Saffet AYASUN


Department of Electrical and Electronics Engineering

Gazi University

What is a Power System?

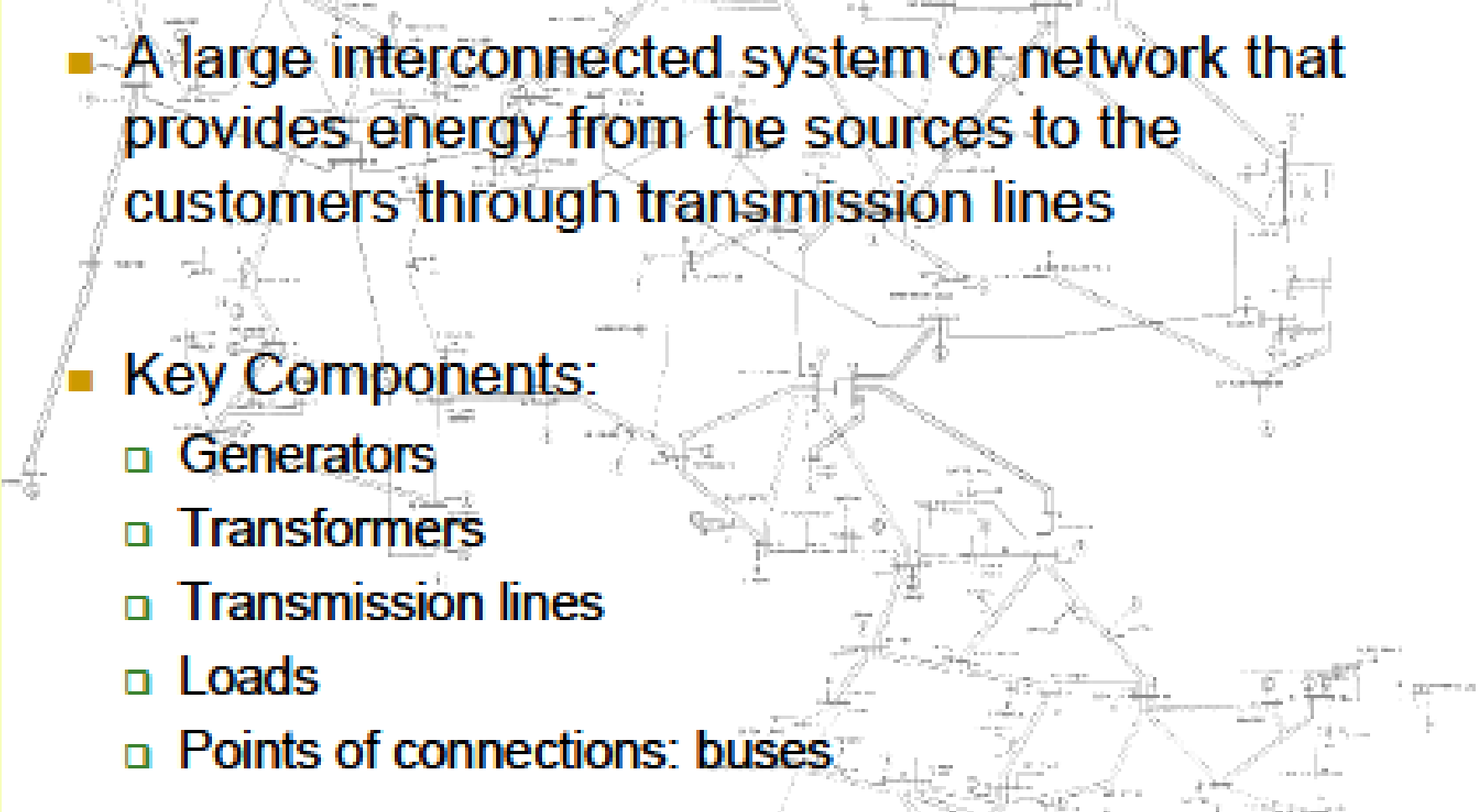- 
- A large interconnected system or network that provides energy from the sources to the customers through transmission lines
 - Key Components:
 - Generators
 - Transformers
 - Transmission lines
 - Loads
 - Points of connections: buses

Electric Power Network

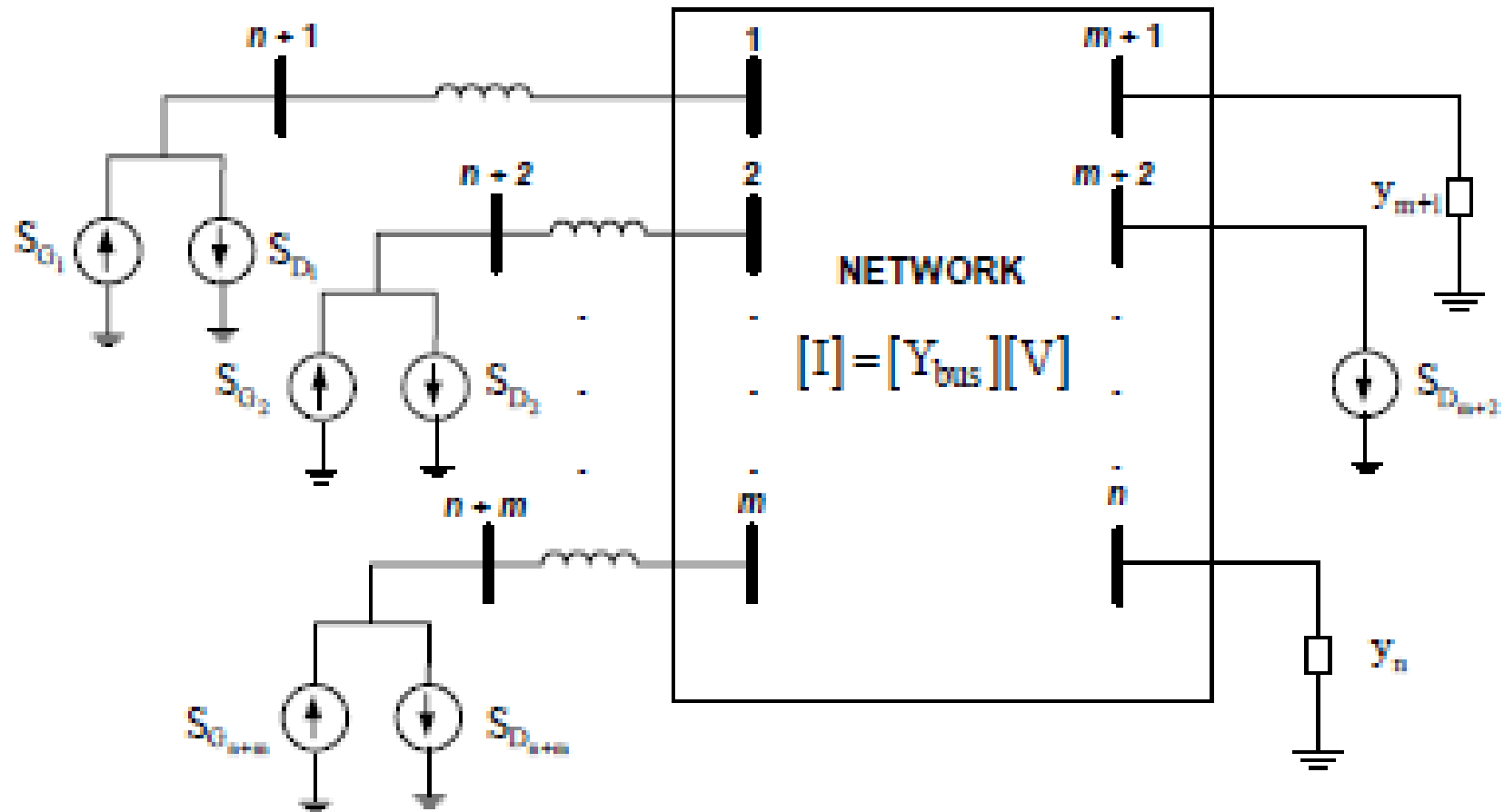


Bus Admittance Matrix

- The injected currents at the nodes of the interconnected network are related to the voltages at the nodes via an admittance representation

$$\mathbf{I} = \mathbf{Y}_{\text{bus}} \mathbf{V}$$

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \vdots \\ \mathbf{I}_N \end{bmatrix} = \begin{bmatrix} \mathbf{Y}_{11} & \mathbf{Y}_{12} & \cdots & \mathbf{Y}_{1N} \\ \mathbf{Y}_{21} & \mathbf{Y}_{22} & \cdots & \mathbf{Y}_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ \mathbf{Y}_{N1} & \mathbf{Y}_{N2} & \cdots & \mathbf{Y}_{NN} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \\ \vdots \\ \mathbf{V}_N \end{bmatrix}$$

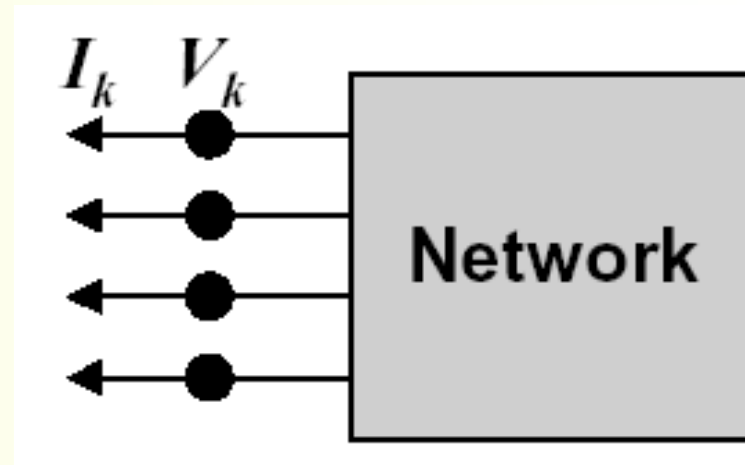

where $\mathbf{I}$ = vector of injected node currents

$\mathbf{Y}_{\text{bus}}$ = bus admittance matrix

$\mathbf{V}$ = vector of node voltages

Bus Admittance Matrix

- Used to form the network model of an interconnected power system
 - Nodes represent substation bus bars
 - Branches represent transmission lines and transformers
 - Injected currents are the flows from generator and loads
- Notes on bus admittance:
 - Large
 - Has a large number of zero entries

Bus Admittance Matrix or Y_{bus}

- First step in solving the power flow is to create what is known as the bus admittance matrix, often called the Y_{bus} .
- The Y_{bus} gives the relationships between all the bus current injections, I , and all the bus voltages, V , $I = Y_{bus} V$
- The Y_{bus} is developed by applying KCL at each bus in the system to relate the bus current injections, the bus voltages, and the branch impedances and admittances.

Bus Admittance Matrix

- Let bus j be an arbitrary bus

$$\sum_{i=1}^n I_{ji} = I_j$$

where I_j = injected current at bus j

I_{ij} = current leaving bus j to bus i

- Branch current I_{ji}

$$I_{ji} = y_{ji} (V_j - V_i)$$

$$y_{ij} = \frac{1}{z_{ij}} = \frac{1}{r_{ij} + j x_{ij}}$$

where y_{ij} = line admittance from bus j to bus i

V_j, V_i = bus voltages

Bus Admittance Matrix

- Injected current I_j

$$I_j = \sum_{i=1}^n y_{ji} (V_j - V_i)$$

- n equations

$$I_1 = \left(\sum_{i=1}^n y_{1i} \right) V_1 + (-y_{12}) V_2 + \cdots + (-y_{1n}) V_n$$

$$I_2 = (-y_{21}) V_1 + \left(\sum_{i=1}^n y_{2i} \right) V_2 + \cdots + (-y_{2n}) V_n$$

⋮

$$I_n = (-y_{n1}) V_1 + (-y_{n2}) V_2 + \cdots + \left(\sum_{i=1}^n y_{ni} \right) V_n$$

Ybus Building Algorithm

- “Inspection” method
- Diagonal entries Y_{jj} : summing the **primitive admittance** of lines and ties to the reference at bus j ($Y_{jj} = \sum_i^n y_{ji}$)
- Off diagonal entries Y_{ij} : the negatives of the admittances of lines between buses i and j
($Y_{ji} = Y_{ij} = -y_{ij}$)
- If there is no line between i and j , this term is zero


Properties of Ybus Matrix

- The matrix is complex and symmetric
- The matrix is sparse since each bus is connected to only a few nearby buses
- The percent sparsity increases with the matrix dimension
- If there is a nonzero admittance tie to the reference bus, Ybus is nonsingular
- If there are no ties to the reference bus, Ybus is singular

Y_{bus} -Summary


- The diagonal terms, Y_{jj} , are the “self admittance” terms, equal to the sum of the admittances of all devices incident to bus k .
- The off-diagonal terms, Y_{ij} , are equal to the negative of the admittance joining the two buses.
- With large systems Y_{bus} is a sparse matrix (that is, most entries are zero):
 - sparsity is key to efficient numerical calculation.
- Shunt terms, such as in the equivalent π line model, only affect the diagonal terms.

Example 1

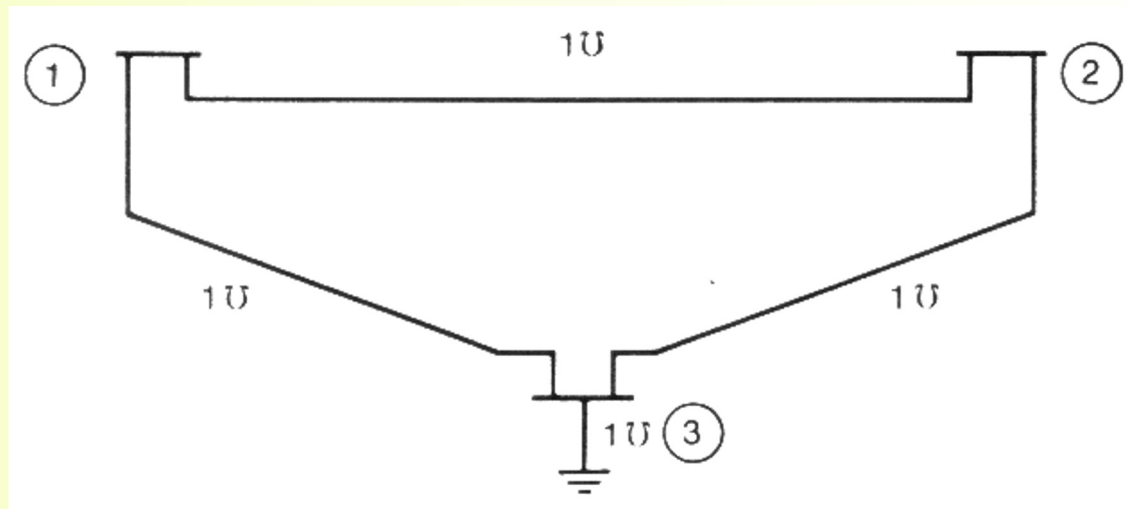


$$\begin{array}{c}
 \textcircled{1} \quad \textcircled{2} \quad \textcircled{3} \\
 \textcircled{1} \begin{bmatrix} 1+1 & -1 & -1 \\ -1 & 1+1 & -1 \\ -1 & -1 & 1+1+1 \end{bmatrix} \\
 \textcircled{2} \\
 \textcircled{3}
 \end{array}
 = \begin{bmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

Example 2

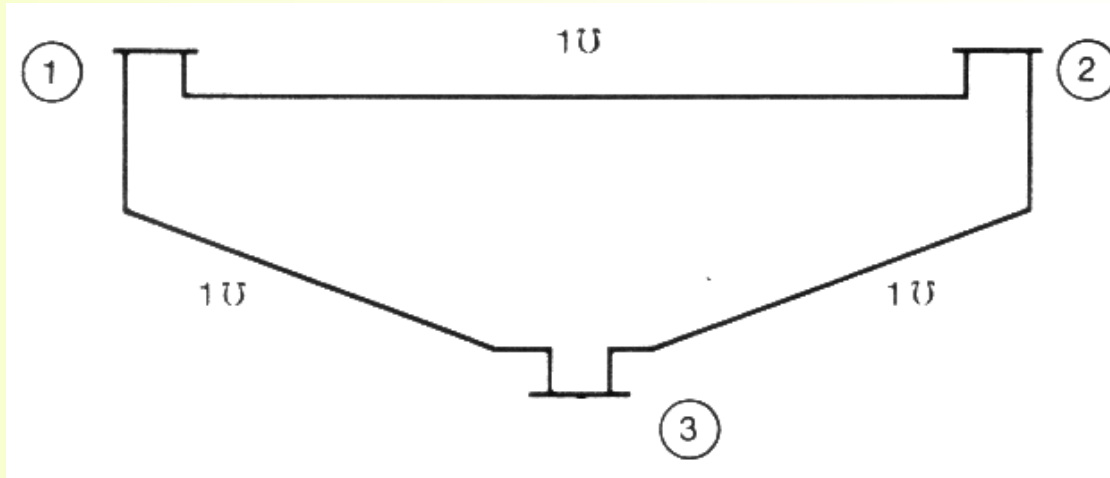


$$\begin{array}{c}
 \textcircled{1} \quad \textcircled{2} \quad \textcircled{3} \\
 \textcircled{1} \quad \begin{bmatrix} 1+1 & -1 & -1 \\ -1 & 1+1 & -1 \\ -1 & -1 & 1+1 \end{bmatrix} \\
 \textcircled{2} \\
 \textcircled{3}
 \end{array}
 = \begin{bmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 2 \end{bmatrix}$$

Example 3

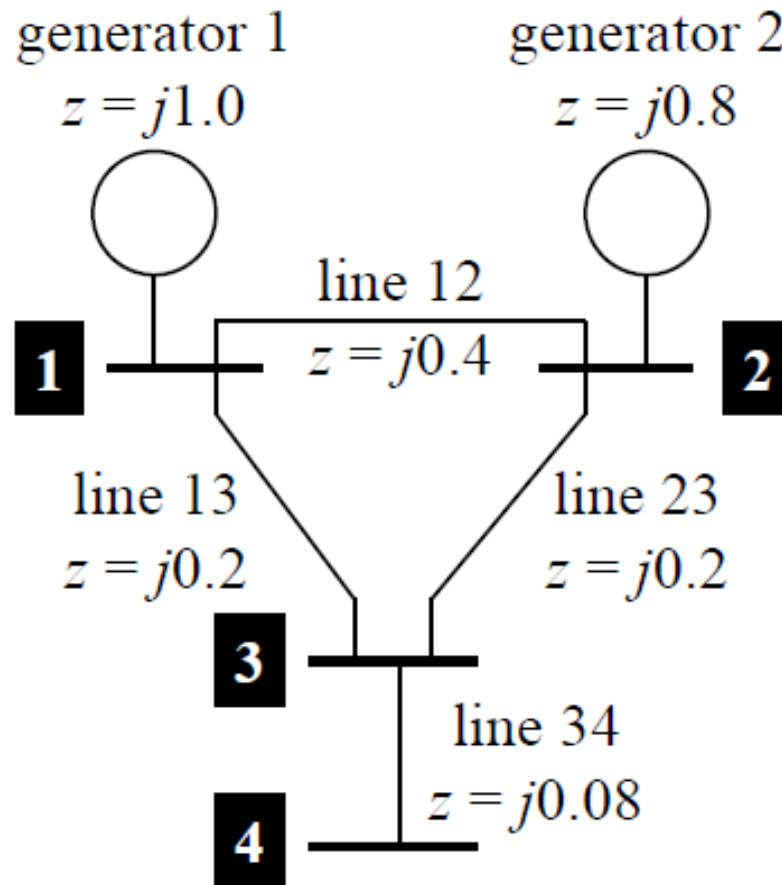


Network Diagram

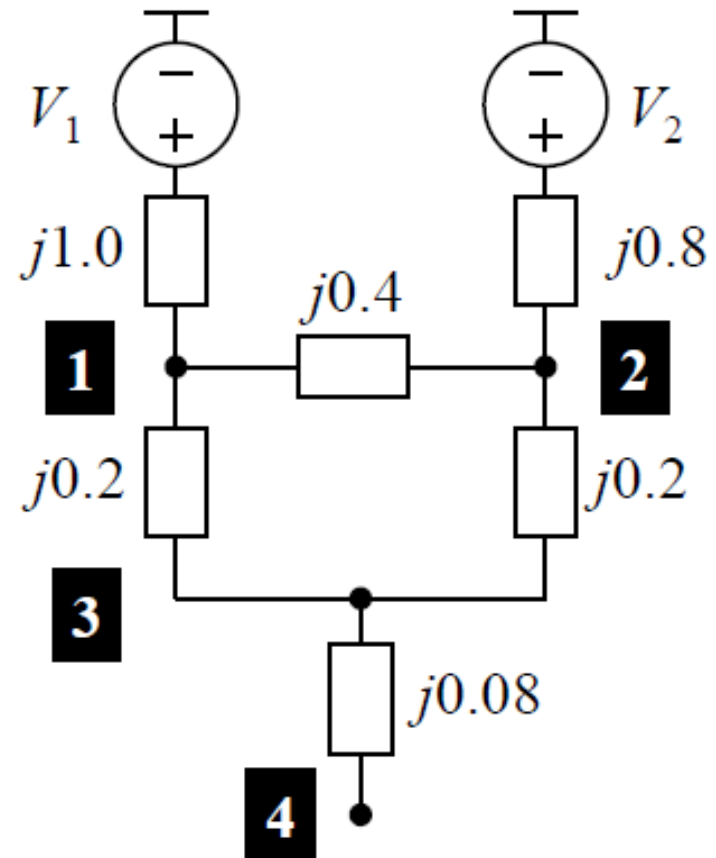

Impedance Diagram

Example 3

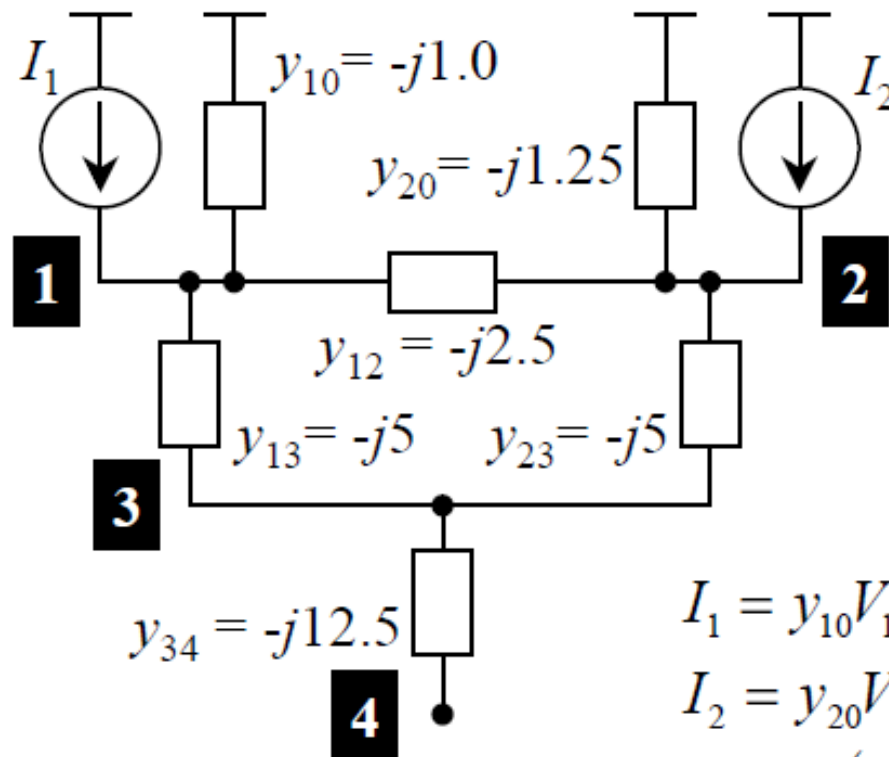

Admittance Diagram

KCL Equations

$$I_1 = y_{10}V_1 + y_{12}(V_1 - V_2) + y_{13}(V_1 - V_3)$$

$$I_2 = y_{20}V_2 + y_{21}(V_2 - V_1) + y_{23}(V_2 - V_3)$$

$$0 = y_{31}(V_3 - V_1) + y_{32}(V_3 - V_2) + y_{34}(V_3 - V_4)$$

$$0 = y_{43}(V_4 - V_3)$$

Example 3

Rearranging the KCL Equations

$$I_1 = (y_{10} + y_{12} + y_{13})V_1 - y_{12}V_2 - y_{13}V_3$$

$$I_2 = -y_{21}V_1 + (y_{20} + y_{21} + y_{23})V_2 - y_{23}V_3$$

$$0 = -y_{31}V_1 - y_{32}V_2 + (y_{31} + y_{32} + y_{34})V_3 - y_{34}V_4$$

$$0 = -y_{43}V_3 + y_{43}V_4$$

Matrix Formation of the Equations

$$\begin{bmatrix} I_1 \\ I_2 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} (y_{10} + y_{12} + y_{13}) & -y_{12} & -y_{13} & 0 \\ -y_{21} & (y_{20} + y_{21} + y_{23}) & -y_{23} & 0 \\ -y_{31} & -y_{32} & (y_{31} + y_{32} + y_{34}) & -y_{34} \\ 0 & 0 & -y_{43} & y_{43} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$


Example 3

Completed Matrix Equation

$$\begin{aligned}
 Y_{11} &= (y_{10} + y_{12} + y_{13}) = -j8.50 & Y_{23} &= Y_{32} = -y_{23} = j5.00 \\
 Y_{12} &= Y_{21} = -y_{12} = j2.50 & Y_{33} &= (y_{31} + y_{32} + y_{34}) = -j22.50 \\
 Y_{13} &= Y_{31} = -y_{13} = j5.00 & Y_{34} &= Y_{43} = -y_{34} = j12.50 \\
 Y_{22} &= (y_{20} + y_{21} + y_{23}) = -j8.75 & Y_{44} &= y_{34} = -j12.50
 \end{aligned}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -j8.50 & j2.50 & j5.00 & 0 \\ j2.50 & -j8.75 & j5.00 & 0 \\ j5.00 & j5.00 & -j22.50 & j12.50 \\ 0 & 0 & j12.50 & -j12.50 \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

Modeling Shunts in Y_{bus}

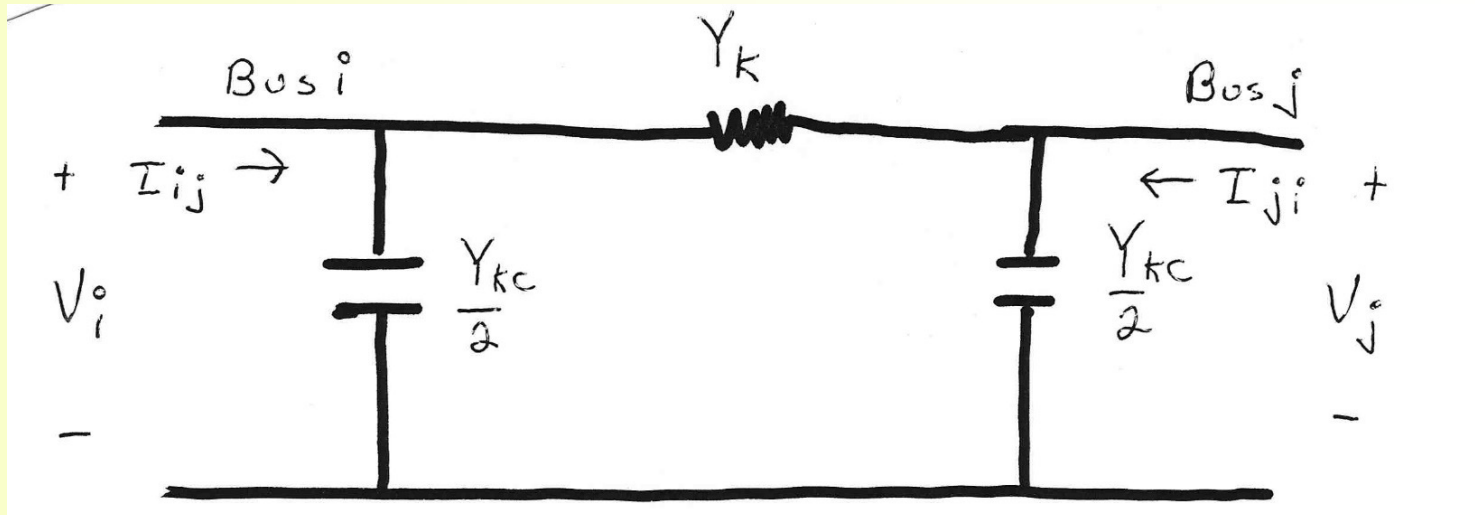


Since
$$I_{ij} = (V_i - V_j)Y_k + V_i \frac{Y_{kc}}{2}$$

$$Y_{ii} = Y_{ii}^{\text{from other lines}} + Y_k + \frac{Y_{kc}}{2}$$

Note
$$Y_k = \frac{1}{Z_k} = \frac{1}{R_k + jX_k} \frac{R_k - jX_k}{R_k - jX_k} = \frac{R_k - jX_k}{R_k^2 + X_k^2}$$

Example 4

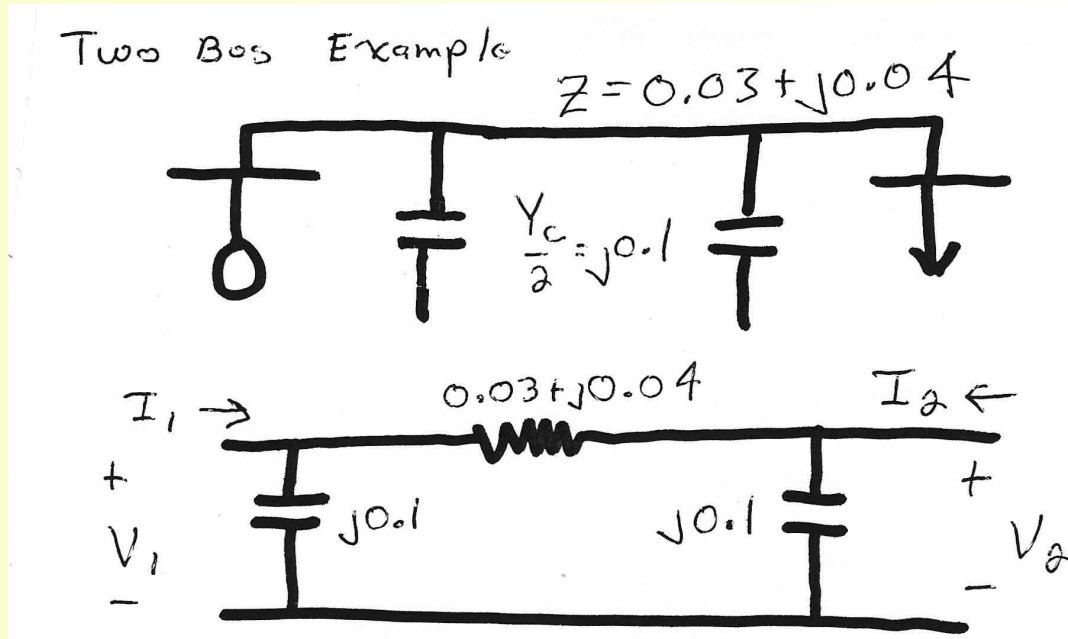

$$I_1 = \frac{(V_1 - V_2)}{Z} + V_1 \frac{Y_c}{2}, \text{ where } \frac{1}{Z} = \frac{1}{0.03 + j0.04} = 12 - j16.$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 - j15.9 & -12 + j16 \\ -12 + j16 & 12 - j15.9 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Using the $\mathbf{Y}_{\text{bus}}$

If the voltages are known then we can solve for the current injections:

$$\mathbf{Y}_{\text{bus}} \mathbf{V} = \mathbf{I}$$

If the current injections are known then we can solve for the voltages:

$$\mathbf{Y}_{\text{bus}}^{-1} \mathbf{I} = \mathbf{V} = \mathbf{Z}_{\text{bus}} \mathbf{I}$$

where $\mathbf{Z}_{\text{bus}} = \mathbf{Y}_{\text{bus}}^{-1}$ is the bus impedance matrix.

Example 5: Solving for Bus Currents

For example, in previous case assume:

$$\mathbf{V} = \begin{bmatrix} 1.0 \\ 0.8 - j0.2 \end{bmatrix}.$$

Then

$$\begin{bmatrix} 12 - j15.9 & -12 + j16 \\ -12 + j16 & 12 - j15.9 \end{bmatrix} \begin{bmatrix} 1.0 \\ 0.8 - j0.2 \end{bmatrix} = \begin{bmatrix} 5.60 - j0.70 \\ -5.58 + j0.88 \end{bmatrix}$$

Therefore the power injected at bus 1 is:

$$S_1 = V_1 I_1^* = 1.0 \times (5.60 + j0.70) = 5.60 + j0.70$$

$$S_2 = V_2 I_2^* = (0.8 - j0.2) \times (-5.58 - j0.88) = -4.64 + j0.41$$

Example 6: Solving for Bus Voltages

As another example, in previous case assume

$$\mathbf{I} = \begin{bmatrix} 5.0 \\ -4.8 \end{bmatrix}.$$

Then

$$\begin{bmatrix} 12 - j15.9 & -12 + j16 \\ -12 + j16 & 12 - j15.9 \end{bmatrix}^{-1} \begin{bmatrix} 5.0 \\ -4.8 \end{bmatrix} = \begin{bmatrix} 0.0738 - j0.902 \\ -0.0738 - j1.098 \end{bmatrix}$$

Therefore the power injected is

$$S_1 = V_1 I_1^* = (0.0738 - j0.902) \times 5 = 0.37 - j4.51$$

$$S_2 = V_2 I_2^* = (-0.0738 - j1.098) \times (-4.8) = 0.35 + j5.27$$

Modifications in Bus Admittance Matrix

Line Outages

■ Line outages

- Let Y_{bus} be given for a system in which a line is to be outaged
- The line outage is equivalent to adding a new line of admittance $-y_{out}$ in parallel with the line to be outaged
- The combination of y_{out} and $-y_{out}$ is a zero admittance (open circuit)

■ Procedure

- Diagonal entries: Add $-y_{out}$ to the ii and jj entries
- Off diagonal entries: Add y_{out} to the ij and ji entries

Deletion of a Bus-Kron Reduction

- A system of n buses in which m buses to be deleted ($m < n$)
- Partition I_{bus} and V_{bus}

$$I_{bus} = \left[\begin{array}{c} I_a \\ \dots \\ I_b \end{array} \right] \left\{ \begin{array}{l} n-m \\ m \end{array} \right.$$

$$V_{bus} = \left[\begin{array}{c} V_a \\ \dots \\ V_b \end{array} \right] \left\{ \begin{array}{l} n-m \\ m \end{array} \right.$$

- Deleted buses = no injected currents
 - Let $I_b = 0$

Deletion of a Bus-Kron Reduction

- Need to find an equivalent admittance matrix with m buses deleted
 - Note: the equivalent admittance matrix is $(n-m) \times (n-m)$

$$I_{bus} = Y_{bus} V_{bus}$$

$$\begin{bmatrix} I_a \\ I_b \end{bmatrix} = \begin{bmatrix} Y_{aa} & Y_{ab} \\ Y_{ab}^T & Y_{bb} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} \quad \left. \begin{array}{l} \left. \begin{array}{l} \left. \begin{array}{l} Y_{aa} \\ Y_{ab} \end{array} \right\} \right\} n-m \\ \left. \begin{array}{l} Y_{ab}^T \\ Y_{bb} \end{array} \right\} m \end{array} \right\}$$

Deletion of a Bus-Kron Reduction

- Set $I_b = 0$ and eliminate V_b

$$I_b = 0 = Y_{ab}^T V_a + Y_{bb} V_b$$

$$V_b = -Y_{bb}^{-1} Y_{ab}^T V_a \quad \Rightarrow \quad \mathbf{Y}_{bb} \text{ is assumably invertible}$$

- Substitute V_b in n-m rows


$$I_a = Y_{aa} V_a + Y_{ab} V_b$$

$$= Y_{aa} V_a - Y_{ab} Y_{bb}^{-1} Y_{ab}^T V_a$$

$$= \underbrace{\left[Y_{aa} - Y_{ab} Y_{bb}^{-1} Y_{ab}^T \right]}_{Y_{bus}^{eq}} V_a$$

Example 1

For the two-bus system given below.

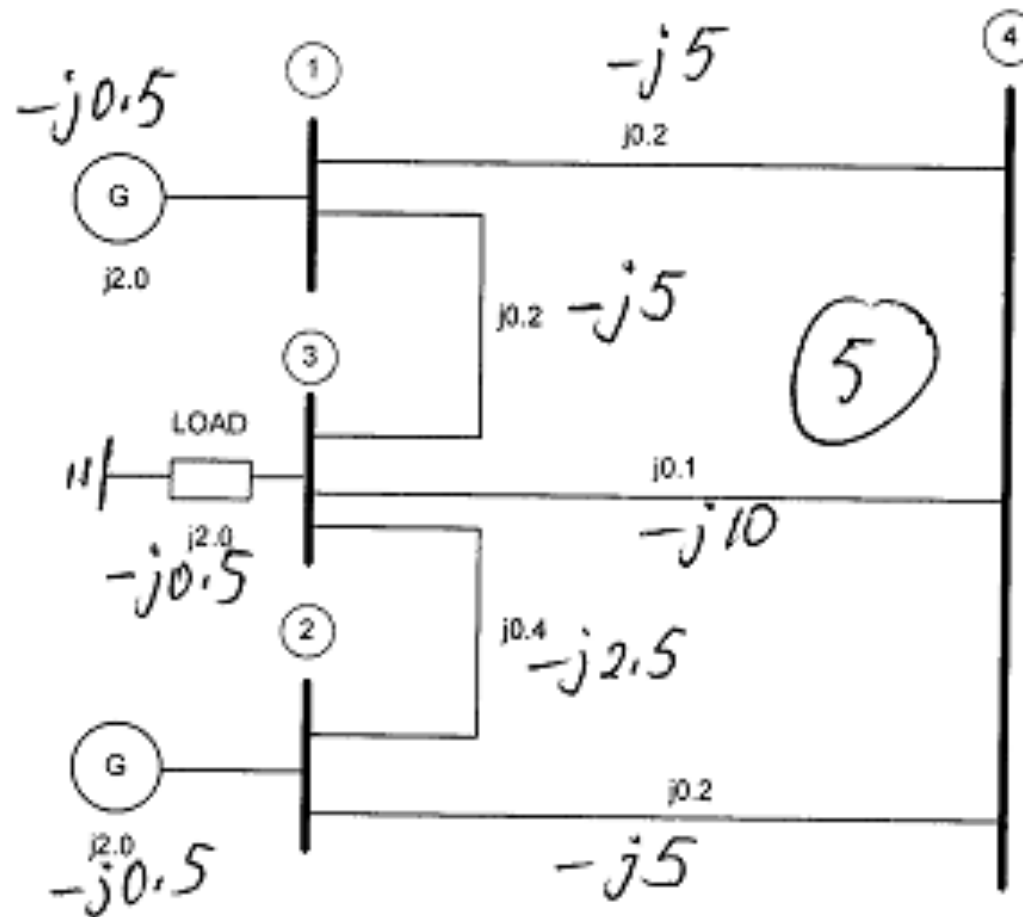

- Find Y_{bus} matrix (15).
- Eliminate buses 3 and 4 using Kron Reduction method (15).
- Find the reactances of generators and the line of the reduced 2-bus system (5).

Example 1: Solution

Find the reactances of generators and the

a) $Y_{bus} = \begin{bmatrix} \textcircled{1} & \textcircled{2} \\ \textcircled{3} & \textcircled{4} \end{bmatrix} = \begin{bmatrix} -j10.5 & 0 & j5 & j5 \\ 0 & -j8 & j2.5 & j5 \\ j5 & j2.5 & -j18 & j10 \\ j5 & j5 & j10 & -j20 \end{bmatrix}$

b) $Y_{aa} = \begin{bmatrix} -j10.5 & 0 \\ 0 & -j8 \end{bmatrix}$

$Y_{ab} = \begin{bmatrix} j5 & j5 \\ j2.5 & j5 \end{bmatrix}$

$Y_{ba} = \begin{bmatrix} j5 & j2.5 \\ j5 & j5 \end{bmatrix}$

$Y_{bb} = \begin{bmatrix} -j18 & j10 \\ j10 & -j20 \end{bmatrix}$

$Y_{red} = Y_{aa} - Y_{ab} Y_{bb}^{-1} Y_{ba}$

$Y_{bb}^{-1} = \frac{1}{(-260)} \begin{bmatrix} -j20 & -j10 \\ -j10 & -j18 \end{bmatrix}$

19.03.2024

$Y_{bb}^{-1} = \begin{bmatrix} j0.0769 & j0.0385 \\ j0.0385 & j0.0692 \end{bmatrix}$

$Y_{ab} Y_{bb}^{-1} Y_{ba} = \begin{bmatrix} -j5.575 & -j4.135 \\ -j4.135 & -j3.173 \end{bmatrix}$

$Y_{red} = \begin{bmatrix} -j4.925 & j4.135 \\ j4.135 & -j4.827 \end{bmatrix}$

c) X_{G1}, X_{G2}

$Y_{12} = j4.135 \rightarrow y_{12} = -j4.135$

$X_{12} = j0.242 \text{ pu}$

$y_{G1} = -j4.925 + j4.135 = -j0.79 \text{ pu}$

$y_{G2} = -j4.827 + j4.135 = -j0.692 \text{ pu}$

$X_{G1} = \frac{1}{-j0.79} = j1.266 \text{ pu}$

$X_{G2} = \frac{1}{-j0.692} = j1.445 \text{ pu}$


Sayasun

Example 2

Name-Last name:
Department:
Student ID #:

SAYASUN

2

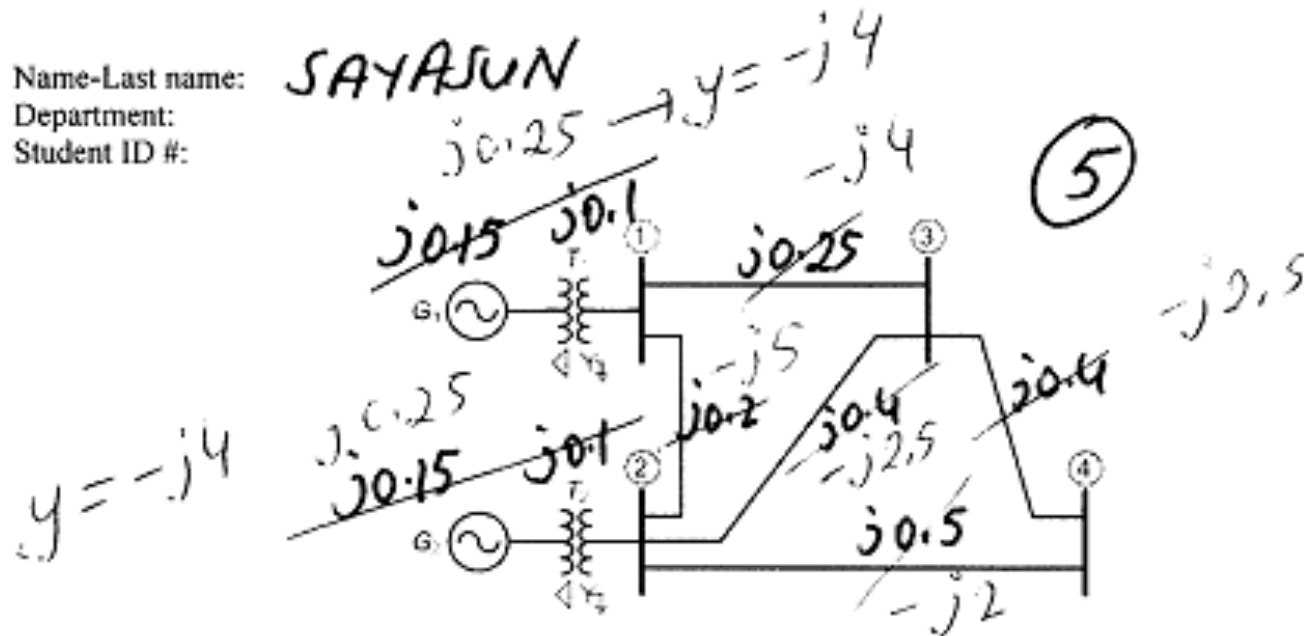

G1 and G2: $x = j0.15$ pu, T₁ and T₂: $x = j0.1$ pu, Lines: $x_{12} = j0.2$ pu, $x_{13} = j0.25$ pu, $x_{23} = x_{34} = j0.4$ pu and $x_{24} = j0.5$ pu

2. For the power system given above

a) Find Y_{bus} matrix (15 pts).

b) Eliminate the bus# 3 and 4 using Kron Reduction method (15 pts).

c) Find the reactances of generators and the line of the 2-bus reduced system (5 pts)

$$I_a = Y_{aa} V_a + Y_{ab} V_b$$

$$0 = Y_{ab}^T V_a + Y_{bb} V_b$$

Example 2: Solution

a) $Y_{BUS} = \begin{bmatrix} \textcircled{1} & \textcircled{2} & \textcircled{3} & \textcircled{4} \\ \textcircled{1} & -j13 & j5 & j4 \\ \textcircled{2} & j5 & -j13.5 & j2.5 \\ \textcircled{3} & j4 & j2.5 & -j9 \\ \textcircled{4} & 0 & j2 & j2.5 - j4.5 \end{bmatrix} Y_{ab}$

b) $Y_{bus}^{red} = Y_{aa} - Y_{ab} Y_{bb}^{-1} Y_{ab}^T$

$Y_{bb} = \begin{bmatrix} -j9 & j2.5 \\ j2.5 & -j4.5 \end{bmatrix}$

$Y_{bb}^{-1} = \frac{1}{(-34.25)} \begin{bmatrix} -j4.5 & -j2.5 \\ -j2.5 & -j9 \end{bmatrix}$

$Y_{bb}^{-1} = \begin{bmatrix} j0.13 & j0.073 \\ j0.073 & j0.26 \end{bmatrix}$ 5

$Y_{ab} Y_{bb}^{-1} Y_{ab}^T = \begin{bmatrix} j4 & 0 \\ j2.5 & j2 \end{bmatrix} \begin{bmatrix} j0.13 & j0.073 \\ j0.073 & j0.26 \end{bmatrix} \begin{bmatrix} j4 & j2.5 \\ 0 & j2 \end{bmatrix}$

19.03.2024

$Y_{ab} Y_{bb}^{-1} Y_{ab}^T = \begin{bmatrix} -j2.08 & -j1.884 \\ -j1.884 & -j2.583 \end{bmatrix}$ 5

$Y_{bus}^{red} = Y_{aa} - Y_{ab} Y_{bb}^{-1} Y_{ab}^T$

$Y_{bus}^{red} = \begin{bmatrix} -j13 & j5 \\ j5 & -j13.5 \end{bmatrix} - \begin{bmatrix} -j2.08 & -j1.884 \\ -j1.884 & -j2.583 \end{bmatrix}$

$Y_{bus}^{red} = \begin{bmatrix} -j10.92 & j6.88 \\ j6.88 & -j10.92 \end{bmatrix}$ 5

c) $y_{12} = y_{21} = -j6.88 \text{ pu}$

Thus, $X_{12} = \frac{1}{-j6.88} = j0.145 \text{ pu}$

$-j4.04$ $-j6.88$ $-j4.04 \text{ pu}$

5

$X_{G1} = X_{G2} = \frac{1}{-j4.04} = j0.248 \text{ pu}$


$j0.248$ 1 $j0.145 \text{ pu}$ 2 $j0.248$

Example 3

Student ID #:

POWER SYSTEM ANALYSIS
2017-2018 FALL TERM MIDTERM EXAM, Nov. 05, 2017
100 MINUTES, PLEASE SHOW ALL YOUR EFFORTS.
GOOD LUCK!!!
PROF. DR. SAFFET AYASUN

Q #	1	2	3	Total
Points	/35	/30	/35	/100

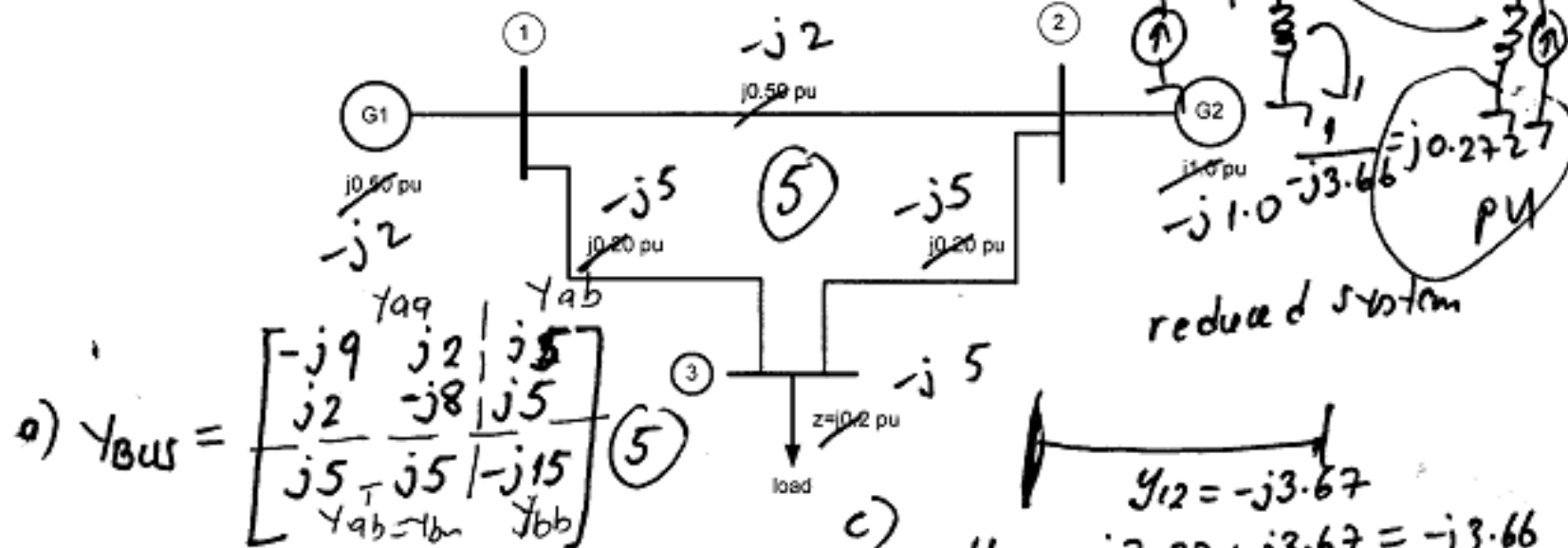

1. For the power system given above

a) Find Y_{bus} matrix (10 pts).

b) Eliminate the bus#3 using Kron Reduction method (10 pts).

c) Find bus voltages V_1 and V_2 if current injections are

$I_1 = 1.0$ pu and $I_2 = 1.2 \angle -10^\circ$ pu (10 pts)

d) Find the reactances of generators and the line of the 2-bus reduced system (5 pts)

Example 3: Solution

b)

$$Y_{red} = Y_{aa} - Y_{ab} Y_{bb}^{-1} Y_{ab}$$

$$= \begin{bmatrix} -j9 & j2 \\ j2 & -j8 \end{bmatrix} - \begin{bmatrix} j5 \\ j5 \end{bmatrix} \left(\frac{1}{-j15} \right) \begin{bmatrix} j5 & j5 \end{bmatrix}$$

$$= \begin{bmatrix} -j9 & j2 \\ j2 & -j8 \end{bmatrix} + \begin{bmatrix} j1.67 & j1.67 \\ j1.67 & j1.67 \end{bmatrix}$$

$$= \begin{bmatrix} -j7.33 & j3.67 \\ j3.67 & -j6.33 \end{bmatrix} \quad (5)$$

c) $I = Y V$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = Y^{-1} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$= \begin{bmatrix} -j7.33 & j3.67 \\ j3.67 & -j6.33 \end{bmatrix}^{-1} \begin{bmatrix} 1.0 \\ 1.2 \angle -10^\circ \end{bmatrix}$$

$$= \begin{bmatrix} j0.192 & j0.111 \\ j0.111 & j0.223 \end{bmatrix} \begin{bmatrix} 1.0 \\ 1.2 \angle -10^\circ \end{bmatrix}$$

$$= \begin{bmatrix} 0.324 \angle 85.93^\circ \\ 0.378 \angle 82.95^\circ \end{bmatrix} \text{ pu}$$

Example 4

Department:
Student ID #:

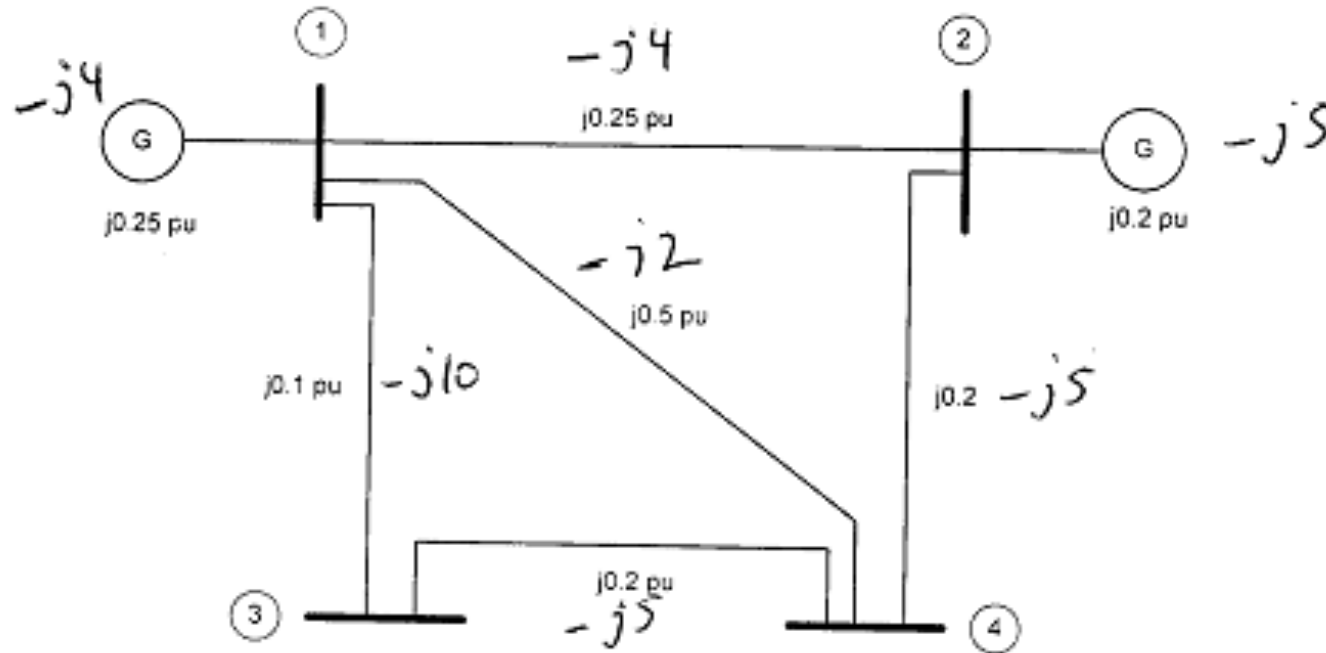

2. For the power system given above
 - a) Find Y_{bus} matrix (10 pts).
 - b) Eliminate buses 3 and 4 using Kron Reduction method (15 pts).

Example 4: Solution

a)

$$Y_{11} = -j4 - j4 - j2 - j10 = -j20 \text{ pu}$$

$$Y_{22} = -j5 - j5 - j4 = -j14 \text{ pu}$$

$$Y_{33} = -j10 - j5 = -j15 \text{ pu}$$

$$Y_{44} = -j5 - j2 - j5 = -j12$$

$$Y_{\text{Bus}} = \begin{bmatrix} \textcircled{1} & \textcircled{2} & \textcircled{3} & \textcircled{4} \\ \textcircled{1} & -j20 & j4 & j10 \\ \textcircled{2} & j4 & -j14 & 0 \\ \textcircled{3} & j10 & 0 & -j15 \\ \textcircled{4} & j2 & j5 & -j12 \end{bmatrix}$$

b)

$$Y_{aa} = \begin{bmatrix} -j20 & j4 \\ j4 & -j14 \end{bmatrix}$$

$$Y_{ab} = \begin{bmatrix} j10 & j2 \\ 0 & j5 \end{bmatrix}$$

$$Y_{ah}^T = \begin{bmatrix} j10 & 0 \\ j2 & j5 \end{bmatrix}, \quad Y_{bb} = \begin{bmatrix} -j15 & j5 \\ j5 & -j12 \end{bmatrix}$$

$$Y_{\text{red}} = Y_{aa} - Y_{ab} Y_{bb}^{-1} Y_{ah}^T$$

$$Y_{bb}^{-1} = \frac{1}{-155} \begin{bmatrix} -j12 & -j5 \\ -j5 & -j15 \end{bmatrix} = \begin{bmatrix} j0.077 & j0.032 \\ j0.032 & j0.097 \end{bmatrix}$$

$$Y_{ab} Y_{bb}^{-1} Y_{ah}^T = \begin{bmatrix} -j9.363 & -j2.57 \\ -j2.57 & -j2.425 \end{bmatrix}$$

$$Y_{\text{red}} = \begin{bmatrix} j20 & j4 \\ j4 & -j14 \end{bmatrix} - \begin{bmatrix} -j9.363 & -j2.57 \\ -j2.57 & -j2.425 \end{bmatrix}$$


$$Y_{\text{red}} = \begin{bmatrix} -j10.632 & j6.57 \\ j6.57 & -j11.575 \end{bmatrix}$$

Example 5

Name/Last Name:
Student ID #:
Signature:

3

3. For the two-bus system given below.

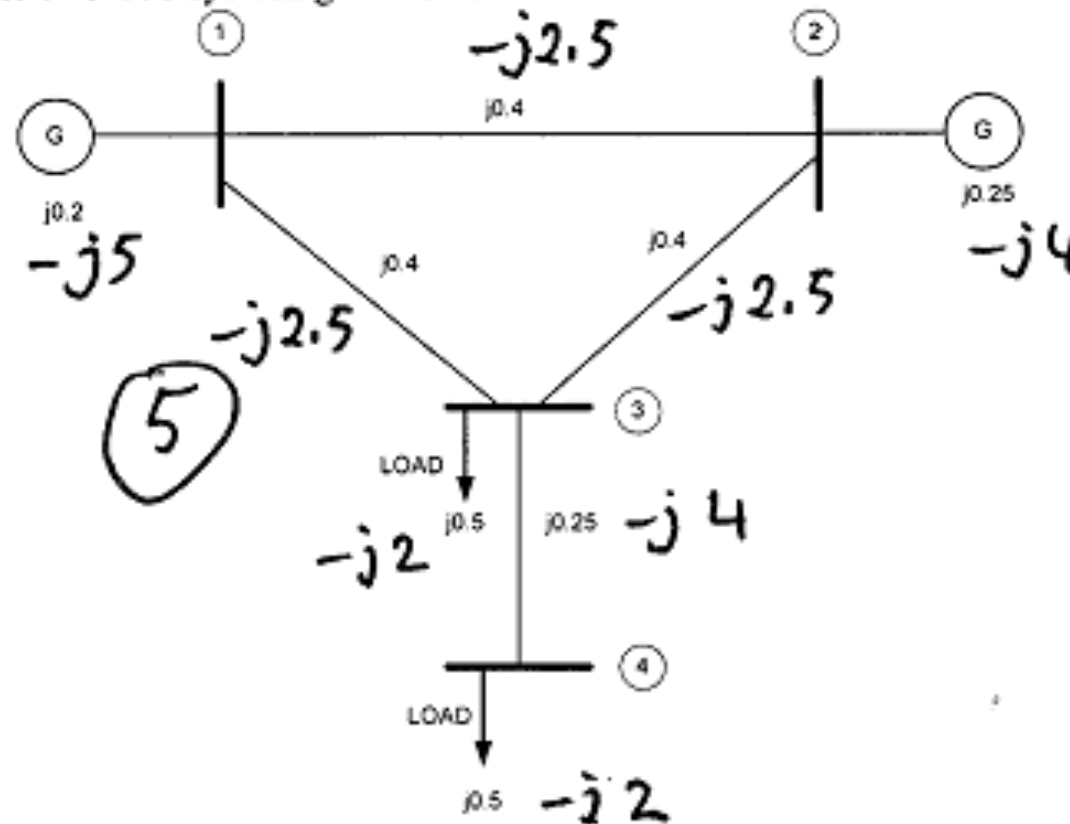

a) Find Y_{bus} matrix (15).

b) Eliminate buses 3 and 4 using Kron Reduction method (15).

Example 5: Solution

b) Eliminate buses 3 and 4 using Kron Reduction method (15).

$$a) Y_{bus} = \begin{bmatrix} \textcircled{1} & \textcircled{2} & \textcircled{3} & \textcircled{4} \\ -j10 & j2.5 & j2.5 & 0 \\ j2.5 & -j9 & j2.5 & 0 \\ j2.5 & j2.5 & -j11 & j4 \\ 0 & 0 & j4 & -j6 \end{bmatrix}$$

(10)

$$b) Y_{bb} = \begin{bmatrix} -j11 & j4 \\ j4 & -j6 \end{bmatrix}$$

$$Y_{bb}^{-1} = -\frac{1}{50} \begin{bmatrix} -j6 & -j4 \\ -j4 & -j11 \end{bmatrix}$$

$$Y_{bb}^{-1} = \begin{bmatrix} j0.12 & j0.08 \\ j0.08 & j0.22 \end{bmatrix} \textcircled{5}$$

$$Y^{red} = Y_{aa} - Y_{ab} Y_{bb}^{-1} Y_{ba}$$

$$Y_{bb}^{-1} Y_{ab} = \begin{bmatrix} j0.12 & j0.08 \\ j0.08 & j0.22 \end{bmatrix} \begin{bmatrix} j2.5 & j2.5 \\ 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} j0.3 & -j0.3 \\ -j0.2 & -j0.2 \end{bmatrix} \quad (-) \quad \text{sign !!}$$

$$Y_{bb}^{-1} Y_{ab} Y_{ba} = \begin{bmatrix} j2.5 & 0 \\ j2.5 & 0 \end{bmatrix} \begin{bmatrix} j0.3 & -j0.3 \\ -j0.2 & -j0.2 \end{bmatrix} \textcircled{5}$$

$$= \begin{bmatrix} -j0.75 & -j0.75 \\ -j0.75 & -j0.75 \end{bmatrix}$$

$$Y^{red} = \begin{bmatrix} -j10 & j2.5 \\ j2.5 & -j9 \end{bmatrix} - \begin{bmatrix} -j0.75 & -j0.75 \\ -j0.75 & -j0.75 \end{bmatrix}$$

$$= \begin{bmatrix} -j9.25 & j3.25 \\ j3.25 & -j8.25 \end{bmatrix} \textcircled{5}$$